

A HOME-BUILT FREQUENCY SYNTHESIZER FOR 45 TO 75MHz

John Crawley, GM3LBX*

(PART 2)

Section F. Loop 1 mixer and bandpass filter (Fig 12)

The buffered input to pin 3 of IC601 is from the selected vco in loop 1 (section A Fig 6) and will be between 45-75MHz. The amplitude at pin 3 should be approximately 50mV peak-to-peak. The input to pin 7 is from the 42MHz filter via the buffer TR602 and TR603. The amplitude need only be about equal to that on pin 3.

The bandpass filter L601-604 is designed to pass 2.5MHz up to 33MHz, and to reject frequencies above and below this band—particularly the 45-75MHz band, and the 42MHz component from loop 2.

The inductances L602 and 603 are Toko 10K formers wound with eight turns 32swg copper wire and mounted in screening cans. They have adjustable cores and a pot-core. L601 and 604 are Toko 3335R.

The filter should be adjusted by injecting a variable frequency into the empty socket of pin 5 of IC601 and monitoring the output. Adjust cores for a sharp cut-off above 35MHz.

Section G. Second loop vco etc (Fig 13)

The circuit for IC702 is similar to that in section E, except that it needs no crystal and that the reference frequency is divided down to 400Hz by using the highest available divisor, 8,192; this is programmed by leaving pins 5, 6 and 7 high.

The section is sited on the right centre of the pcb. L701 is a Toko Style MC120 No 100075. It has a screened inductance of 0.17µH. This vco (T603) should be tested after assembly to see that it runs in the region of 95MHz.

When checking the MC145151 here, and in the other place where it is used, there are two useful guides to what is going on inside it. Pin 10 is connected internally to the output of the main divider so that when all is well, this should be showing the reference frequency (400Hz in this case) if a counter is placed on the pin. Pin 28 is a lock detector output. It is high when the loop is locked and pulses low when out of lock. Some constructors may wish to use this pin to drive a l.e.d. indicator to show when the loop is locked.

Section H. Loop two mixer and 6-4 filter (Fig 14)

TR801 buffers the input to pin 3 of the SL1640. The frequency at "n" and pin 3 should be between 95.3876 and 95.6432MHz when the loop is locked. TR802 is a tuned buffer to double the 44-545MHz from section C. The tuned circuit is L803 (12 turns of 28swg wire on a 1MΩ resistor 0.25W and a 2.8-12pF ceramic trimmer). The bandpass filter has two inductances of 15 turns, 32swg insulated copper wire on Toko 10K formers. Ready-wound devices such as 10K SW1 KANK3333 would do the job. The filter should be tuned to 6.4MHz sited in the middle of the right-hand edge of the pcb. Layout as in Fig 7.


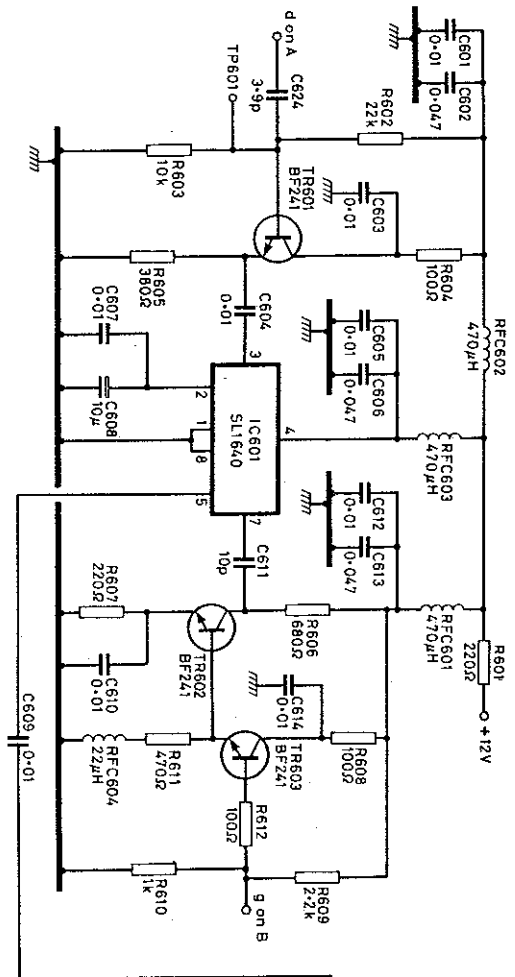


Fig 12. Section F. Mixer and broadband filter

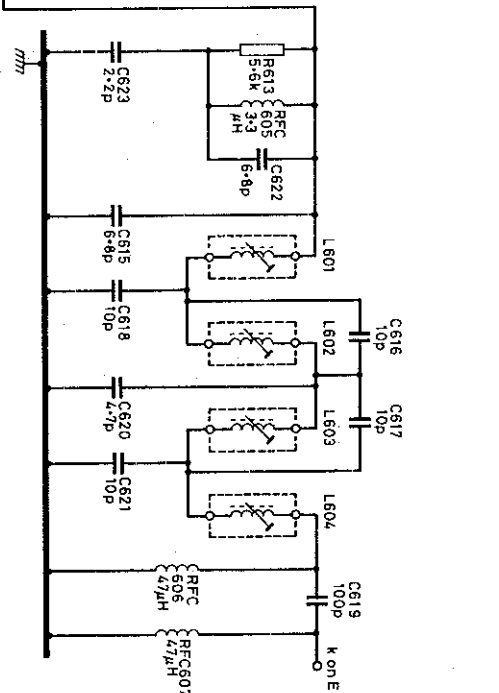

*Cove, Campbeltown Road, Tarbert, Argyll PA29 6SX

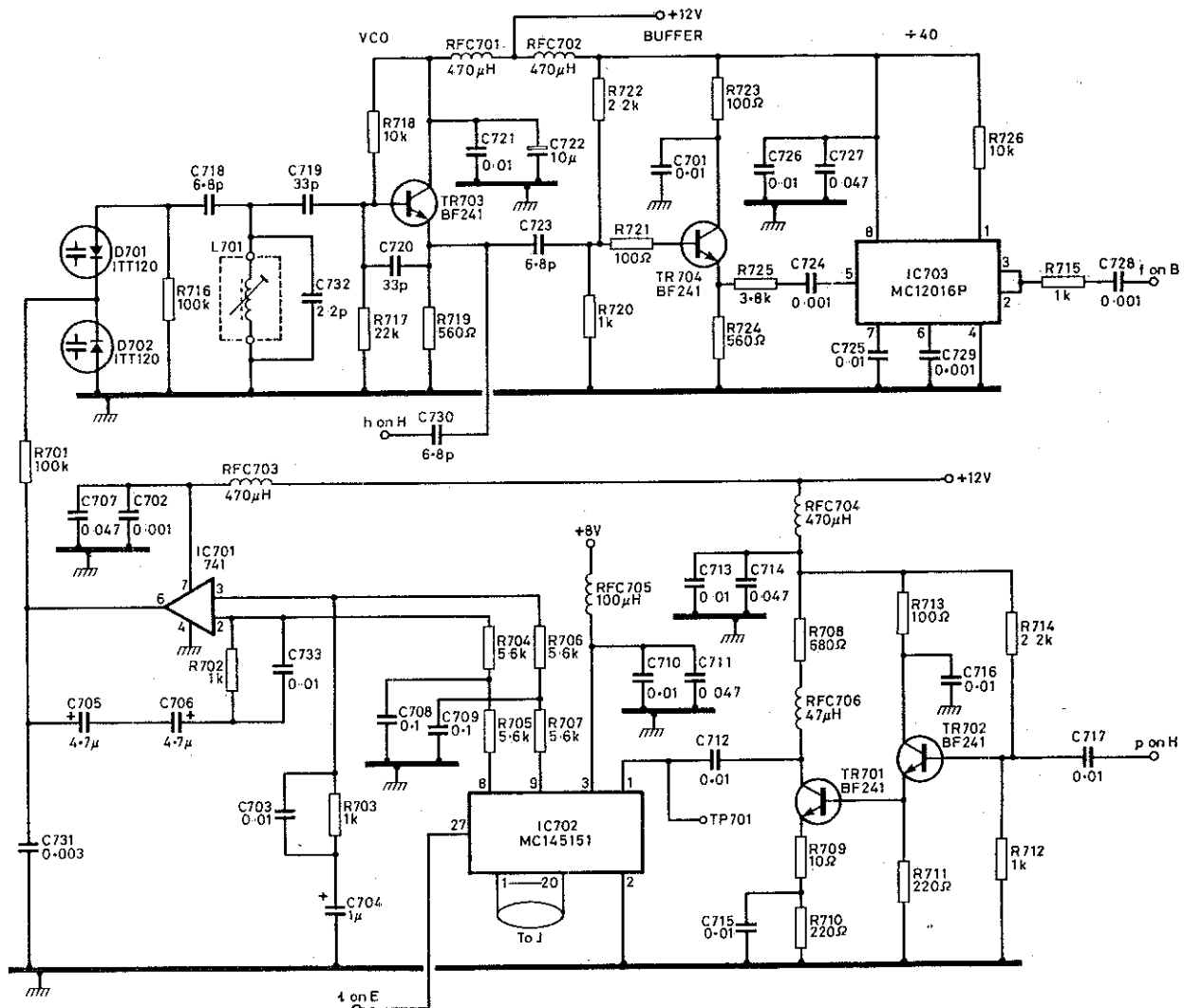


Fig 13. Section G. Second loop phase discriminator and lpf


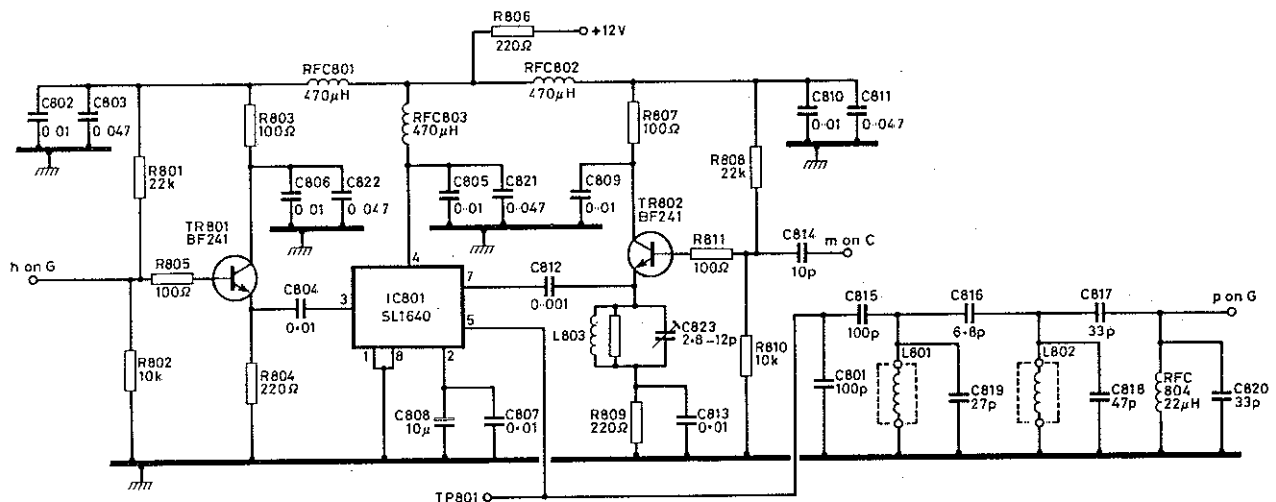



Fig 14. Section H. The mixer and 6-4MHz filter in Loop 2

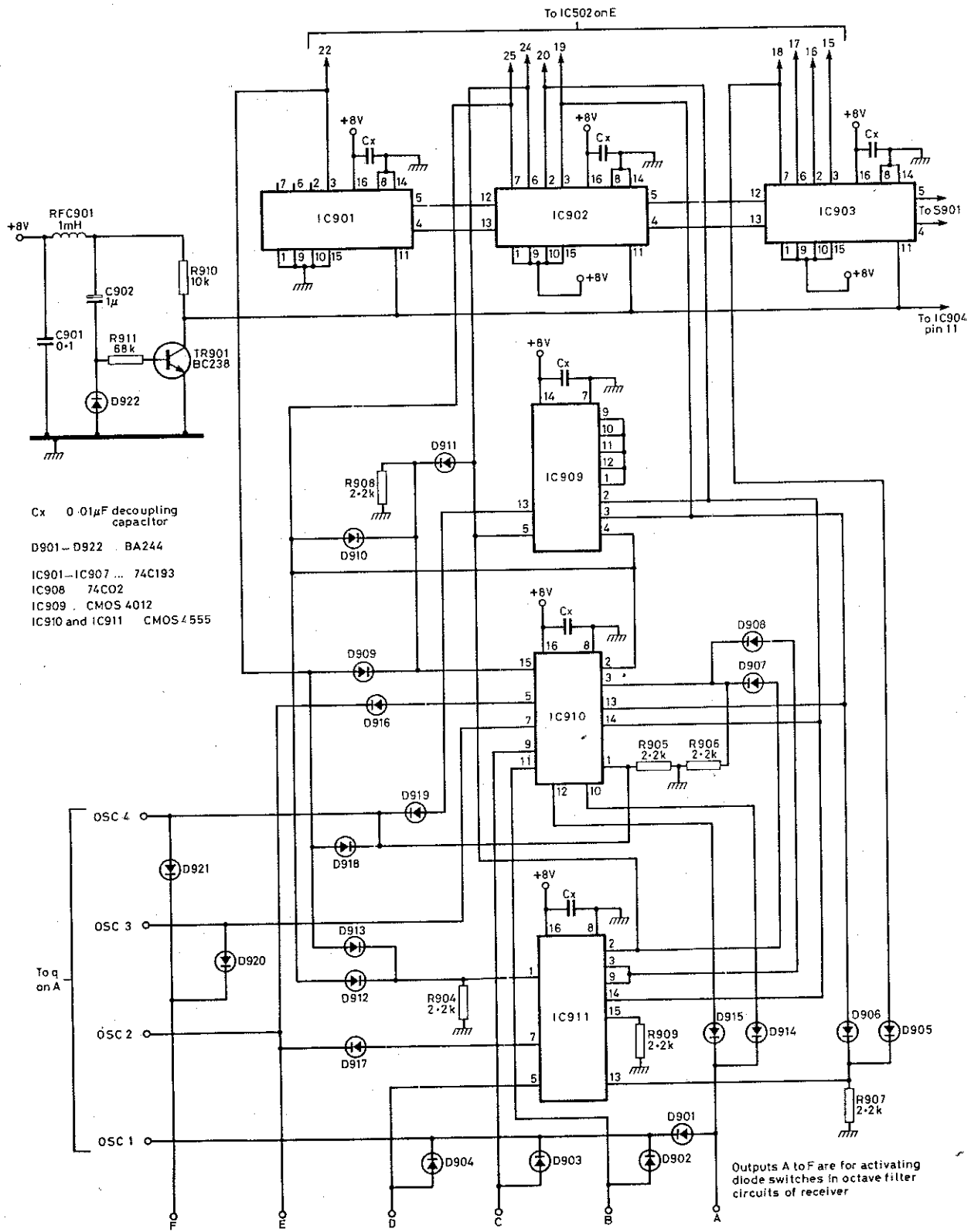

Cx 0.01 μ F decoupling capacitor
 D901-D922 BA244
 IC901-IC907 ... 74C193
 IC908 74CO2
 IC909 CMOS 4012
 IC910 and IC911 CMOS 4555

Outputs A to F are for activating diode switches in octave filter circuits of receiver

Fig 15. Section J. Frequency control, part 1. Part 2 on facing page

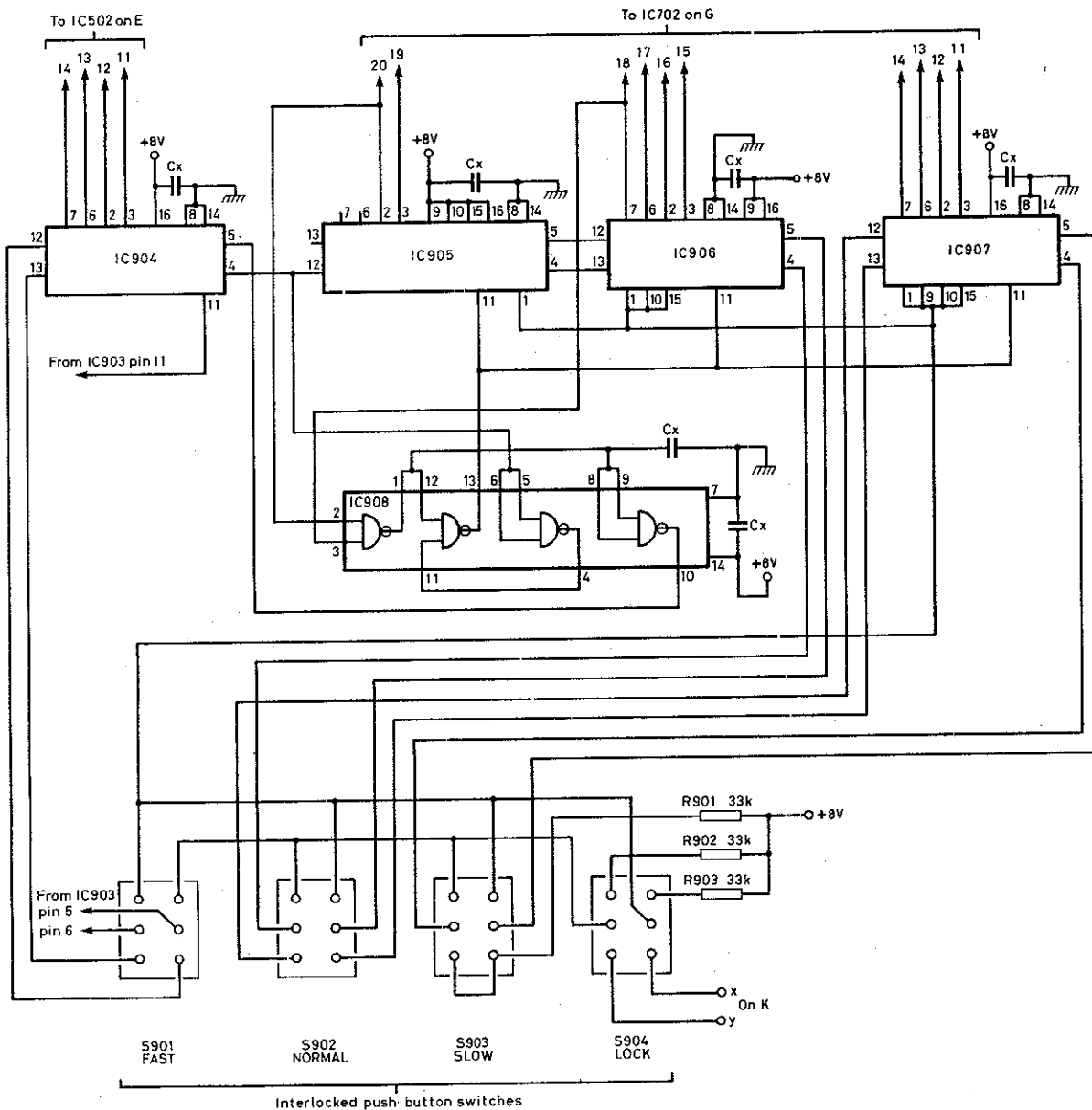

Section J. The up/down counter (Fig 15)

The main function of this section is to control the state of the programming inputs to the MC145151 in the two loops. IC901-7 are all 74C193. These are CMOS up/down binary counters which have their parallel outputs on pins 3, 2, 6 and 7. The count on these is implemented with each falling edge on pin 5 (the up-count pulses) and decremented with each pulse falling edge on pin 4 (the down-count pulses). Pins 12 and 13 are the "carry" and "borrow". Parallel data inputs are at pins 15, 1, 10 and 9.

The main tuning is done by the introduction of up or down pulses to pins 4 or 5 on IC907. The tuning pulses are derived from a "shaft encoder". (I used an Alps device from Cirkit—an IA226 (stock No 48-00226) and a decoder circuit, which routes the up and down pulses separately to the correct pins). These pulses are then routed to the selected part of the counter-chain by the press switches SW1-4. R901, 902 and 903 keep the inputs of unused parts of the counter high when they are switched out. If this is not done, they will oscillate. IC908 (74CO2) limits the count for loop 2 to the range between 15744 and 16383, and passes on a carry or borrow


pulse as appropriate to the rest of the counter chain which controls the count in loop 1. On IC901 and 902, the parallel data inputs are wired to preset the counter to a point near the low-end of the frequency spectrum of the synthesizer. Other builders may wish to set the count at other parts of the band. The BC238 (TR901) generates a negative-going pulse at switch-on which performs the preset operation.

A further part of this section (IC909, 910, 911) deals with the selection of the appropriate vco in loop 1 and also the selection of the correct front-end filter in the receiver. There are seven board pins for connecting the control lines to the front-end filters. From the front of the pcb they are: (a) up to 1MHz; (b) 1 up to 2MHz; (c) 2-4MHz; (d) 4-8MHz; (e) 8-16MHz; (f) combines the outputs of the sixth and seventh pins via diodes for 16-30MHz.

Since there are a large number of wire links and diode links in this section, reference should be made to the detailed overlay: Fig 7

IC909 is a CMOS4012, a double four-input NAND gate. IC910 and 911 are CMOS4555 decoders. Table 1 gives the truth table for these.

Fig 17. Section L. Power supply and regulators (with spare power for receiver etc). These provide spare power at 12V and 6V for the receiver

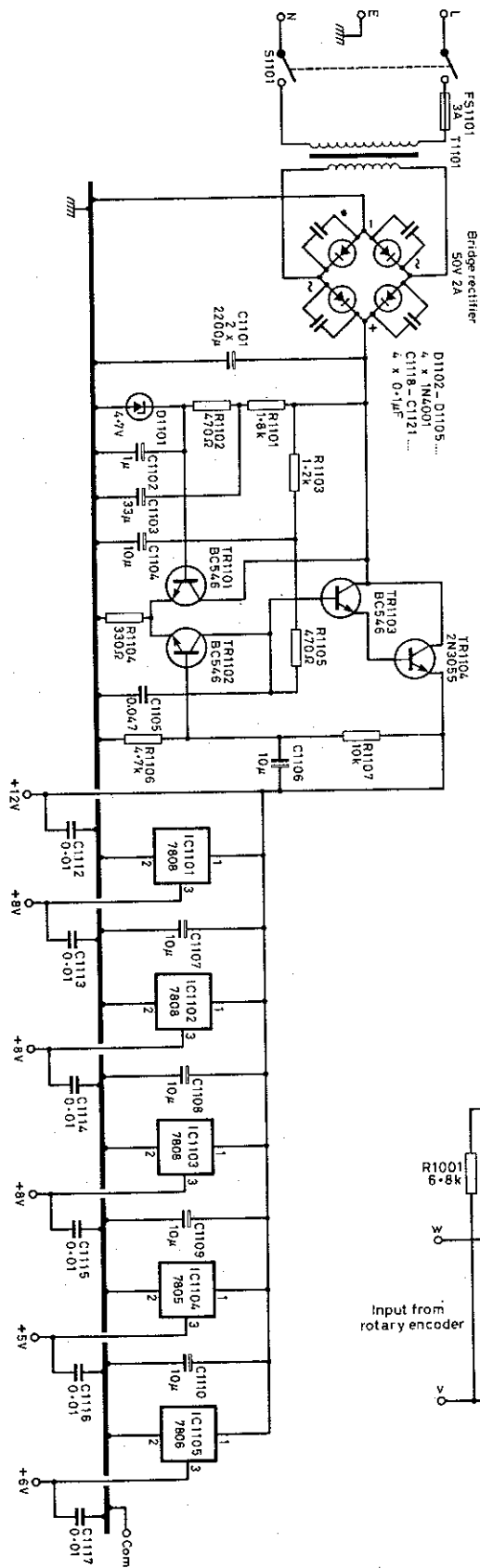

Section K. Pulse decoder (Fig 16)

This section is on a small separate pcb (Fig 20) which can be mounted directly over the rotary encoder. The circuit and layout are self-explanatory. IC1002 and 1003 shape the pulses and the flip-flop IC1001 routes them to the up or the down line x and y. I added the resistor R1007 to protect the 4013, which appeared to be suffering from surges of spiky voltage. Anyway, the last one has lived on, so all seems well.

The rotary encoder gives 50 pulses per revolution of the shaft. It has three terminals, the outer ones go to w and v and the centre one to ground. Choose the direction of rotation for up and down as best suits your ideas on such things. Fig 21 shows the component placing.

Section I. Power supply (Fig 17)

Three regulated 8V supplies, one at 5V regulated and a 12V regulated supply are required for the synthesizer. In addition, a 6V regulated supply is provided for the receiver board; and the 12V line is hefty enough to run a two or three watt audio output stage on the receiver. The mains transformer used is a Drake P1215, a 12VA job. It runs warm when the receiver is working and some builders may prefer a larger unit. If the synthesizer is to have sole use of this power then the P1215 is certainly ideal. Heat sinking for the regulators and for the 2N3055 is provided by the enclosure side. Figs 22 and 23 show the pcb layout and component placing. The board can be soldered directly onto the transformer secondary lugs. The other end is supported on a 0.75in pillar.

Enclosure

I mounted the synthesizer in the top-half of a steel box, 350mm by 230mm. The lower-half houses the rest of the receiver. The synthesizer compartment, which is 60mm deep, also houses the power supply and the rotary encoder and decoder. Fig 5 shows the scheme. The pcbs are on 0.75in pillars, the larger board needs five. Coaxial lead-throughs are required for the connections to the receiver of the injection frequencies.

Inter-board wiring

These are: (a) mains power to transformer via fuse and switch (not shown); (b) 8V lines to section J, E and G; (c) 12V to the pin in the top right-hand corner of the board, just above section C. The latter must run right round the board wherever 12V is required, and various wire links are needed as shown on the overlay. The two leads carrying the up and down pulses from the decoder board are most easily soldered to the front pair of pins on the "lock" switch.

Each board needs an earth-line to ground the board to the enclosure. The 5V line goes to the left-hand side of the board to feed the display, and another 5V line goes to the decoder board. In the first instance it is best to make all these leads long enough to enable the builder to lift the whole of the large pcb out of the enclosure for the exciting job of de-bugging.

Alignment

This needs to be tackled slowly and calmly! Get section J and the tuning pulse system working perfectly first. Check with a logic tester if you have one, but a voltmeter will do. Check output of pulses at the decoder, "up" pulses only on one line, and "down" pulses only on the other. Next check

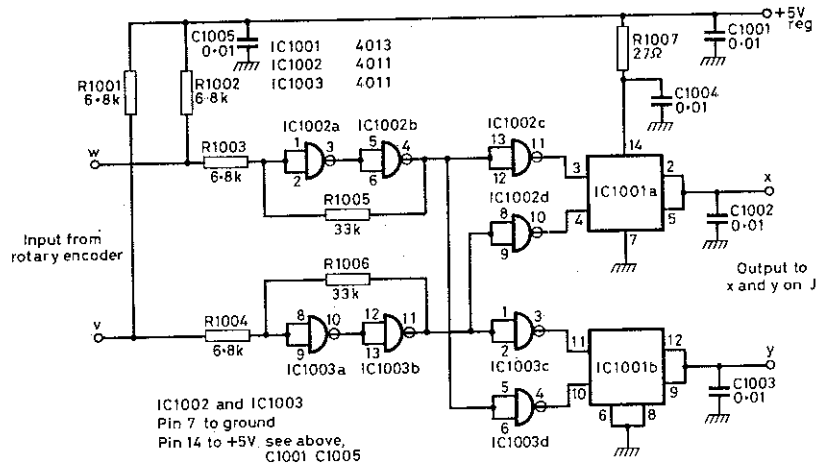


Fig 16. Section K Pulse decoder

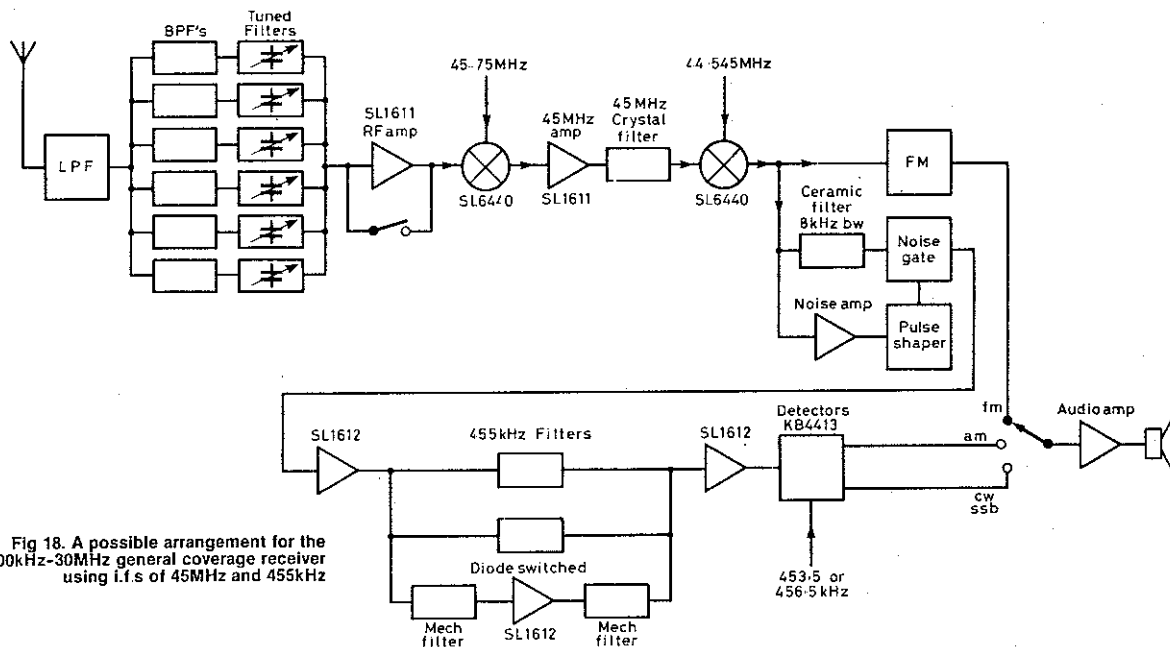


Fig 18. A possible arrangement for the 100kHz-30MHz general coverage receiver using i.f.s of 45MHz and 455kHz

the count on the whole string of 74C193s, checking the output pins 3, 2, 6, 7 in that order, and check the continuity of the lines to the equivalent pins on the MC145151. Remember that a common fault is bridged tracks on the pcb where the copper tracks are very close. The whole board should be examined in a good light with a magnifying glass.

Make sure that the count control is working (IC908). Start with the output pins on IC905, 906, and 907 in J all high (except pins 6 and 7 on IC905 which should never show up high) and tune the count slowly down, by turning the knob in the right direction. When pin 7 on IC906 drops for the second time, the count has reached its limit and IC905, 906, and 907 should set back to high again. Check the up-count from the bottom limit; when all pins of IC905 have reached "high" (except pins 6 and 7 of IC905) the next "up" pulse should re-set to 15744 again. ie to 11110110000000. The first four 1s of this number are there all the time on the MC145151 (pins 22, 23, 24 and 25 have no connection to them) so the highs on IC905, 906 and 907, should be on pin 3 of IC905 and pin 7 of IC906.

The next check is to see that the digital switching, IC909, 910, 911, is working correctly—only one vco should be "on" at a time! Check the inputs and outputs of IC910 and 911. If all is not well, the truth table for the 4555 (Fig 19) will help.

Perhaps the most critical part of the setting-up is the tuning of the filters in sections B and F. The most convenient way to do this is to take out the SL1640 mixer immediately before the filter, and, using a suitable signal generator, inject 200mV or so into the empty mixer socket at pin 5. Watch the output of the filter after amplification by the following amplifier, and swing the signal generator slowly across the part of the spectrum we are concerned with. Take the 42MHz filter in section B first. The main concern here is to let through as much energy at 42.16MHz while keeping out the 44.545MHz component. This is quite a tall order and persons of wealth may prefer to order a special crystal filter! However with care and attention the filter shown will work very well.

If you have trouble getting a narrow enough passband, try reducing the coupling by making C212, 213, and 214 even smaller. Tune the filter so that the upper frequency of the pasband is at 42MHz, and the fall-off of response towards 45MHz as steep as possible.

Table 1. Truth table for the 4555 decoders

Pinout		Truth Table						
		E	A	B	Q1	Q2	Q3	Q4
1 Enable	16 +8V	H	x	x	L	L	L	L
2 A	15 Enable	L	L	L	L	L	L	L
3 B	14 A	L	L	L	L	L	L	L
4 Q1	13 B	L	H	L	L	H	L	L
5 Q2	12 Q1	L	L	H	L	L	H	L
6 Q3	11 Q2	L	H	H	L	L	L	H
7 Q4	10 Q3	L	H	H	L	L	L	H
8 Ground	9 Q4							

Each 4555 has two decoders each with two inputs and four outputs plus an "enable"

The filter in section F is broadband. The coils are hand-wound, and you may want to alter the number of turns and experiment with different values of capacitance. The aim is to get a steep fall in response above 35MHz and a fall also below 2.5MHz, though this latter does not seem to be nearly so critical, and, in fact, needs no adjusting.

The lowpass filter before the display, situated on the left-hand end of the board, may give trouble. If the display is not steady, and all other indications are that the rest of the synthesizer is working properly, try the arrangement shown in the appendix.

Now turn to loop 2, sections G and H, and check for volts and oscillation. See that there is 44.545MHz from section C. Tune the doubler in section H, then, with a voltmeter on pin 6, IC701 section G, watch the voltage while you move the core in L701 (G). When the loop is locked, the voltage will rise and fall with equivalent movements of the core: move the core until the voltage is about 6V. If no lock is achieved, check the circuit and the tuning of L801 and L802 in section H. These can be peaked at 6.4MHz. When the loop is working properly, the voltage at R701 in section G should rise slowly as you tune, and then drop suddenly as the first part of the counter resets.

You should also look at the R701 point to see that the lowpass filter is working properly. To do this, substitute a scope at its most sensitive setting for the voltmeter; there should be no trace of the 400Hz reference frequency.

Next, turn to loop 1 and repeat the same procedure. Set the cores of each of the four vcOs starting from the low-end. In each case set the core so that the tuning voltage is centred at about 6V.

Checking for sideband suppression

Since I do not possess a spectrum analyser or a receiver which will cover 45 to 75MHz, the final adjusting of the synthesizer was done using a receiver at 10MHz, and a double-balanced mixer with an injection from a Marconi signal-generator running at a frequency 10MHz higher than the frequency of the synthesizer. See Fig 19.

Using the lowpass filter in section E as shown, the 6.4kHz sidebands should be over 40dB below the output at the required frequency.

The bandpass filter in section B can be adjusted for the best "note"

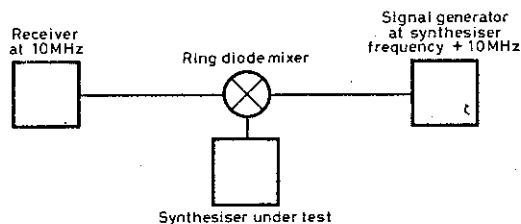


Fig 19. Using a receiver to check synthesizer output

Components list

<p>SECTION A</p> <p>R101 33k R102, 104 100k R106 10k R103 10k R105 100k R107 6.8k R108 22k R109 470Ω R110 2.2k R111, 116 1k R112 22k R113, 114 100Ω R115 10kΩ R117 220Ω C101, 102, 115 3 9pF C103 2 2pF C104, 106, 113 0.01μF C105, 114 0.047μF C107 6.8pF C109 39pF C110 10pF C111 100pF C112 See text C116, 117 0.01μF C118 10μF electrolytic L101 See text D101, 102 BB109 D103 BA244 TR101 BC238 TR102 BC308 TR103, 104, 105 BF241 RFC101, 103, 104 470μH RFC102 10μH RFC105 1.2μH <p style="text-align: center;">All RFCs are Toko 7BS series</p> </p>	<p>R403, 406, 410, 411, 416 220Ω R404 380Ω R412 68k R414 680Ω R415 150Ω C401, 418 2.7pF C402, 403, 404, 405, 406, 408, 409, 410, 412, 420, 423, 430, 431, 433, 434, 436 0.01μF C407 10μF C411, 421, 427, 428, 429, 432, 435, 437, 438, 439 0.047μF C413, 414 3 9pF C415 4 7pF C416, 426 2 2pF C417, 419, 422 0.001μF C424 10μF electrolytic C425 12pF RFC401, 402, 403, 404, 406, 408 470μH RFC405 1mH RFC407 10μH L401, 402, 403, 404, 405 3 3μH Toko 7BS TR401, 402, 403, 404, 405 BF241 IC401 SL1640 IC402 HD10551 LCD FC177 Cirkkit 39-17700</p>	<p>SECTION B</p> <p>R201 380Ω R202 100k R203 680Ω R204 100Ω R205 220Ω C201 6.8pF C202 2.2pF C203, 204, 205, 207, 209 0.01μF C206, 210 0.047μF C208 10μF electrolytic C211 10pF C212, 213, 214 See text C215 22pF C216 3.9pF C217, 218 4 7pF L201, 202, 203, 204 Toko K3344 TR201 BF241 IC201 SL1640 RFC201, 202 470μH, Toko 7BS</p>	<p>SECTION C</p> <p>R301, 305 22k R302, 304 5.6k R303 1k R306 4.7k R307 220Ω R308 10k C301, 304, 307, 308 0.01μF C302, 306 22pF C303, 310 10pF C305, 309 0.047μF X301 Crystal 44.545MHz with 20pF in series L301, 302 K3335 (1.2μH) RFC301, 302 100μH, Toko 7BS TR301, 302 BF241</p>	<p>SECTION D</p> <p>R401, 407, 408 100k R402, 405, 409, 413 100Ω</p>	<p>SECTION E</p> <p>R501, 519 100Ω R502, 506, 514 1k R503 560Ω R504, 511, 512, 518 3.3k R505, 507 33k R513 2.2k R515, 516, 517 220Ω R510 100Ω C501, 510, 511, 516, 517, 518, 519, 520 0.01μF C502, 512, 521, 522, 523 0.047μF C503, 508, 509 0.1μF C504, 505 1μF C506, 507, 513, 514 0.001μF C515 6.8pF X501 Crystal 3.2768MHz. HC18U Cirkkit 45-03000</p>	<p>SECTION F</p> <p>R601, 607 220Ω R602 22k R603 10k R604, 608, 612 100Ω R609 2.2k R610 1k R611 470Ω R613 5.6k C601, 603, 604, 605, 607, 609, 610, 612, 614 0.01μF C602, 606, 613 0.047μF C608 10μF electrolytic C611, 616, 617, 618, 621 10pF C615, 622 6.8pF C619 100pF C620 4.7pF C623 2.2pF</p>	<p>SECTION G</p> <p>R701, 716 100k R702, 703, 712, 716, 720 1k R704, 705, 706, 707 5.6k R708 680Ω R709 10Ω R710, 711 220Ω R713, 721, 723 100Ω R714, 712, 722 2.2k R717 22k R718, 726 10k R719, 724 560Ω R725 3.8k C701, 702, 703, 710, 712, 713, 715, 716, 717, 721, 725, 726, 733 0.01μF C704 1μF tantalum C705, 706 4.7μF tantalum C707, 711, 714, 727 0.047μF C708, 709 0.1μF C718, 723, 730 6.8pF C719, 720 33pF C722 10μF electrolytic C724 728, 729 0.001μF electrolytic C731 0.003μF C732 2.2pF L701 0.17μH Toko MC120 100075</p>	<p>SECTION H</p> <p>R801, 808 22k R802, 810 10k R803, 805, 807, 811 100Ω R804, 806, 809 220Ω C801, 815 100pF C802, 804, 805, 806, 807, 809, 810, 813 0.01μF C808 10μF electrolytic C811, 821, 822 0.047μF C812 0.001μF C814 10pF C816 6.8pF C817, 820 33pF C818 47pF C819 27pF C823 2.8-12pF min ceramic RFC801, 802, 803 470μH RFC804 22μH TR801, 802 BF241 IC801 SL1640</p>	<p>SECTION I</p> <p>L801, L802 { 15 turns of 32swg wire on 10k former with pot-core } L803 { 12 turns 28swg enam copper on 0.25W 1MΩ resistor }</p>	<p>SECTION J</p> <p>R901, 902, 903 33k R904, 905, 906 907 908, 909 2.2k R910 10k R911 68k C901 0.1μF C902 1μF electrolytic C903-12 0.01μF for decoupling the ics and for pin 12 on IC8</p>	<p>SECTION K</p> <p>R1001, 1002, 1003, 1004 6.8k R1005, 1006 33k R1007 27Ω C1001, 1002, 1003 1004, 1005 0.01μF IC1001 CMOS4013 IC1002 1003 CMOS4011</p>	<p>SECTION L</p> <p>R1101 1.8k R1102 1105 470Ω R1103 1.2k R1104 330Ω R1106 4.7k R1107 10k C1101 2 × 2 200μF electrolytic C1102 1μF C1103 33μF C1104, 1106, 1107, 1108 10μF electrolytic C1105 0.047μF C1112, 1113, 1114, 1115, 1116, 1117 0.01μF C1108, 1119 0.1μF T1101 Transformer Drake 12VA P1215 D1101 Zener diode, 4.7V Cirkkit 12-00478 D1102, 1103, 1104 1105 4 rectifier diodes, 1N4001 or similar TR1101, 1102 1103 BC546 TR1104 2N3055 S1101 Mains switch FS1101 3A fuse IC1101, 1102, 1103 Regulators 7808 IC1104 Regulator 7805 IC1105 Regulator 7806</p>	<p>Holders for all ics Board pins for connections Incremental encoder Alps LA226 Cirkkit 48-00226 Connecting wire and miniature coaxial All RFCs are standard value Toko 7BS or 7BA series</p>
--	--	--	--	--	--	---	--	--	---	---	---	---	---

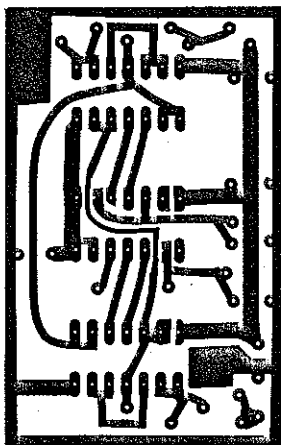


Fig 20. Pulse decoder pcb layout

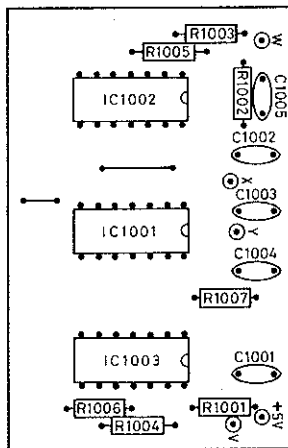


Fig 21. Pulse decoder component layout

Putting the synthesizer to use

Each builder will have his own ideas about the ideal receiver circuit. I used chiefly the Plessey SL series ICs. Fig 18 shows the block diagram of the complete receiver. The 45MHz filter is a cheap two-pole crystal device, 45M15A, supplied by Cirkit. The two balanced mixers are SL6440. The synthesizer could very well drive a compact QRP all-band transceiver.

EDITOR'S NOTE
Because of its large dimensions, it has not been possible to reproduce the main pcb layout, the component layout for which (Fig 7) was published in Part 1. Photocopies of the master negative can be obtained on request from the editor at RSGB HQ.

Errata. In Part 1, page 562, under the heading "The circuit described by sections", Section A, lines 5, 7 and 10 for C122 read C112; line 8 for C102 read C112.

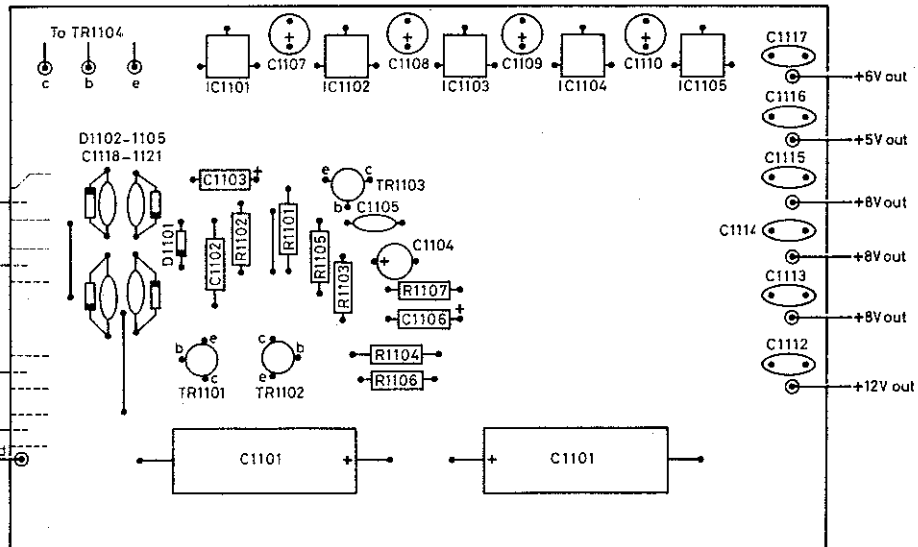


Fig 22. Power supply component layout

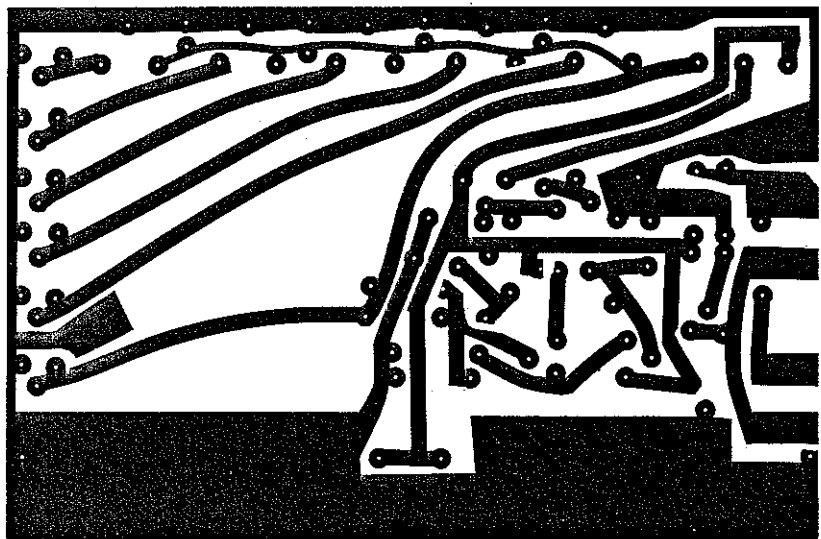


Fig 23. Power supply pcb layout

Components

All the components are readily available. Resistors are all carbon film 0.25W per cent. Capacitors: 0.1 are Mylar; 0.001, 0.01, 0.047 are low-voltage disc ceramic, smaller values are mostly ceramic chip. Electrolytics are 16V working radial leads, except those indicated on the components list. Builders interested in purchasing a set of pcbs for the project, should contact me.

APPENDIX

