

# Micropower crystal oven

Commercial crystal ovens are notoriously power hungry, being designed to work way above room temperature. Operating at a user-defined temperature just above the maximum anticipated ambient, Rae Perälä's oven can be run from a battery.

The circuit presented here can be used as a battery operated thermostat oven. It consists of two 7555 timer circuits, but it could incorporate a dual timer circuit 7556. Both the 7555 and 7556 are c-mos types, which guarantees a very low power consumption.

Figure 1 shows the complete circuit. Timer  $IC_1$  acts as an oscillator, and  $IC_2$  as a heating control circuit. Figure 2 shows the IC output voltages. Output voltage of  $IC_1$  lies mostly at the positive battery voltage  $V_B$ , giving only short 23µs zero voltage pulses, represented by  $T_2$ , in the intervals of 3.5ms, shown as  $T_1$ .

Output pulses of  $IC_1$  trigger  $IC_2$ , which is connected as a monostable multivibrator. It produces a positive-going 2.5ms pulse, represented by  $T_3$ , every time its trigger input in pin 2 goes below the one third of the battery voltage.

Timer  $IC_2$  output controls an n-type enhancement mos transistor, used for driving current pulses to the heating resistor.

The triggering voltage of  $IC_2$  is formed from the output pulses of  $IC_1$  by a voltage divider. One

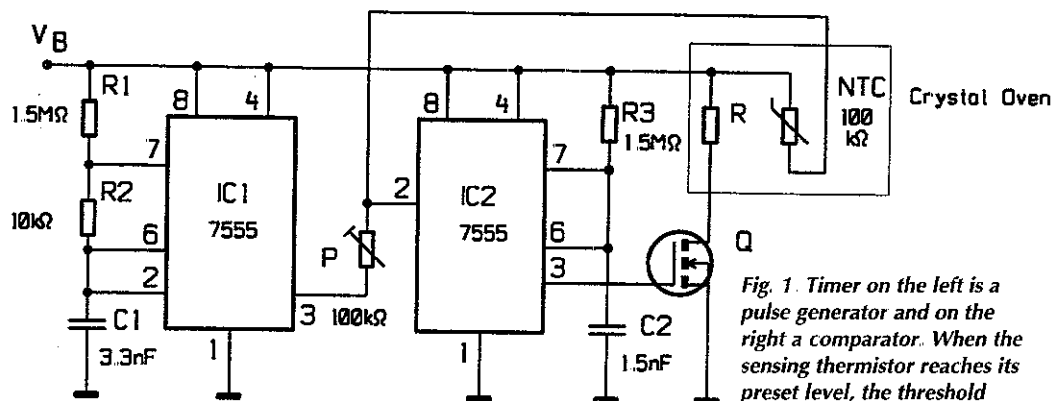


Fig. 1. Timer on the left is a pulse generator and on the right a comparator. When the sensing thermistor reaches its preset level, the threshold becomes too high to let the comparator trigger and heater resistor  $R$  receives no heating pulses.

part of the potential divider is a potentiometer used to adjust the temperature. The other is a 100kΩ negative temperature coefficient thermistor mounted inside the oven.

The advantage of using a voltage divider is that changes in the battery voltage have no influence on the circuit operation. The circuit is adjusted so, that the resistance value of  $P$  is exactly one half of the resistance value of the thermistor at the temperature required in the oven.

## How it works

While the oven temperature is

below the preset value, the trigger input voltage of  $IC_2$  at pin 2 goes below the triggering limit  $V_B/3$  during every zero pulse from  $IC_1$ . This means that  $IC_2$  is triggered, producing heating current pulses to the oven.

When the oven temperature reaches the value attained, the thermistor's resistance value decreases. This prevents the trigger pulses for  $IC_2$  from going below one third of the battery voltage. Now, the heater no longer turns on.

From Fig. 2, you can see that the positive output pulses from  $IC_2$  begin exactly at the rising edge of triggering pulses from  $IC_1$ . In this illustration, the first two triggering pulses trigger  $IC_2$ , as would be the case if the oven temperature were too low. During the third pulse the oven temperature level is assumed to have increased so. Triggering does not take place and the heater remains off.

The oven temperature should be adjusted a little higher than the maximum expected ambient temperature, via potentiometer  $P$ . An unnecessary high oven temperature increases the heating power demand.

The circuit is a micro power one. While the heater is off battery current of 170µA will be sufficient for the whole circuit. A small crystal oven can be heated by a current of few milliamps. The heating resistor and the type of the mos transistor can be selected according to the amount of heat needed. Heater current can be minimised by making sure that the oven is well insulated.

The circuit operates with battery voltages between 8 V to 15 V. Theoretically, the circuit is not sensitive to battery voltage because operation depends on the resistance ratio of the thermistor and potentiometer  $P$ . In practice, I have found that the oven temperature alters a little when the battery voltage changes. This problem can be avoided by regulating the voltage connected to the ICs using a micropower regulator. Voltage supplying the heating resistor needs no regulation, so adding such a regulator does not have a significant affect on consumption.

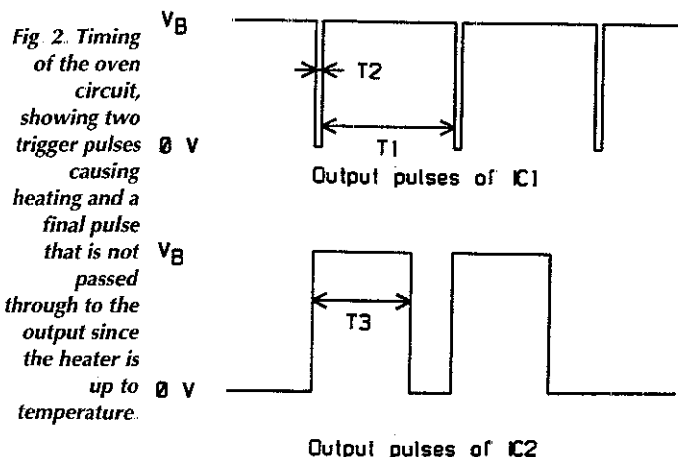


Fig. 2. Timing of the oven circuit, showing two trigger pulses causing heating and a final pulse that is not passed through to the output since the heater is up to temperature.