

A perfect variable oscillator?

Think of a sinewave, distort it to stabilise the amplitude, take away the harmonics you first thought of, and the answer's a pure sinewave. Not quite that straightforward, but that is roughly what Ian Hickman's latest invention amounts to.

This design more or less materialised by itself – perhaps harmonic serendipity describes it. Low distortion audio frequency oscillators have always held a fascination for me. Several designs have appeared in these pages over the years. Some, like the one described in reference 1, offer a modest performance – around 0.07% THD – while the configuration described in reference 2 improves on this by a factor of 20 or more.

Many low-distortion audio oscillator designs, like the one in reference 3, use a thermistor such as the famous R53, or the R54, for amplitude stabilisation. Though effective, this has certain disadvantages, one of which is the high cost of the device.

The main disadvantage though is a rise in third-harmonic distortion at frequencies below 100Hz, becoming quite marked at 20Hz. This is due to the period of the waveform beginning to approach the thermal time-constant of the thermistor, so that the element tends to cool between each half cycle of the waveform, as it passes through zero voltage.

With this in mind, some years ago I designed a 20Hz-20kHz audio oscillator⁴ using diodes to stabilise the amplitude in place of the expensive R53. The advantage here is that the limiting action is totally independent of frequency.

At 0.04% total harmonic distortion plus noise over the whole audio frequency range, its performance was good, bearing in mind the low component cost. But in another application⁵ even the diodes were dispensed with. Here, the oscillator consisted of a frequency-selective amplifier whose gain was allowed to reach infinity. The relationship between oscillators and selective amplifiers was discussed in reference 6 which, though predating op-amps, nevertheless contains some interesting ideas.

Another look at the problem

Being now equipped with an HP3580A audio frequency spectrum analyser, I decided it was time to take another look at just how good a low a distortion oscillator could be designed, without recourse to a thermistor for amplitude stabilisation.

As an exercise in making a silk purse out of a sow's ear, that standard low-cost standby of FET input op-amps, the TL084 was selected. I started with the circuit of Fig. 1, which, apart from the frequency, is the same basic circuit as in reference 5. This circuit produces an output at approximately 1kHz, the peak to peak amplitude just reaching to the supply rails.

Output spectrum is shown in the upper trace of Fig. 2. This shows the measured at the output of the second integrator, deliberately plotted with rather a wide IF bandwidth. The

largest harmonic is the third, being 63dB down on the fundamental or 0.07%. Other harmonics are about 70dB or more down.

Amplitude stabilisation took the form of reducing loop gain at the fundamental component, due to the output hitting the supply rails. In theory, the loop phase shift is exactly 180°, corresponding to a circuit Q of infinity; in practice, the phase shift will be a smidgeon more, due to the inevitable residual phase lag in the integrators, even though this is very small at 1kHz.

The output waveforms of all three op-amps in the circuit were substantially similar. All were limiting gently, to slightly different degrees. The obvious next step, therefore, was to confine the limiting to the first op-amp, so that the harmonic distortion products caused by the limiting were attenuated by the the 6dB/octave roll-off of each of the two following integrators.

This was achieved by raising the gain of the first op-amp, so that the amplitude at its output – the high-pass node of the

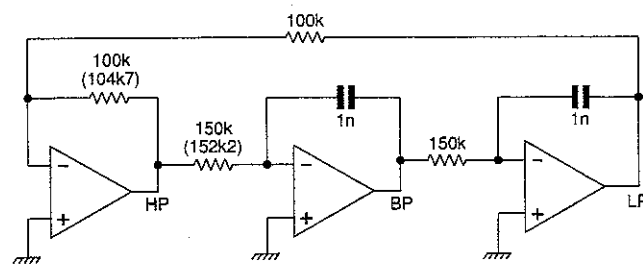


Fig. 1. Simple low distortion sinewave oscillator

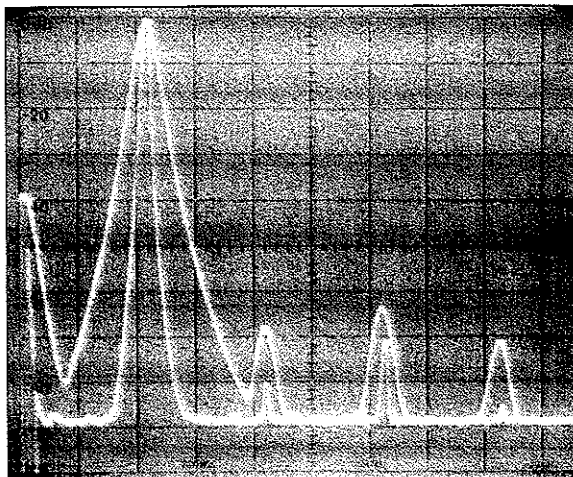


Fig. 2. Upper trace, output of the circuit of Fig. 1. Span 0-5kHz, 100Hz resolution (IF) bandwidth, video (post detection) filter off. Lower trace, as above, but with component values in brackets, resolution bandwidth 30Hz.

Fig. 3. Modified circuit designed to produce little or no third harmonic component at the lowpass output.


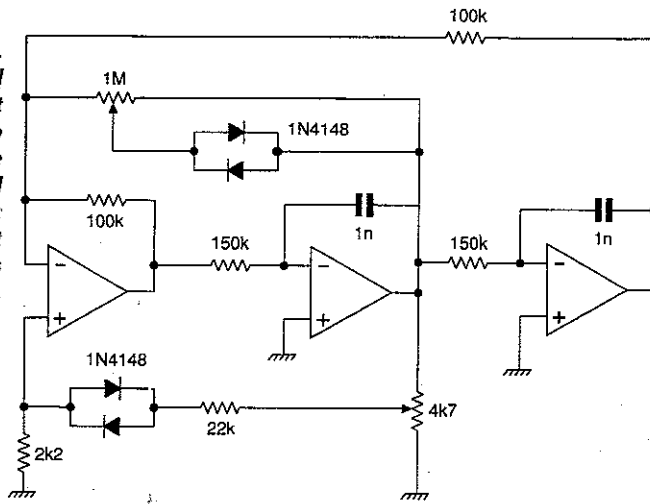


Fig. 4. Output of the circuit of Fig. 3. Span 0-10kHz, 100Hz resolution (IF) bandwidth, video filter off.

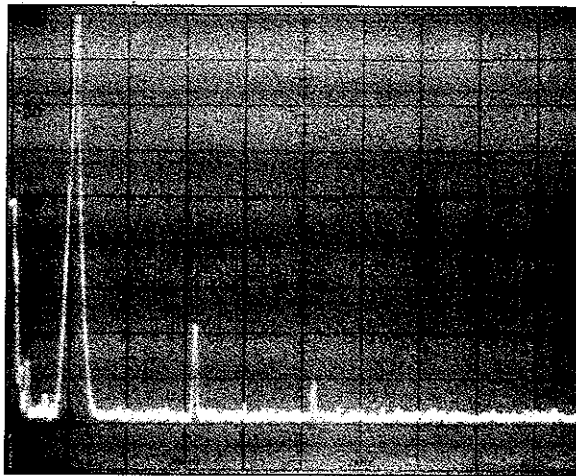

filter – was larger than at the output of the second integrator – the low-pass output. Its feedback resistor was therefore raised by 4.7kΩ, the integrators between them now providing a gain of 4.7% less than unity.

To do this, the frequency automatically adjusts itself up a little. If the integrator components remained the same, the first integrator would still run at a slightly higher amplitude than the second, so its input resistor was raised by 2.2kΩ, giving roughly equal amplitude non-limiting outputs at the bandpass and lowpass output nodes.

The spectrum was now as shown in Fig. 2, lower trace. For clarity, this has been recorded at a narrower IF bandwidth, and the slight increase in frequency is clearly visible, more so at the higher harmonics.

The third harmonic is now 70dB down on the fundamental, and others 80dB or more down. Incidentally, the reduction in the second harmonic was not all due to the component changes; the opportunity was taken to tweak one of the supply rails to more nearly equalize the clipping of the positive and negative peaks.

For such a simple circuit, a thd plus noise figure of 0.03% is not at all bad, and it is a very useful and economical arrangement for a fixed frequency oscillator. For a wide-range audio frequency oscillator it is less suitable, since the excess phase shift in the integrators will increase with frequency, leading to a much worse distortion figure at 10kHz and above. So my thoughts turned to the type of oscillator described in reference 4.

Diodes for stabilisation

This circuit incorporated negative feedback of such a value as to set the filter to a Q of 11. Positive feedback was applied from the bandpass output, BP, of a value exceeding the neg-

ative feedback, effectively providing the filter with an input derived from itself.

However, as the amplitude of the oscillation builds up, diodes start to limit the positive feedback, so that the fundamental component of it ceases to increase, or does so only marginally.

As the negative feedback continues to increase proportionally with the amplitude of the oscillation, an equilibrium point is reached, where the net loop gain at the fundamental just equals infinity. The circuit was arranged so that this occurred at a level well below the maximum possible swing set by the supply rails, with the result that the second harmonic distortion was negligible.

An advantage of an oscillator such as this, based upon the state variable filter, is that the circuit can be used both as an oscillator, and simultaneously as a second-order elliptic low-pass filter. Any third harmonic, due to the limiting action of the diodes, present at the high-pass output will be attenuated by a factor of three in each of the integrators.

Furthermore, as each integrator provides a 90° phase shift regardless of frequency, the third harmonic present at the high-pass output is in antiphase to that present at the lowpass output. So by using an additional summing amplifier to combine one ninth of the highpass output with the full lowpass output, the third harmonic sits in a notch.

This results in a signal entirely free of any third harmonic, an arrangement used in reference 4. Meanwhile, the fundamental output is of course also reduced, but only by a ninth.

Handy though this arrangement is, there is a down side to it. While the third harmonic is outphased completely, the fifth harmonic is actually made 5dB worse. But there is still a net reduction in thd, since, due to the fairly soft limiting action of the diodes, the amplitudes of the harmonics at the high-pass output drop off much more rapidly than in an ideal squarewave.

Outphasing the fifth harmonic

It occurred to me that if I could arrange that the amplitude limiting method inherently did not produce third harmonic, then the fifth harmonic could be outphased instead – simply by adding a twentyfifth of the high-pass output to the low-pass output.

Reduction of selected harmonics by waveform shaping is a technique long familiar in power engineering. There, it can be used to minimise the filtering required at the output of an inverter, as in for example reference 7. So I experimented with a circuit designed to avoid producing third harmonic in the stabilisation department, permitting outphasing of the fifth.

This is shown in Fig. 3. Oscillation commences since there is positive feedback from the bandpass output via 1MΩ to the inverting input of the first op-amp. Initially, there is no negative feedback via the 22kΩ resistor to the noninverting input, as it is blocked by the diodes.

As the amplitude increases, their forward voltage is overcome, and thereafter the stronger negative feedback increases more rapidly than the positive feedback. This leads to equilibrium at a level which can be adjusted by means of the 4.7kΩ potentiometer. The 1MΩ potentiometer can then be adjusted to feed narrow additional positive feedback pulses at the tips of the waveform.

Following careful setting up, the output spectrum was as shown in Fig. 4. The third harmonic at the low-pass output is at -69dB, about as low as the diode-free circuit of Fig. 1. It is also lower – without the benefit of outphasing – than achieved by the circuit of reference 4 with diodes.

But setting up was fairly critical, and performance with tuning and with change of ambient temperature would clearly have been unsatisfactory. Nevertheless, the low level of fifth harmonic was encouraging, so the circuit was rear-

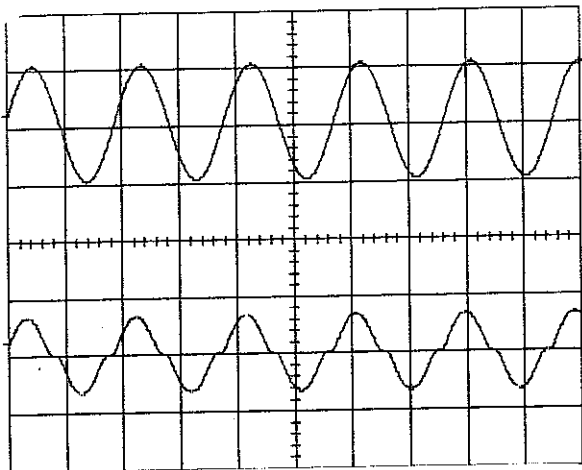


Fig. 11. Upper trace, the waveform at point B in Fig. 9. Lower trace, the waveform at point C in Fig. 9. Both traces, 2V/division vertical, 500µs/division horizontal.

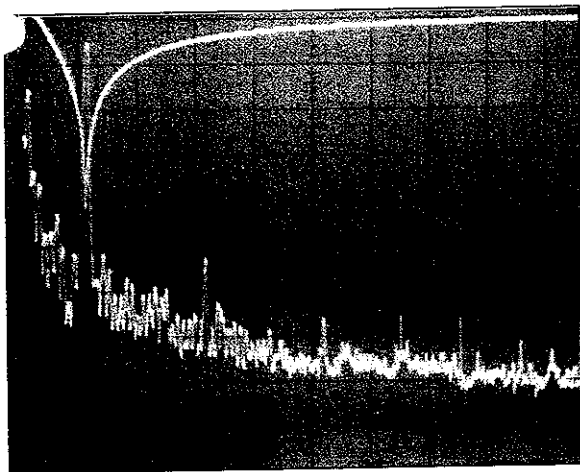


Fig. 12. Upper trace, the response of a 1kHz (nominal) notch filter. Lower trace, the LP output of the circuit of Fig. 9 with the fundamental in the notch, and the sensitivity of the spectrum analyser increased by 40dB. Span 0-10kHz, 30Hz bandwidth, video filter at medium, 20s/div sweep speed.

trated, is listed as 0.003% or -90dBc.

Together with IC₅, IC₆ provides a choice of a 600Ω output, or a variable voltage source for driving high impedance loads. Amplitude monitoring is provided by IC₇, enabling any output level variations with temperature to be trimmed out, by adjustment of R_A.

The value of R_m is determined by the sensitivity of the meter used, while another resistor R_p, of suitable value, may be included if desired, for meter protection in the event of overload.

Finally, IC₈ provides a means of adjusting R_B so that the output of difference amplifier IC₄ contains zero contribution at the fundamental. As R_B is adjusted, the sudden complete disappearance of the fundamental is very obvious, no need for the aid of a spectrum analyser

A switch to turn the stage off once the adjustment is complete, is clearly a good idea. Resistors R_A and R_B should preferably be multi-turn types, and for convenience can be made adjustable via the oscillator's front panel.

Setting up

Setting up the circuit for optimum performance is very straightforward, and no special equipment is needed. The sequence is as follows.

Disconnect the 560kΩ resistor from the point DP and connect it to ground instead. This isolates the effect of R_B, preventing it interacting with the next step, while ensuring the effective positive feedback ratio is unchanged.

Set R_A to give the desired output level. Assuming 15V supply rails, 10V peak to peak is a suitable value.

Using the audio monitor of Fig. 13, adjust R_B for zero fundamental component in the output of IC₄; this is conveniently carried out at 1kHz.

Disconnect the 560kΩ resistor from ground and reconnect it to IC₄'s output. Check that this does not alter the level at the LP output

References

- 1 Krause VR. F.E.I. audio oscillator. *Wireless World* September 1971 p. 427.
- 2 Rosens, R. Phase-shifting oscillator. *Wireless World* February 1982. pp. 38-41.
- 3 Ridler, PF. Distortion in Feedback Oscillators. *Electronic Engineering*, Vol. 37, No 451, September 1965. p. 604
- 4 Hickman, I. Low distortion audio frequency oscillators. *Wireless World*, April 1982 pp. 345-346; reproduced in *Analog Circuits Cookbook* by the same author, ISBN 07506 20021. Butterworth-Heinemann 1995
- 5 Hickman, I. LCR measuring transformer. *Electronics World*, November 1994, pp. 931-934; reproduced in *Hickman's Analog & RF Circuits*. ISBN 07506 37420. Butterworth-Heinemann 1998.
- 6 Butler, F. Transistor R-C Oscillators and Selective Amplifiers. *Wireless World*, December 1962. pp. 583-589.
- 7 Turnbull, FG. Selected Harmonic Reduction in Static DC-AC Inverters, *IEEE Trans on Comm. and Electronics*, July 1964. p. 374.

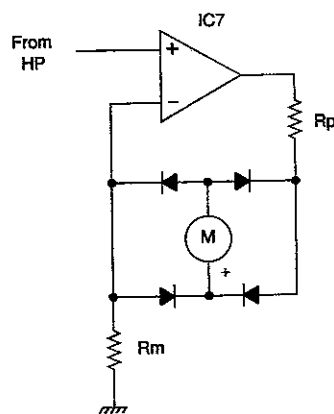


Fig. 13. Some useful add-ons for the circuit of Fig. 9 (see text).

