

Underground radio or, "You thought you heard what?"

A medical friend wanted to listen to her mains-powered radio in her office between patient visits while coping with the paperwork, but didn't want it to be known – patients can be impatient. This circuit arrangement switches the radio off when the office door is opened, leaving an



impression of industry and innocence

Door-mounted switch D has its contacts open when the door is closed, as in the type used for cupboard lights. As the door opens, the switch shorts the latching relay coil opening the contacts and turning the radio off. When the

coast is clear, the relay may be relatched and the Archers brought back by momentarily closing switch B, which can be anywhere convenient.


The 240V ac, 15-100W lamp acts as a current limiter to prevent damage when the coil is shorted, flashing as the door opens. A 6-48V dc relay may be used with a series 400V dc (i.e. 250V ac) 1µF capacitor with a 1MΩ bleed resistor.

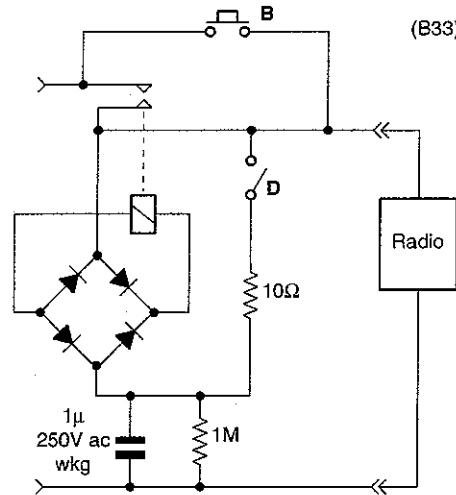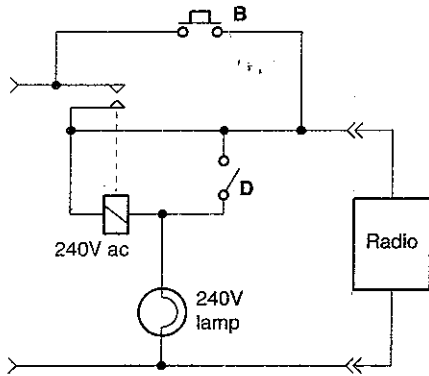Switch B will need the 10Ω series resistor to limit inrush current. Take care with the switch wiring; both are at mains potential. **Hugh T Wynne**
Glasgow



Clandestine radio switch switches off the radio as soon as the door opens, leaving a lot of very baffled people.

No-trim If balanced mixer

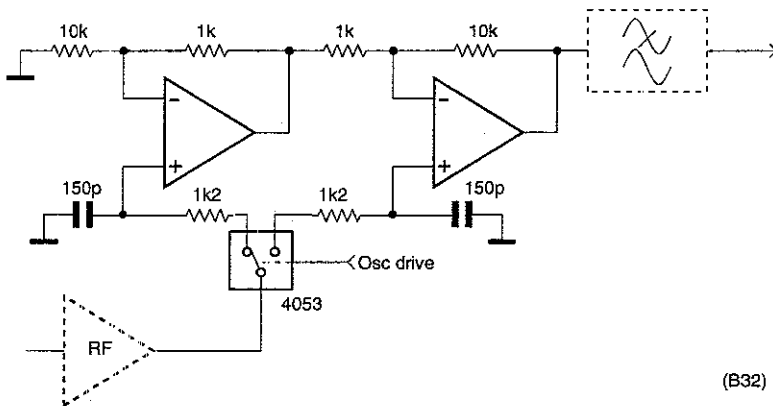

For a low-frequency ssb cave radio, I wanted to use a pair of balanced mixers that needed no balance control without resorting to multiplex ics or analogue gates, which need trimming to reduce the effect of unbalanced inputs. This circuit is probably familiar to instrument engineers, but I have not seen it used in a radio design.


The right-hand op-amp's non-inverting input gain is 11 and its inverting input sees a gain of 10; the other amplifier has a gain of 11, so that the overall gain is 11. With 1% resistors, balance is excellent.

Series 1.2kΩ resistors and capacitors perform the sample-and-hold at our 87kHz frequency. Oscillator drive to this circuit and its partner is at 12V digital level in phase-quadrature.

Output is very pure and the circuit is difficult to overload.

John R Hey
MIE Medical Research Ltd
Leeds

Alternative audio agc

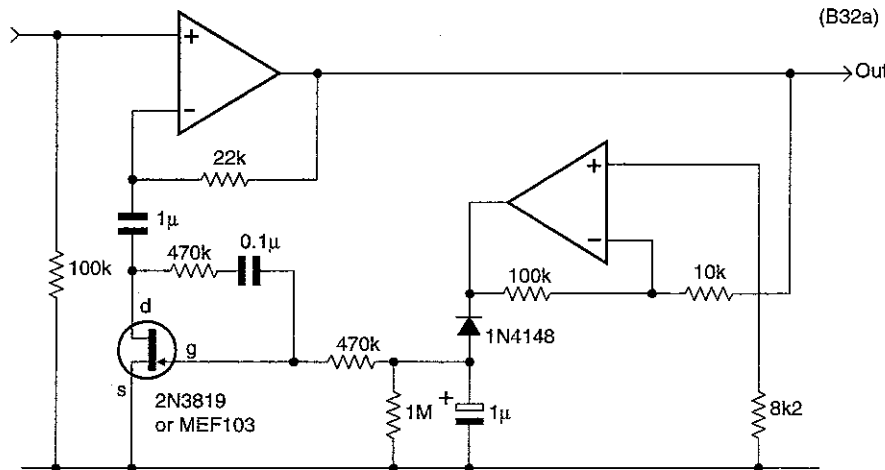


Plessey's 6270 gain-controlled microphone preamp having been discontinued, I had to find a replacement for an audio agc system and have found other ics to be somewhat expensive. This circuit works well and is cheap.

Gain in the non-inverting op-amp is set by the 22kΩ feedback resistor and the return via the 1µF capacitor and fet, whose local feedback prevents waveform distortion. Overall feedback comes from the other op-amp with a gain of 10, its output being rectified and smoothed.

I have tried various fets, but have settled on the 3819 and MEF103, which work well: signal levels in the 4mV-4V range all output at about 200mV.

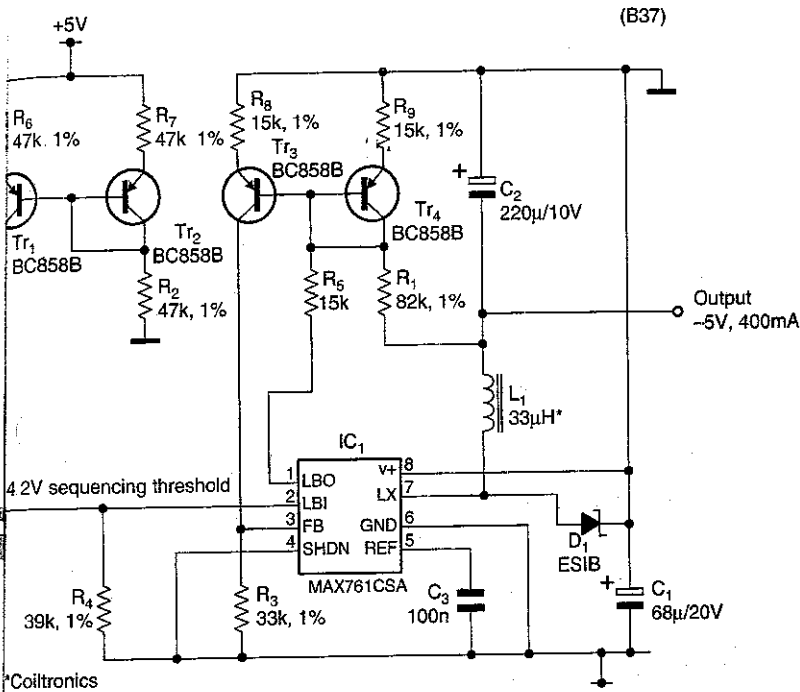John R Hey
MIE Medical Research Ltd
Leeds



Maxim's MAX761CSA used as a negative buck regulator to provide -5V from a -12V supply, the -5V appearing in sequence with a separate +5V supply during switch-on and switch-off.

Sequenced step-down converter

This -12V to -5V converter only provides the -5V output when a separately regulated +5V has made its appearance, shutting down the -5V output if the +5V is not present. Λ -to-d and d-to-a converters often need this sequencing to avoid latch-up.

Regulator IC₁, a MAX761CSA, is an efficient, switching boost device used here as a negative buck regulator. The boost regulator arrangement is correct for the switching control. But the feedback, being referred to the positive rail and compared with a reference from the negative rail, needs a voltage level shift, which is provided by the current mirror Tr_{3,4}; emitter resistors R_{8,9} reduce mismatch error.

An internal comparator and 1.5V reference in the 761, which are intended for low-battery detection on the low-battery input and output pins, monitor the +5V rail. Current from the Tr_{1,2} current mirror develops a voltage across R₄, proportional to the +5V rail, that is applied to LBI.

If this drops below a nominal

4.2V, LBO pulls R₅ to the negative rail, causing an increase in current through the diode-connected Tr₄; this is mirrored in Tr₃ and develops a voltage across R₃, applied to the feedback pin of the regulator. The action indicates that no further output is needed and the regulator shuts down, a minimum of 10k Ω load preventing D₁ leakage charging up C₂.

This buck-regulator arrangement delivers around 400mA at -5V, instead of the 150mA when used as intended as a boost converter, driven by +5V. Efficiency is 90% at 400mA, down to 85% at 100mA; ripple under 25mV at any load and accuracy dependent on the internal reference and tolerance of R_{1,3,8,9}.

Different V_{BE} in Tr_{3,4} introduces more errors, but these can be greatly reduced and the need for R₆₋₉ eliminated, by substituting dual transistors such as the Rohm UMT1N.

Tim Herklots
Maxim Integrated Products
Reading
B37

Universal active filter

Switching a capacitor in the manner shown in Fig. 1 simulates a resistance having the value $R_{eq} = 1/f_c C_u$, f_c being the clock frequency. In this case, the simulated resistance is used to control the cut-off frequency and Q of a universal active filter.

Figure 2 shows the circuit, a low-pass filter of the second order with the possibility of interchanging the connections to pins 1 and 2 to make a band-pass filter, also of the second order.

In addition, with pin 2 grounded and pin 3 taken to pin 1 - shown by the dotted line - an all-pass filter is the outcome; adding C₂ turns the circuit into a band-stop filter. To get a high-pass filter, interchange C₁ and R_{eq}, place C₂ in parallel with R_{eq} to pin 4 and take the input to C₁.

For all versions, $f_0 = f_c C_u / C_1$ and $Q = C_1 / C_2$. Frequency range lies within the audio band, although the use of current-mode op-amps such as the OPA 603 would extend the range into the megahertz region.

Kamil Kraus
Rokycany
Czech Republic

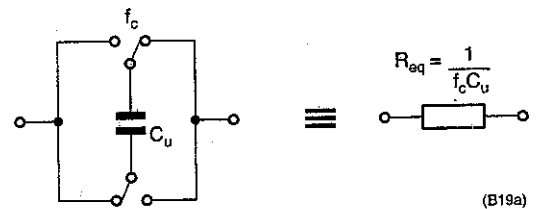


Fig. 1. Switched capacitor simulates a resistance, variable with switching frequency.

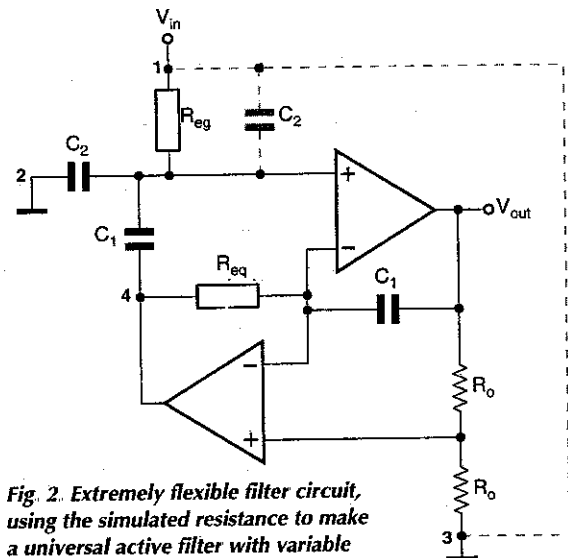


Fig. 2. Extremely flexible filter circuit, using the simulated resistance to make a universal active filter with variable cut-off and Q.