

# INDUCTANCE-CAPACITANCE METER

based on a design by H. Kühne

## FRONT COVER PROJECT


When the value of a capacitor or inductor is measured, it is imperative that ohmic losses do not affect the result. The principle of measurement used in the meter presented here ensures that the influence of ohmic losses is reduced to nil.

**B**ASICALLY, there are two problems in measuring inductance or capacitance: ohmic losses and frequency-dependence of the component. The effect of ohmic losses has been nullified in this design, while the frequency-dependence is, as usual, negated by choosing a measurement frequency that lies in the range in which the component is to operate. In the present design, the frequency lies in the audio range.

The principle of the design is shown in Fig 1. The value of an inductance,  $L_x$ , is determined by passing a sinusoidal current of constant amplitude through the inductor and measuring the resulting voltage across it. The value of a capacitance,  $C_x$ , is determined by applying a constant-amplitude sinusoidal voltage across the capacitor and assessing the resulting current through it by measuring the voltage drop across  $R_C$ . In either case, that voltage (measured at A) is directly proportional to the inductance or capacitance plus the loss resistance. How that resistance is removed from the measurand (measured quantity) will be discussed later.

We will now consider how the current through the inductance, or the voltage across the capacitance, is held constant. The inverting input of the differential amplifier at the input of the circuit is fed with a sinusoidal measurement signal,  $U_E$ , and the non-inverting input with part of the voltage at G,  $U_A$ . Since the gain of the amplifier is unity, the voltage at B is  $U_A - U_E$ . The potential difference between A and B is  $U_A - (U_A - U_E)$ , which is  $U_E$ . Assuming that  $U_E$  is a constant-amplitude sinusoidal voltage depending on the setting of switch  $S_2$ , a constant voltage exists across  $R_L$  or  $C_x$ . This causes a constant current through  $R_L$  and thus through  $L_x$ . Since a constant current flows through the inductance, or a constant voltage exists across the capacitance, the loss resistances,  $R_L$  and  $R_C$ , have no effect on the measurement.

The signal at G consists of two components: a sinusoidal voltage that is *in phase* with  $U_E$  and a sinusoidal voltage that is *90° out of phase* with  $U_E$  ( $\cos U_E$ ). Added together, the components form a sinusoidal voltage that is  $x^\circ$  out of phase with  $U_E$ . The components are separated by synchronous rectification of the signal. The rectifier is driven by a square wave (F) that is shifted 90° with respect to  $\sin U_E$ . That means that only the cosine component in the signal is rectified: the resulting mean value is directly proportional to the inductance or capacitance, whereas rectifi-

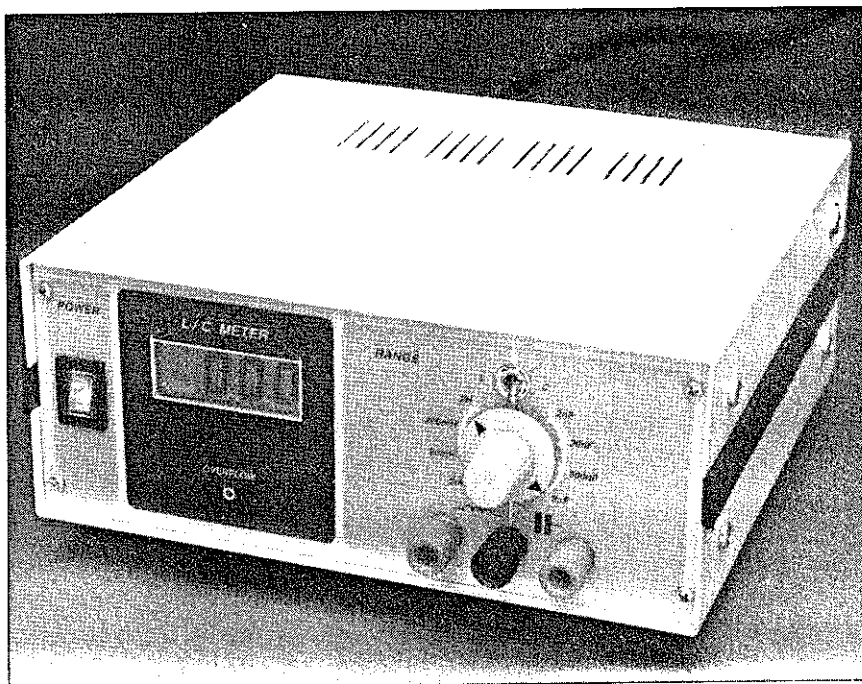

### TECHNICAL DATA

Measurement frequency	1 kHz
Measurement ranges:	
inductance	2, 20, 200 mH, 2 H
capacitance	2, 20, 200 nF, 2 $\mu$ F
Accuracy (calibrated with 1% capacitor)	
with moving-coil meter	$\pm(1.5\% \text{ of reading} + 2\% \text{ of FSD})$
with 3.5 digit digital voltmeter	$\pm(1.5\% \text{ of reading} + 1 \text{ digit})$

cation of the sine component yields a mean value of zero.

The various signals encountered in this process are shown in Fig 2. Figure 2a shows the situation when a perfect inductance or capacitance is being measured. Since ideal components are considered, both the measured signal,  $U_A$ , and the square-wave voltage,  $U_F$ , driving the rectifier are 90° out of phase with  $U_E$ . This means that the rectifier will switch exactly at the zero crossings of the measured signal, which results in a voltage whose mean value is directly proportional to the measured reactance.

If a resistance is substituted for the in-

ductance or capacitance—Fig 2b—the measured signal will be in phase with  $U_E$ . The rectifier then switches exactly at the peaks of the signal, resulting in a mean voltage whose value is zero.

Although practical inductors and capacitors have parasitic or stray resistance, the effect of this is nullified in the synchronous rectification. When a practical inductor or capacitor is measured, the phase shift between the measuring signal,  $U_E$ , and the measured signal,  $U_A$ , will be somewhere between 0° and 90°. This means that the signal is neither wholly rectified nor reduced to zero: the resulting mean value will be representa-

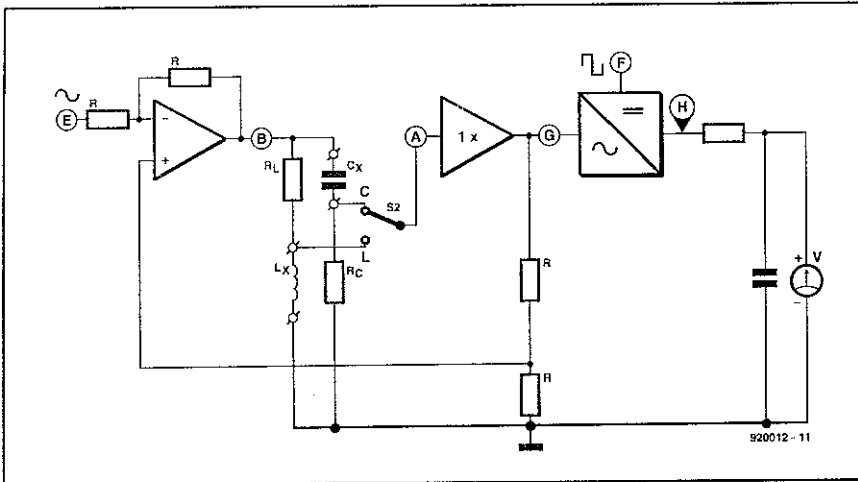


Fig. 1. Principle of the design of the meter.

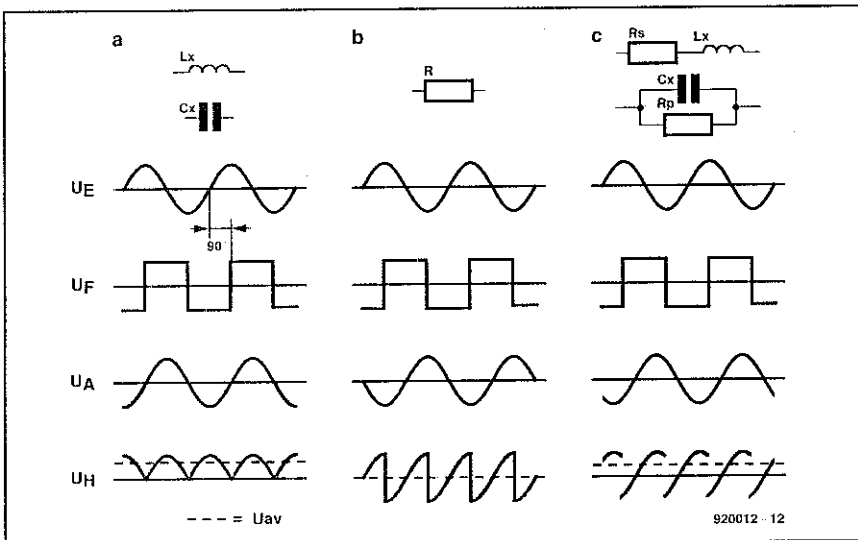


Fig. 2. Waveforms associated with the measurement process.

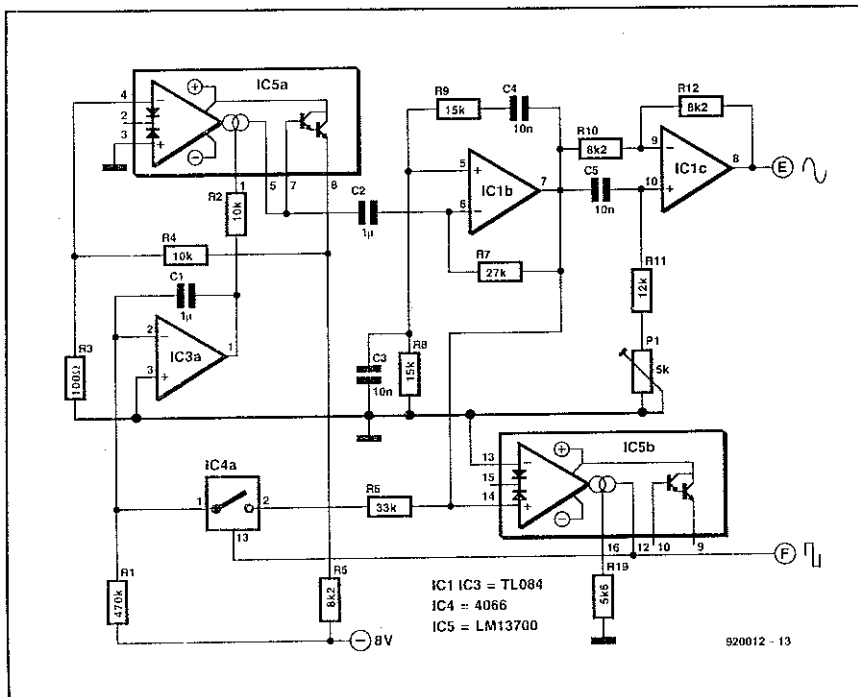


Fig. 3. The oscillator circuit.

tive of the real inductance or capacitance

Returning to Fig. 1 for a moment, the rectifier is followed by an RC network which averages the rectified voltage before that is applied to a meter

**Oscillator**

The measurement signal,  $U_E$ , and the square wave voltage,  $U_F$ , that drives the rectifier are generated by a Wien-bridge oscillator,  $IC_{1b}$ —see Fig. 3. The sinusoidal output of this stage is converted into a square-wave voltage by  $IC_{5b}$ , an operational transconductance amplifier (OTA) connected as a comparator. Since the square-wave and sinusoidal signals are in phase, the latter is applied to phase shifter  $IC_{1c}$ . The required  $90^\circ$  phase difference between the two signals is set with  $P_1$ .

The remainder of the circuit in Fig. 3 serves to stabilize the level of the oscillator output. To that end, the output, pin 5, of  $IC_{5a}$  is used as a preset resistance in the feedback loop of  $IC_{1b}$ . That resistance is determined by the current entering via the control input, pin 1. This current, provided by integrator  $IC_{3a}$ , can be used to influence the gain of  $IC_{1b}$  and thus the amplitude of the sinusoidal signal. Its level is in turn determined by the amplitude of the positive halves of the sinusoidal signal. The negative halves are not passed by switch  $IC_{4a}$  since that is closed by  $IC_{5b}$  only during the positive halves of the signal.

Regulation is arranged so that the gain of  $IC_{1b}$  diminishes when the amplitude increases and vice versa. Ultimately, the amplitude stabilizes around a value of 1.2 V.

**Measuring circuit**

Basically, of course, the measuring circuit in Fig. 4 is similar to Fig. 1 with the rectifier and meter omitted.

The differential input amplifier consists of  $IC_{1d}$ . Its output current is doubled in  $IC_{1a}$ , since the peak level should be about 15 mA, which a single TL084 cannot provide. The design ensures that the level of the voltage across  $R_{17}$  is identical to that across  $R_{16}$ . Consequently, the currents through these resistors are also identical. Observe that one half of the current fed to the measuring circuit is provided by  $IC_{1d}$  and the other half by  $IC_{1a}$ .

Range switch  $S_1$  is provided with a section,  $S_{1c}$ , that enables the decimal points of a digital meter module, if used, to be controlled. In case of an LCD module, the pole of  $S_{1c}$  must be fed with the back-plane (BP) signal or, if an LED display is used, with a logic high or low, depending on the type of the display.

The various ranges are determined with the aid of 0.1% resistors. This has two advantages: calibration of only one range suffices and the tolerance of the resistors has a negligible effect on the total accuracy of the meter (if the tolerance were 1%, the meter accuracy would deteriorate by at least 1%). Note that the 1% resistors in parallel with  $R_{43}$ ,  $R_{47}$ , and  $R_{48}$ , can be ignored since their tolerance is tiny compared with that of the parallel-connected low-value resistors.

### Rectifier and power supply

The remainder of the circuit, that is, rectifier, meter, power supply and overflow indicator, is shown in Fig 5

The rectifier proper, IC<sub>2d</sub>, is preceded by an amplifier, IC<sub>2c</sub>, because the output of the metering circuit at full-scale deflection (FSD) is only 150 mV (assuming a perfect inductance or capacitance) and that is not enough to ensure a mean voltage of 2 V to the meter. The rectifier elements are not diodes, but two electronic switches, IC<sub>4b</sub> and IC<sub>4d</sub>, that are operated by the square-wave signal in step with the sinusoidal output of the oscillator. An inverter based on IC<sub>4c</sub> controls IC<sub>4d</sub>, so that IC<sub>4b</sub> and IC<sub>4d</sub> are alternately opened and closed. When IC<sub>4b</sub> is closed, IC<sub>2d</sub> amplifies  $\times 1$ ; when IC<sub>4d</sub> is closed, IC<sub>2d</sub> amplifies  $\times -1$ . This ensures operation in step with the square-wave signal.

The output of the rectifier is smoothed by network R<sub>27</sub>-C<sub>7</sub>. Because this network can be loaded only lightly, the potential across C<sub>7</sub> is buffered by IC<sub>2a</sub> before the signal is applied to the meter. The meter may be a digital or an analogue type. The digital type may be connected directly to buffer IC<sub>2a</sub>. Series resistors and protection diodes for a moving coil meter are provided.

At first glance, an overflow indicator may seem superfluous, since the meter, M<sub>1</sub> or DM<sub>1</sub>, shows immediately if the meter range is exceeded. That is true enough, but consider that if the meter range is grossly exceeded, IC<sub>2c</sub> will clip and the resulting mean value of the rectified voltage may then fall under 2 V, that is, in the meter range. The meter reading then means nothing and this would not be evident without the overflow indicator.

The indicator is based on IC<sub>3b</sub> (connected as comparator) and IC<sub>3c</sub>. The output of the rectifier is compared by IC<sub>3b</sub> with a voltage set with P<sub>5</sub> to a level of 4 V. If the rectified output exceeds the set level, buffer capacitor C<sub>8</sub> is charged via D<sub>3</sub>. This results quickly to the output of IC<sub>3c</sub> changing state and D<sub>4</sub> lighting.

### Construction and calibration

There should be no particular difficulties in the construction of the instrument if the PCB shown in Fig 6 is used. As usual start with the lowest-lying components, that is, the wire links. When the highest protruding components, that is, electrolytic capacitors, IC<sub>6</sub> and IC<sub>7</sub> and the mains transformer, have been fitted, wire up those components that are not fitted on the board.

The low-tolerance resistors should be soldered direct to the range switch, S<sub>1</sub>. It is, therefore, advisable to use a type of switch that has solder eyelets and not

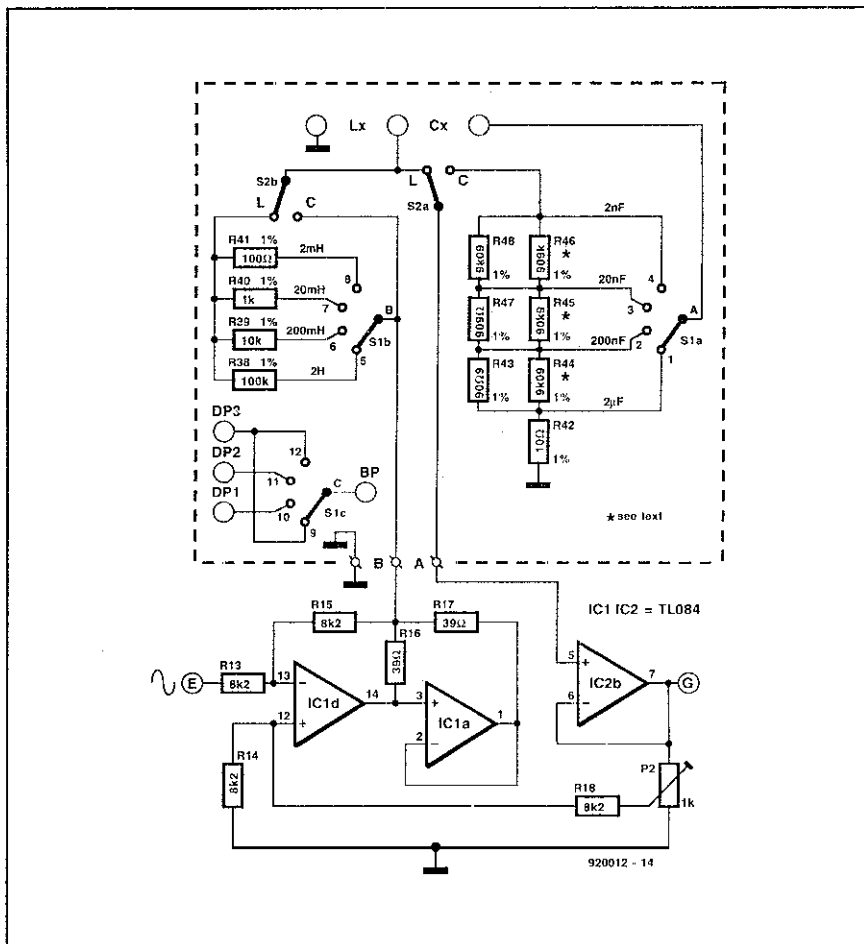


Fig. 4. The metering circuit proper.

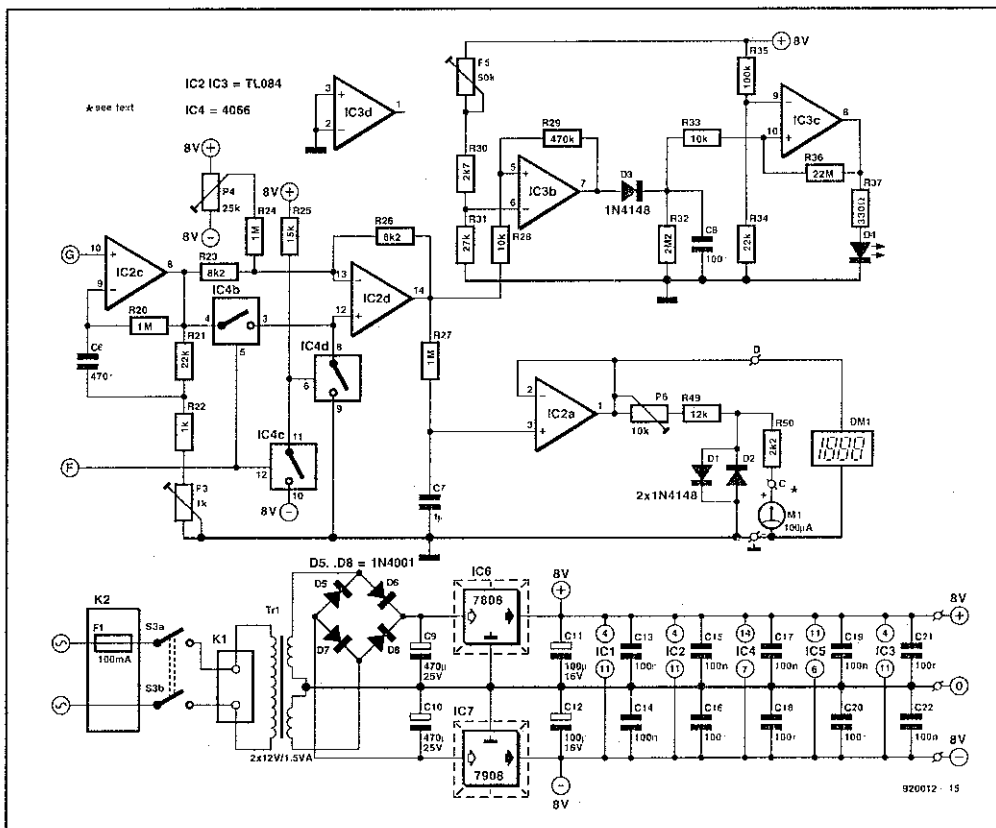


Fig. 5. Circuit of the rectifier, power supply, meter and overflow indicator.

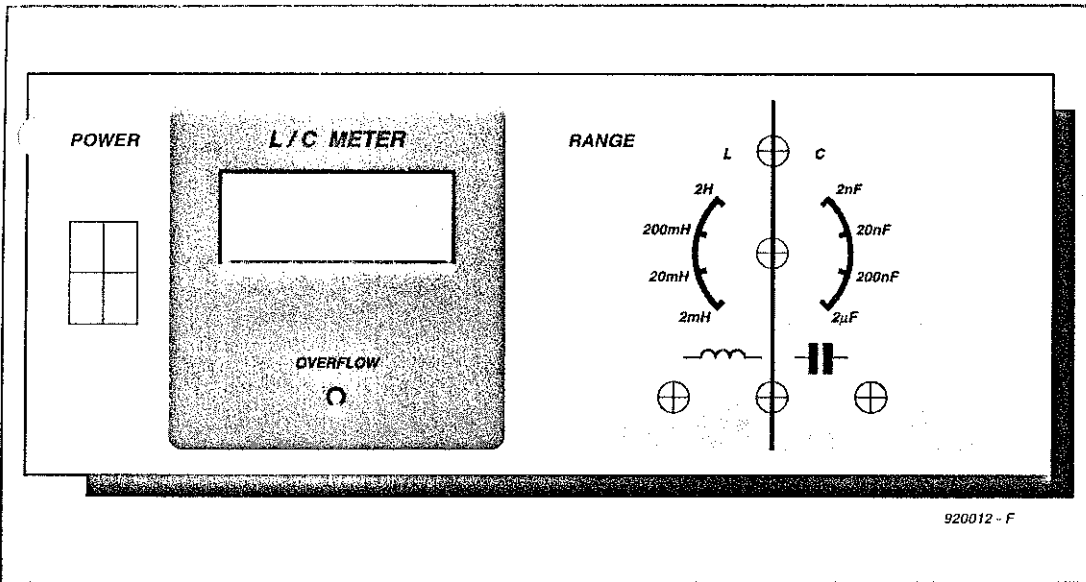


Fig. 6. Proposed front panel layout (foil Type 920012-F).

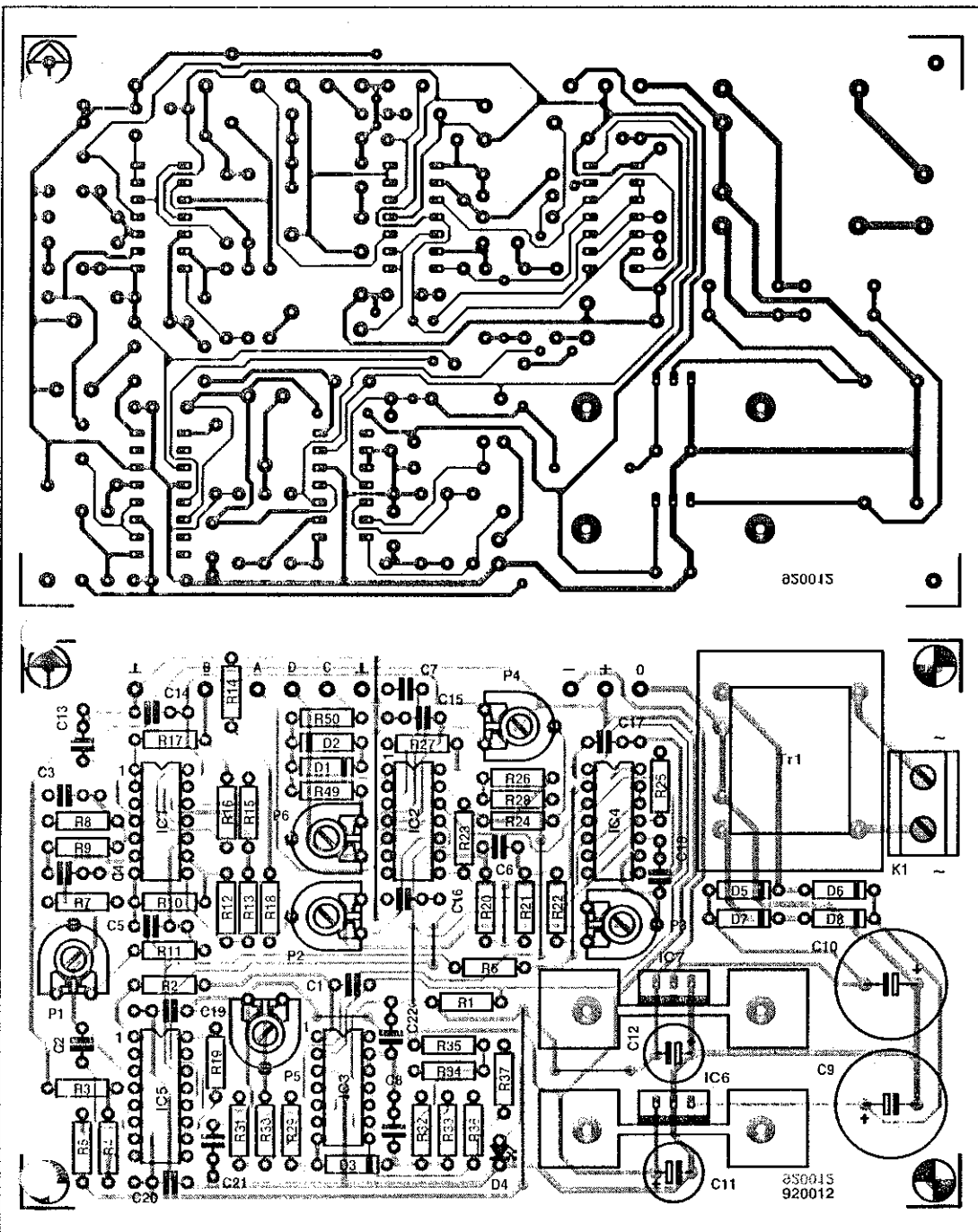


Fig. 7. Printed-circuit board for the inductance-capacitance meter – Type 920012.

**PARTS LIST**

**Resistors:**

- R1, R29 = 470 kΩ
- R2, R4, R28, R33 = 10 kΩ
- R3 = 100 Ω
- R5 R10, R12–R15, R18, R23, R26 = 8.2 kΩ
- R6 = 33 kΩ
- R7, R31 = 27 kΩ
- R8, R9 = 15 kΩ
- R11 = 12 kΩ
- R16, R17 = 30 Ω
- R19 = 5.6 kΩ
- R20, R24, R27 = 1 MΩ
- R21, R34 = 22 kΩ
- R22 = 1 kΩ
- R25 = 15 kΩ
- R30 = 2.7 kΩ
- R32 = 2.2 MΩ
- R35 = 100 kΩ
- R36 = 22 MΩ
- R37 = 330 Ω
- R38 = 100 kΩ, 0.1%
- R39 = 10 kΩ, 0.1%
- R40 = 1 kΩ, 0.1%
- R41 = 100 Ω, 0.1%
- R42 = 10 Ω, 0.1%
- R43 = 90.9 Ω, 0.1%
- R44 = 9.09 kΩ, 1%
- R45 = 90.9 kΩ, 1%
- R46 = 909 kΩ, 1%
- R47 = 909 Ω, 0.1%
- R48 = 9.09 kΩ, 0.1%
- R49 = 12 kΩ
- R50 = 2.2 kΩ
- P1 = 4.7 kΩ preset
- P2, P3 = 1 kΩ preset
- P4 = 25 kΩ preset
- P5 = 47 kΩ preset
- P6 = 10 kΩ preset

**Capacitors:**

- C1, C2, C7 = 1 µF
- C3–C5 = 10 nF
- C6 = 470 nF
- C8, C13–C20 = 100 nF
- C9, C10 = 470 µF, 25 V, radial
- C11, C12 = 100 µF, 16 V, radial (1×180 nF, 1%) for calibrating 2×100 nF, 1%) meters

**Semiconductors:**

- D1–D3 = 1N4148
- D4 = 5 mm LED, yellow
- D5–D8 = 1N4001
- IC1–IC3 = TL084
- IC4 = 4066
- IC5 = LM13700
- IC6 = 7808
- IC7 = 7908

**Miscellaneous:**

- K1 = 2-way terminal block for PCB mounting, 7.5 mm pitch
- K2 = mains panel plug with integral fuse holder and fuse, 100 mA delayed action
- K3–K5 = banana socket
- S1 = 3-pole, 4-position rotary switch with solder eyelets
- S2 = 2-pole change-over switch
- S3 = double-pole, double-throw switch with integral lamp
- Tr1 = mains transformer, 2×12 V, 1.5 VA
- M1 = 100 µA moving-coil meter
- DM1 = 3.5 digit digital voltmeter, 2 V
- Heat sinks for IC6 and IC7
- PCB 920012
- Front panel foil 920012-F

one for PCB mounting. It may be possible to bend these eyelets slightly outwards to give more space for the resistors.

If a digital meter module is used, do not forget to wire switch section  $S_{1c}$ , which controls the decimal points.

In spite of there being six preset potentiometers, the calibration of the instrument is fairly straightforward. Start with setting all the presets to the centre of their travel.

If a moving coil meter is used, connect a voltmeter between D and earth. With the instrument switched off, zero the moving-coil meter manually. When a digital meter is fitted, an external voltmeter is not required.

Set  $S_2$  to position C (capacitor) and leave the input terminals open. Adjust  $P_4$  till the voltmeter (or internal digital meter) reads 0. This arranges the offset compensation.

Connect two 100 nF in parallel to the input terminals and set the range switch to 200 nF. The value of these capacitors need not be accurate, since this test only serves to set the gain of  $IC_{2c}$ . This is done by adjusting  $P_3$  until the voltage at D is 2 V. Because of  $R_{27}$  and  $C_7$  ( $\tau = 1$  s), this voltage rises only slowly;  $P_3$  should, therefore, be adjusted slowly also. When  $P_3$  has been adjusted as required, connect a resistor of 10 k $\Omega$  in parallel with the 100 nF capacitors. Then adjust  $P_1$  to return the voltage at D to 2 V. This arranges the phase difference between sinusoidal and square-wave signals at 90°.

Next, remove the 10 k $\Omega$  resistor, but not the capacitors, from the input terminals. Ideally,  $P_2$  should be set with its wiper at the output of  $IC_{2b}$ . This would, however, create a positive feedback loop with a gain of  $\times 1$ : not exactly conditions for oscillation, but very nearly so. It is, therefore, necessary to connect an oscilloscope to the output of  $IC_{2b}$  and adjust

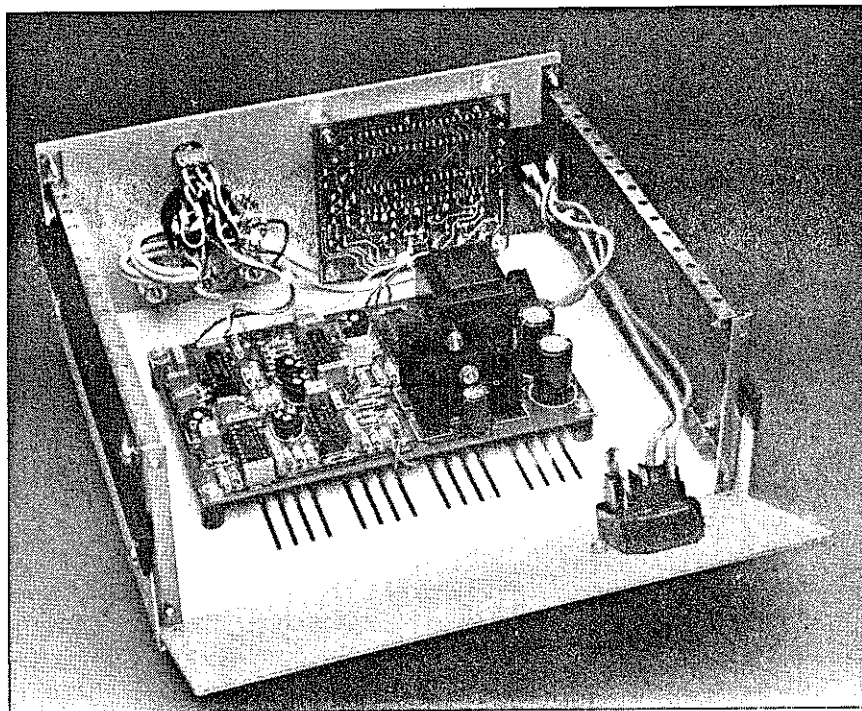


Fig. 8. Inside view of meter with top panel removed and rear panel hinged down

$P_2$  so that oscillation just does not set in. If an oscilloscope is not available, set  $P_2$  to about  $\frac{3}{4}$  of its travel, that is, 750  $\Omega$  between wiper and earth.

If, apart from an oscilloscope, a function generator that provides a triangular output is available,  $P_2$  can be adjusted even more accurately. To that end,  $R_{13}$  must be unsoldered from  $IC_{1c}$  and a 3-V, 1 kHz triangular signal applied across it. An oscilloscope connected to the output of  $IC_{2b}$  will then show a

square wave-form (because of the integrating action of the capacitors at the input). Adjust  $P_2$  so that this wave-form is 'clean', that is, shows no overshoot.

Connect two 100 nF, 1% capacitors (if a moving coil meter is used) or an 180 nF, 1% capacitor (if a digital display is used) to the input terminals and adjust  $P_6$  (moving-coil meter) or  $P_3$  (digital display) until the correct value is read. ■

## MEASUREMENTS ON POWER SUPPLIES

by our technical staff

**How do you know whether your precious laboratory/workshop power supply unit is still working to specification? How do you measure the parameters of the PSU you have just built or purchased for fitting into an electronic apparatus and what do you specifically have to look out for? The answers to these and many other questions connected with the testing of power supplies are given in this practice-based article.**

**T**HE requirements of a laboratory/workshop power supply unit are exacting. Not only the output voltage and current, but also the dynamic and static internal resistance, noise, overshoot and thermal stability, to name but a few, are important. Any electronic apparatus is only as good as its power supply is an adage that remains true.

The extent to which a power supply can be tested depends primarily on the available

test equipment. Normally, the output voltage can be measured with a simple multimeter.

But even this measurement may be more complicated than appears at first sight. Imagine, for instance, that you have obtained a 6 V mains adapter to replace the batteries in a normally battery-operated apparatus, which is not only less expensive in the long run, but also more sensible from an ecological viewpoint. To your surprise, when you measure

the output voltage, it is 9–11 V. The first question that pops into your mind is: "Is it safe to connect to the equipment?" Practical considerations show that there is no harm in that whatsoever. The explanation for this statement is that such a simple mains adapter usually consists of a small transformer, rectifier and reservoir capacitor, nothing more. For all sorts of reason, small transformers generally have a fairly high internal resistance—