

Another interesting application is in the light pointer as used nowadays on projected images in lectures, film shows, and so on. The red-light laser diode is far more suitable than the He-Ne laser for fitting into a reasonably small tubular holder terminated in a convex (focusing) lens. Moreover, it can be powered by alkaline batteries. Such a pointer would cost about a third of the price of an He-Ne laser, and be only a third of the size and weight of an He-Ne laser.

### Use in compact and video disk players?

Believe it or not, the price of a compact or video disk player is determined to a larger extent than generally known by the laser it uses. Why this is so will be clear from the following.

In Fig. 5, light falls on to a convex lens of diameter  $d$ . The lens concentrates the light at principal focus  $F$ , which is a distance  $f$  (the focal length) from the optical centre of the lens. The ray of light along the principal axis passes unhindered through the lens to  $F$ , but most other rays are refracted to points other than  $F$  on the focal plane by an angle,  $\alpha$ , with respect to the principal axis. From the curve at the right of Fig. 5 it is seen that the light-intensity varies around  $F$ . Indeed, when focusing is poor (normally caused by a cheap lens), light at  $F$  is not a sharply defined point, but a disc of diameter  $a$  around the principal focus. This disc

colour	wavelength (nm)
infra-red	1000-740
red	740-620
orange	620-585
yellow	585-575
green	575-500
blue	500-445
indigo	445-425
violet	425-390
ultraviolet	390-5

is bright at its centre and becomes virtually dark at the nulls. Note that by convention the null below the principal axis is negative and that above is positive.

The angle of aberration,  $\alpha$ , is found from

$$\tan \alpha = (a/2)/f, \quad [2]$$

where  $a/2$  is the distance between the nulls and the principal axis.

The angle is also related to the wavelength of the light in the formula

$$\sin \alpha = 1.22\lambda/d \quad [3]$$

These two formulae can be combined provided  $\alpha$  is small (the normal case) into

$$a = 2.44f\lambda/d.$$

In an ideal lens,  $f = d$  so that the diameter of the focal disc is

$$a = 2.44\lambda$$

[4]

To ensure error-free scanning of the pits on the compact or video disc, the focal disc of the light must not be larger than the pits or wider than the tracks between the pits. This has two important consequences.

First, since the wavelength of the light determines the diameter of the focal disc, non-chromatic light will cause several (overlapping) discs. Only a laser will thus give one focal disc.

Second, the smaller the wavelength, the smaller the diameter of the focal disc, and the smaller the pits and track-width of the compact or video disc can be.

Currently, the wavelength of the laser light in CD players is 780 nm. This makes possible a distance of 1.9  $\mu\text{m}$  between tracks and, consequently, about 18 000 tracks on the 33 mm wide recording surface of a CD. If the wavelength of the laser light is brought down to 660 nm, the number of tracks on a CD, and thus the playing time, can be increased by 18%. The same applies to video disks and CD-ROM. ■

### References

"Lasers: an overview"; *Elektor Electronics*, July/August 1987, p. 27.

"The compact disc"; *Elektor Electronics*, July/August 1987, p. 39.


# LCD FOR INDUCTANCE/CAPACITANCE METER

Design by L. Pijpers

The liquid crystal display described in this article and shown in the photograph below is intended primarily for use with the inductance-capacitance meter published last month.

IN the design of a 3½ digit voltmeter module, IC Type ICL7106 has attained virtually the same status as a 555: universally known and suitable for almost any application. It has nearly everything needed on board: an analogue-to-digital (A-D) converter with automatic zero-setting and the required display drivers. All that is needed additionally are a reference voltage source and some passive components.

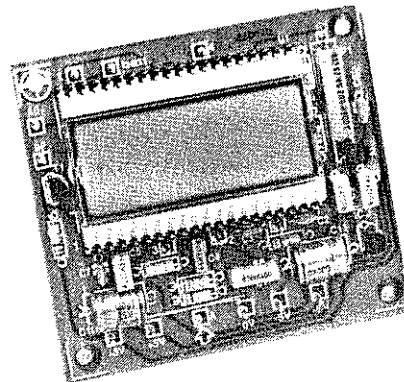The signal that renders the display black must be in anti-phase with the signal at the back-plane (BP) of the display. The same is true for that controlling the decimal points and the LoBat indication. Unfortunately, the 7106 does not provide these signals and, therefore, transistor  $T_1$  has been added to invert the BP signal. By connecting board pins  $dp_n$ ,



$dp_p$  and bat to BP, the associated parts of the display become visible.

If non-connected pins or the LoBat indication pick up noise that causes the relevant information to become visible, the former can be linked to pin 40 (AC) directly and the latter via a 10 M $\Omega$  resistor.

The input circuit is a low-pass filter with a cut-off frequency of 16 Hz that refrains any noise at the input from reaching the A-D converter.

The clock that 'motivates' the 7106 has a frequency determined by  $C_2$ , that makes two measurements per second possible.

Resistor  $R_4$  and capacitors  $C_3$ - $C_5$  form part of the A-D converter circuit.

The supply voltage is high enough to ensure that the reference voltages, connected

## PARTS LIST

## Resistors:

R1 = 22 M $\Omega$   
 R2, R5 = 1 M $\Omega$   
 R3 = 100 k $\Omega$   
 R4 = 470 k $\Omega$   
 R6 = 18 k $\Omega$   
 R7 = 10 k $\Omega$   
 P1 = 10-turn preset, 4.7 k $\Omega$

## Capacitors:

C1 = 10 nF  
 C2 = 150 pF  
 C3, C6, C7 = 100 nF  
 C4 = 47 nF  
 C5 = 220 nF  
 C8, C9 = 330 nF  
 C10, C11 = 100  $\mu$ F, 25 V, radial

## Semiconductors:

T1 = BS170  
 IC1 = ICL7106  
 IC2 = 78L05  
 IC3 = 79L05

## Miscellaneous:

LCD1 = 3 $\frac{1}{2}$  digit display  
 40-pin low-profile IC holder  
 2 off 20-pin terminal strip  
 PCB 920018

to V+ and Comm of IC<sub>1</sub>, are sufficiently stable for the A-D conversion to be accurate to 1 digit. This assumes, of course, that the reference voltages, REF HI and REF LO, have been preset correctly with P<sub>1</sub>. The voltage between REF HI and REF LO must be half the full-scale value, that is, here 1 V. Presetting is easiest by applying a voltage of 1.9 V to the input and adjusting P<sub>1</sub> till the display indicates the same value as the meter with which the input voltage is measured. Do not make the input voltage much higher, because if P<sub>1</sub> is then turned a little too far, IC<sub>1</sub> will indicate an 'overload' which complicates the setting.

To make the circuit suitable for supply voltages of  $\pm 8$ – $\pm 20$  V, it has been provided with two voltage regulators, IC<sub>2</sub> and IC<sub>3</sub>, which provide a supply of  $\pm 5$  V. If such a supply is already available, IC<sub>2</sub>, IC<sub>3</sub> and C<sub>8</sub>–C<sub>11</sub> may be omitted.

The circuit is best built on the printed-circuit board shown in Fig. 2. Start the construction with the wire links and end with placing the display into its holder. Since the display is mounted over IC<sub>1</sub>, it is important that the 7106 is fitted in a low-profile holder. If the display does not fit properly on to the two terminal strips, plug another pair of terminal strips into the first and then the display into the second pair.

It is, perhaps, interesting to note that the type of display specified is also suitable for (diffused) back lighting. ■

## PARAMETERS

Metering range  
 Accuracy  
 Supply voltage

$\pm 2$  V with respect to earth  
 $\pm 1$  digit (see text)  
 Regulated:  $\pm 5$  V  
 Unregulated:  $\pm 8$ – $\pm 20$  V  
 dp1–dp3; ddp (:); LoBat

Display connections

