

Frugal buzzer

Four components make this very simple buzzer. Some n-p-n transistors oscillate at audio and low ultrasonic frequencies when polarity is reversed. Lowest working voltage depends on power rating, but it is about 7-8V for devices such as the BC109, BC337 and BC238, 12V for the BD139 and around 16V for power transistors 2N6543 and BUX22.


Oscillation frequency for the circuit shown is given by the empirical

equation

$$f = (V_b - 5.5) / RC$$

and is constant for devices of the same type. Power requirements are 5mA at 9V, 10mA at 12V; increasing R and decreasing C reduces power drain and also sound output. Higher voltage supplies can be used with increased values of R.

D Di Mario
Milan
Italy

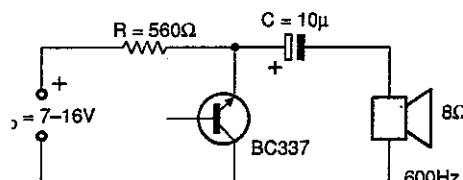

Buzzer using reversed-polarity transistor as oscillator. Since the base is left open, it could be used to gate the buzzer.

10pF-10μF capacitance meter

A very simple circuit using a 555 timer and a few passive components forms a capacitance meter measuring full-scale ranges of 100pF-10μF.

Figure 1 shows the meter circuit, in which the 555 is connected as a free-running multivibrator, the frequency of the output rectangular wave being determined by

$$f = 1/T = 1.44 / (R_A + 2R_B)C,$$

and

$$D = R_B / R_A + 2R_B,$$

T being the period and D the duty cycle, which is made asymmetrical by setting $R_A = R_B$, since charging through the meter takes longer than

discharging via the diode. Unknown capacitors connect points A and B and C takes the form of six components selected by the switch in Fig. 2. If V is the amplitude of the 555 output, current through the meter is $I = VCf$, capacitance being therefore proportional to current for a constant

frequency. The table shows the ranges and frequencies for a 10V supply. Without the damping components $R_{1,2}, C_1$, the meter bounces a little on the highest range, since the frequency is 1Hz; at higher frequencies it is steady.

The charge-pump power supply shown in Fig. 3 also uses a 555 to double the input voltage and produce a 10V output, filtered sufficiently by C_3 . A regulated supply would give better stability.

Calibration in the original was by the use of known capacitors, adjustment being by the trimmer for one range.

Raj K Gorkhali
Kathmandu
Nepal

Fig. 3. Another 555 forms the power supply, a charge-pump voltage doubler to give 10V from the 6V supply.

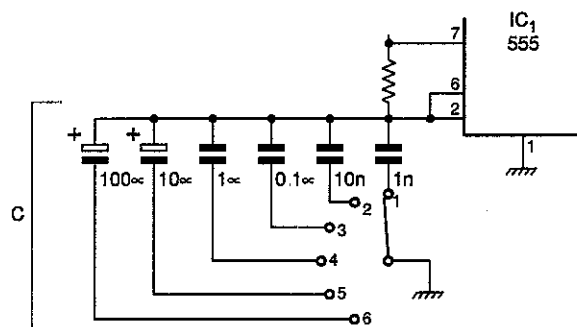


Fig. 2. Range-selection switch.


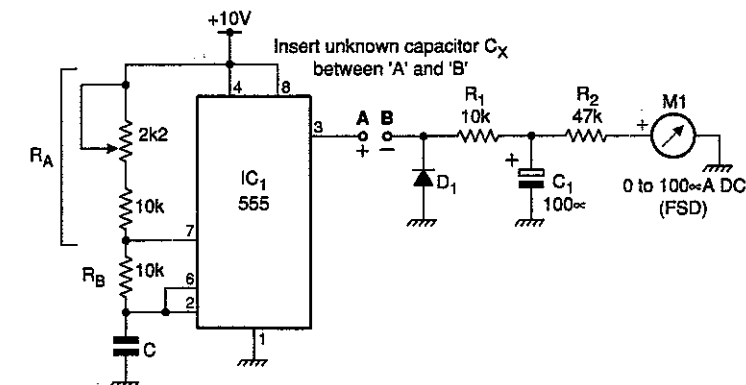


Fig. 1. Linear, direct-reading capacitance meter for values of 10pF-10μF.

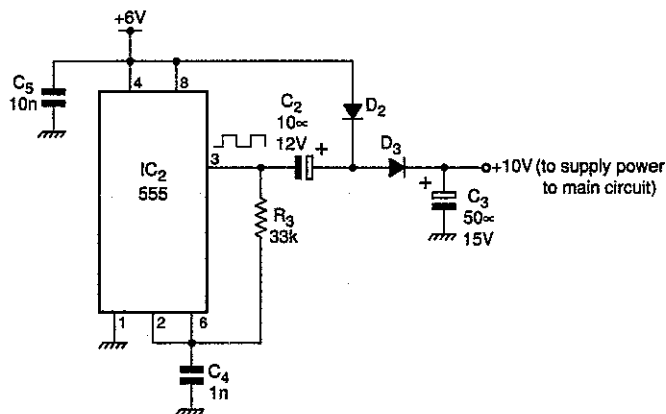