

High-current variable lipstick

If you remove all the metallic parts – and the red part – of a lipstick applicator and substitute a ferrite rod for the lipstick, the result is the core of a variable inductor capable of carrying an alternating current of several amps.

Maximum inductance is given by the standard formula:


$$L = \frac{n^2 A \mu_0 \mu_r}{l} \text{ henries}$$

and the minimum inductance approaches the value given when the relative permeability $\mu_r=1$.

Using the layout shown in the diagram with about 20 turns, inductance ranged from 4-20 μ H with my prototype.

Name not supplied

Edinburgh

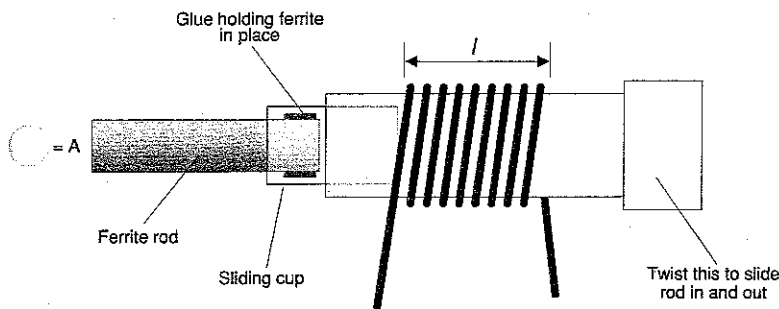

Mechanics of a lipstick make a low-value variable inductor.

Monitor RS-232 activity

Using only a moving-coil voltmeter, you can observe the average activity on an RS-232 link and easily detect oddities.

A centre-zero meter in voltmeter configuration with a suitable series resistor is simply connected between common and the line to be watched.

Since RS-232 transmission is in the form of two voltages with opposite polarity to indicate binary 0 or 1. If you assume one start and one stop bit, maximum usage will show on the meter, scaled for $\pm 100\%$, as zero. Idling shows up as -90% to -100% , fairly busy as -50% to -20% and flat out as -20% to $+20\%$. The region $+20\%$ to $+50\%$ means that something is not quite right. Anything over $+50\%$ indicates a probable fault.

Trim the series resistor to obtain a -100% reading for zero traffic.

Keith Wootten

Reading

Transconductance square rooter

In the simple circuit of Fig. 1, output signal V_o is the square root of input voltage V_i . The circuit is based on the quadratic law connecting I_D and V_{GS} in an enhancement mode mosfet, $I_D = K(V_{GS} - V_T)^2$. This may also be written $V_{GS} = V_T + \sqrt{I_D/K}$, where V_T is the threshold voltage and K is a constant depending on the physical parameters of the mosfet.

Together with Tr_1 , op-amp A_1 forms a voltage follower, so $V_{R2} = V_i$, $I_D = V_i/R_2$ and V_{GS} , which is buffered and referred to ground by a difference amplifier, is then $V_T + \sqrt{(V_i/KR_2)}$.

The second stage allows V_T to be subtracted, through RV_1 , and it allows total gain to be adjusted through RV_2 , in order to obtain $V_o = \sqrt{V_i}$.

To avoid thermal drift problems, the mosfet works close to the threshold voltage, with low values of I_D , where $I_D = f(V_{GS})$ is exponential rather than quadratic. However, a good adherence to the root law can be obtained by iteratively adjusting RV_1 and RV_2 .

Figure 2 shows V_o versus V_i with an input range of 0 to 1V with a root function.

Giorgio Delfitto

University of Padova

Department of Physics

Istituto Nazionale per la Fisica

Nella Materia

Italy

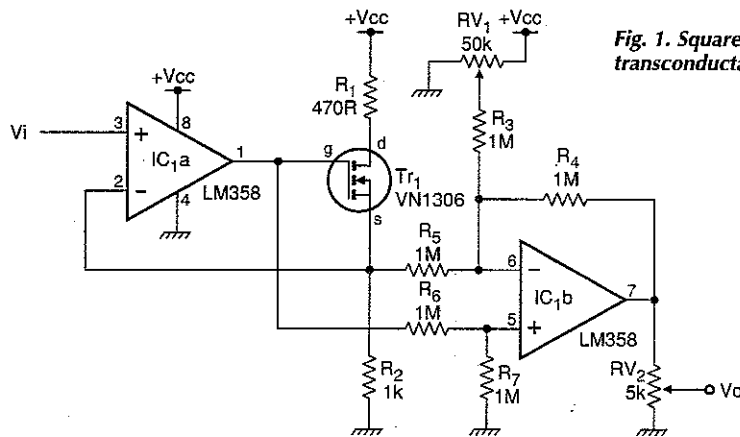


Fig. 1. Square rooting circuit based on transconductance.

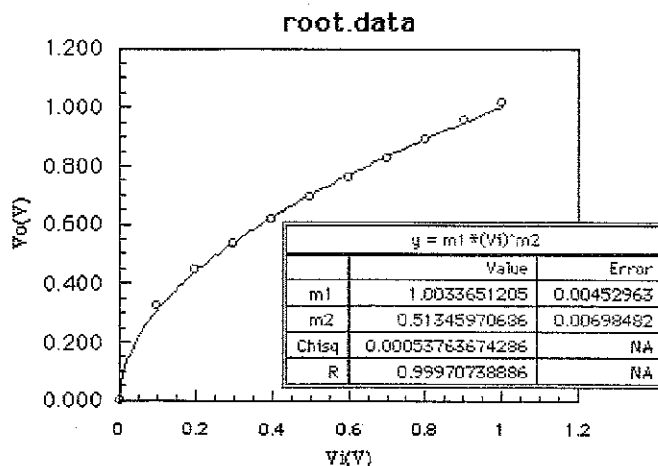


Fig. 2. Graph showing how voltage V_o closely approximates the square root of V_i .