

Here's a quick and easy-to-build device that certainly will come in handy during emergencies.

How To Keep Your Emergency Back-up Station Battery Charged

BY PHIL SALAS*, AD5X

Surplus 12 volt, lead-acid gel-cells are becoming fairly abundant. These are great for emergency backup power for your station, or as a supplement to a low-current power supply so that you can take up any necessary power peaks required by your equipment with the battery. As an example, I've been using a 12 volt, 6 amp-hour battery across the output of a 12 volt, 10 amp small switching power supply. This permits me to run my ICOM IC-706 at full power, since the battery provides the additional peak current requirements (20 amps peak required by the IC-706).

Recently, I found a good deal on a 12 volt, 15 amp-hour lead-acid gel-cell battery. (It cost me \$10!) I wanted to use this for emergency power back-up for my station. Unfortunately, these batteries can be ruined if you let them completely discharge. Therefore, you need to make sure you keep at least a partial charge on your battery. To accomplish this, I occasionally had been hooking up one of those cheap 12 VDC, 500 milliamp wall transformers to the battery in order to keep it charged. However, this has been kind of a hassle, and the battery is not convenient from an emergency-use point of view. So how do you keep these batteries charged and readily available for emergency power for your station?

My solution is shown in fig. 1. The circuit is designed such that the battery is disconnected from the power supply when the power supply is turned off (the relay normally-open contacts are used). I did this because some power supplies have a finite output resistance even when they are off, and we don't want to discharge the battery when everything is off! The charging current is limited to about 6 amps by the 0.47 ohm resistor (this would only occur for a totally discharged battery). The relay contacts can easily handle the 6 amp maximum charging current (RadioShack mini 10 amp relay—RS 275-248). Diode D1 eliminates negative voltage pulses when the relay is de-energized. Diode D2 is needed to make the

relay de-energize when S1 is OFF and the power supply is also turned off.


I built everything into a small plastic box (RS 270-231). I mounted the switch on the long side of the project box. I brought 12-gauge pendant cables (RS 278-1268) out of the project box for the power supply, battery, and station connection. I connectorized the cables with RadioShack nylon 20 amp connectors (RS 274-151 male, RS 274-154 female). These connectors are heavy-duty versions of the standard "RACES-style" connectors. I attached a short 12-gauge cable directly to the battery and connectorized it with a female connector. The battery and power-supply interface cables from the project box should have male connectors on them. The "to the rig" cable from the project box should have a female connector on it.

Normally, you'll leave S1 in the OFF position. When you want to use the battery to power your station, flip S1 ON. This switch is rated for 30 amps, and it does need to have a high current rating, since it must supply the full current demanded of the battery. You'll notice that when you turn S1 ON, the relay coil will draw current from the

battery. This is only around 35 milliamp however. Incidentally, the switch is a lighted switch, but **don't use the internal lamp**. If you connect the switch ground terminal (required for the switch to light), the center pin of the switch is shorted to ground when the switch is OFF. This would short the external power supply in this application.

That's it. This circuit can now stay permanently in line with your station power. Every time you turn on your power supply you'll be keeping the battery topped off. Don't worry about over-charging the cell. It will just "float" charge if your power supply stays on for extended periods (float voltage for these batteries is 13.8 VDC, the same as your power-supply output voltage). Also, don't worry about the diode voltage drop in series with the battery. As the battery approaches full charge, reduced current flows into the battery, and therefore the current through the diode drop. As the diode current drops, the diode voltage drop also becomes less. Theoretically when the battery is fully charged, no current will flow, so there is no voltage drop.

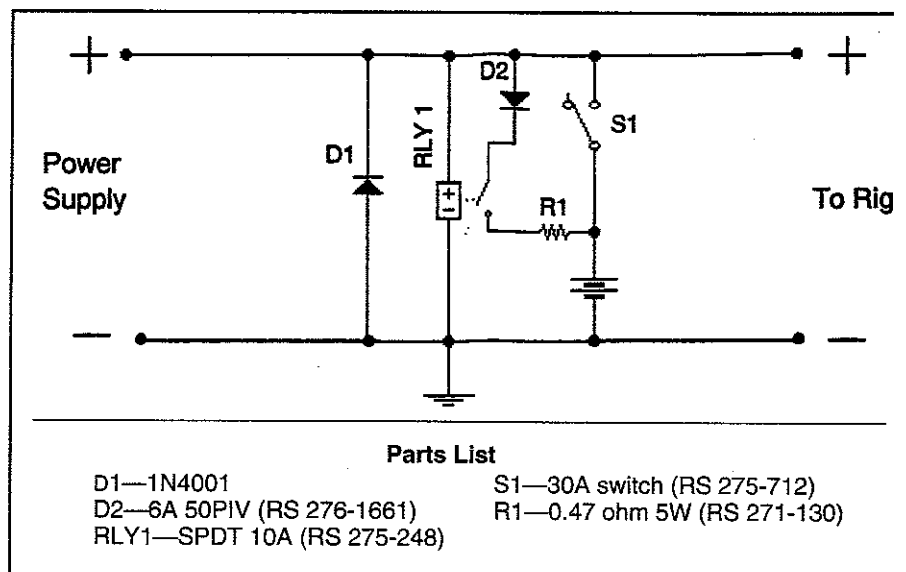Now you're all set if you need emergency power!



Parts List

- | | |
|----------------------------|-----------------------------|
| D1—1N4001 | S1—30A switch (RS 275-712) |
| D2—6A 50PIV (RS 276-1661) | R1—0.47 ohm 5W (RS 271-130) |
| RLY1—SPDT 10A (RS 275-248) | |

*1517 Creekside Drive, Richardson, TX 75081

Fig. 1—The battery charger circuit.