

SIMPLIFIED TIME-SIGNAL RECEIVER

The automatic synchronization facility of many microprocessor-based clocks ensures reasonable long-term accuracy even when the relevant time-signal transmitter is received for only a couple of minutes each day. Obviously, this feature relaxes the design requirements of the receiver, which can be kept relatively simple. Such a receiver is described here: it has a digital pulse output, excellent sensitivity, and can be tuned to time-standard stations transmitting in the VLF band between 50 and about 100 kHz.


Time-signal transmitters such as Rugby MSF, HBF and DCF77 operate in the VLF (very low frequency) band, at frequencies between 50 and 100 kHz. The VLF band is characterized by very predictable propagation characteristics, but received signals often suffer from interference generated by electrical apparatus such as TV sets and dimmers. The receiver should, therefore, have good or very good selectivity. The frequency conversion principle (heterodyne receiver) must be dismissed, however, when the practical design is to remain as simple as possible.

Circuit description

Selectivity of the present VLF receiver is determined solely by the aerial and two tuned circuits. High-gain RF amplifiers are used, and a special, non-linear, demodulator extracts the time signals from the still relatively noisy RF input signal.

The circuit diagram of Fig. 1 shows that the RF signal from the transmitter is picked up by an active aerial circuit, whose output signal is filtered by tuned circuit L_1-C_2 , and amplified by dual-gate MOSFET T_1 . A further tuned circuit inserted in the drain line of this transistor ensures adequate receiver selectivity. The drain signal is rectified by D_1 to provide automatic gain control (AGC) on gate 1 of the MOSFET. The AGC has a relatively slow response because fading is generally slow on VLF.

Circuit IC_1 is a Type SO42P balanced mixer/oscillator from Siemens. In the present application, it functions as a four-quadrant multiplier, so that its output signal is proportional to the square of the input signal provided by T_1 . The modulation frequency on DCF77 is relatively low, so that a single R-C network, R_8-C_{15} , is sufficient for removing the RF component from the rectified time signals. These are filtered and shaped in a further (active) rectifier, IC_2 , whose output signal is a measure of the instan-

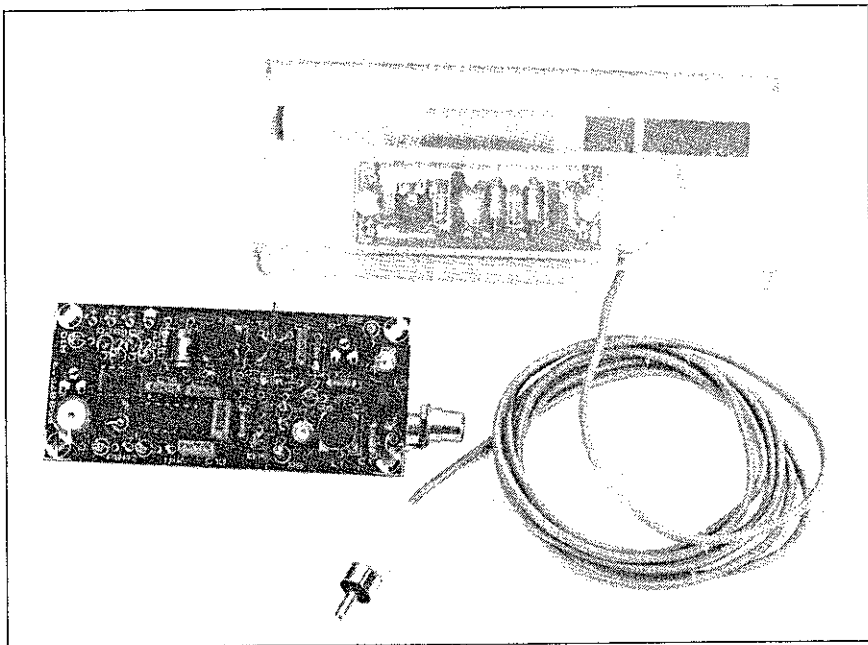

Completed prototype of the simplified time signal receiver, connected to the associated active aerial.

taneous amplitude of the time signals. The discharge time of C_{16} is relatively long (P_2-R_{10}), so that the voltage on this capacitor is largely constant for the duration of the time pulses. Comparator IC_2 compares the instantaneous amplitude of the rectified voltage to a part of the absolute amplitude, set with P_2 . The output of the receiver supplies time pulses as they are modulated, i.e., a time pulse corresponds to a logic low level. This makes the present time signal receiver compatible with the Intelligent Time Standard published in Ref. (2), but only if DCF77 is being received. The circuit diagram shows the capacitor values needed for reception of DCF77 on 77.5 kHz. The tuned circuits can be modified for reception of, for instance, Rugby MSF at 60 kHz, by multiplying the value of C_2 , C_7 and C_8 by a factor $(77.5/60)^2 \approx 1.67$, and using the closest practical capacitor value.

Construction and alignment

The receiver is composed of two boards: active aerial and receiver/demodulator. The active aerial is identical to that used for the DCF77 receiver and locked frequency standard (see Ref. (1)). The unit is constructed on the small printed circuit board shown in Fig. 2. The aerial, L_5 , is formed by about 200 closewound turns of 0.2 mm dia enamelled copper wire on a 30 mm long cardboard or paxolin former. This is slid on to a 12-20 cm long ferrite rod of 10 mm diameter. The rod and associated former used for building the prototype receiver were parts salvaged from a discarded MW/LW radio.

Populating the receiver/demodulator board shown in Fig. 3 should not present problems. A 15 mm high tin plate or brass screen is fitted across T_1 as shown

on t
has
is se
sold
of p

Use
pho:
the
Firs
tive
setti
cuit
to
77.5
and
inst
to t
couj
acti

fr
ac

Fig

on the component overlay. The screen has small clearances for T₁ and R₃, and is secured to the PCB with the aid of two soldering terminals. Note that a number of parts are fitted upright.

Use one metre or so of screened microphone wire to connect the active aerial to the main receiver board.

First, concentrate on setting up the active aerial. Power up and check the DC settings at the points indicated in the circuit diagram. Set a sine-wave generator to the receiving frequency (e.g., 77.5 kHz), and connect a coupling loop and a series resistor to the output of the instrument. Wind the coupling loop on to the ferrite rod, and connect an AC-coupled oscilloscope to the output of the active aerial. Slide the former until the

signal amplitude is a maximum. Reduce the output of the generator, and move the coupling loop away from the rod.

Again slide the former on the rod to find the resonance point. If this is found with the former partially off the rod, the number of turns of L₅ should be reduced. Experiment with the value of C₄₄ and the setting of P₂ until the completed active aerial has a selectivity of about 10 kHz, and the former is about flush on the rod. When this cannot be achieved, the ferrite rod may have incorrect RF properties, and there is no alternative but to try out another type. After adjustment, the former is secured on the ferrite rod by means of wax or sellotape. Do not use a metal support for fixing the rod.

Switch off the generator, increase the sensitivity of the scope, and rotate the rod in the horizontal plane until the RF signal from the time signal station is observed on the oscilloscope screen. The signal is relatively small, but should have an amplitude between 5 and 50 mV_{pp}. Connect the probe to the drain of T₁, and carefully peak L₁ and L₂ for maximum amplitude. If clipping or oscillation occurs, reduce the gain of T₁ by adjusting P₁. Readjust the active aerial and the tuned circuits with a high-impedance voltmeter connected to pin 2 of IC₁.

The time signals can be heard on high-impedance (600 Ω) headphones connected between the positive supply and test point TP2. Finally, mount the active aerial in a position well away from

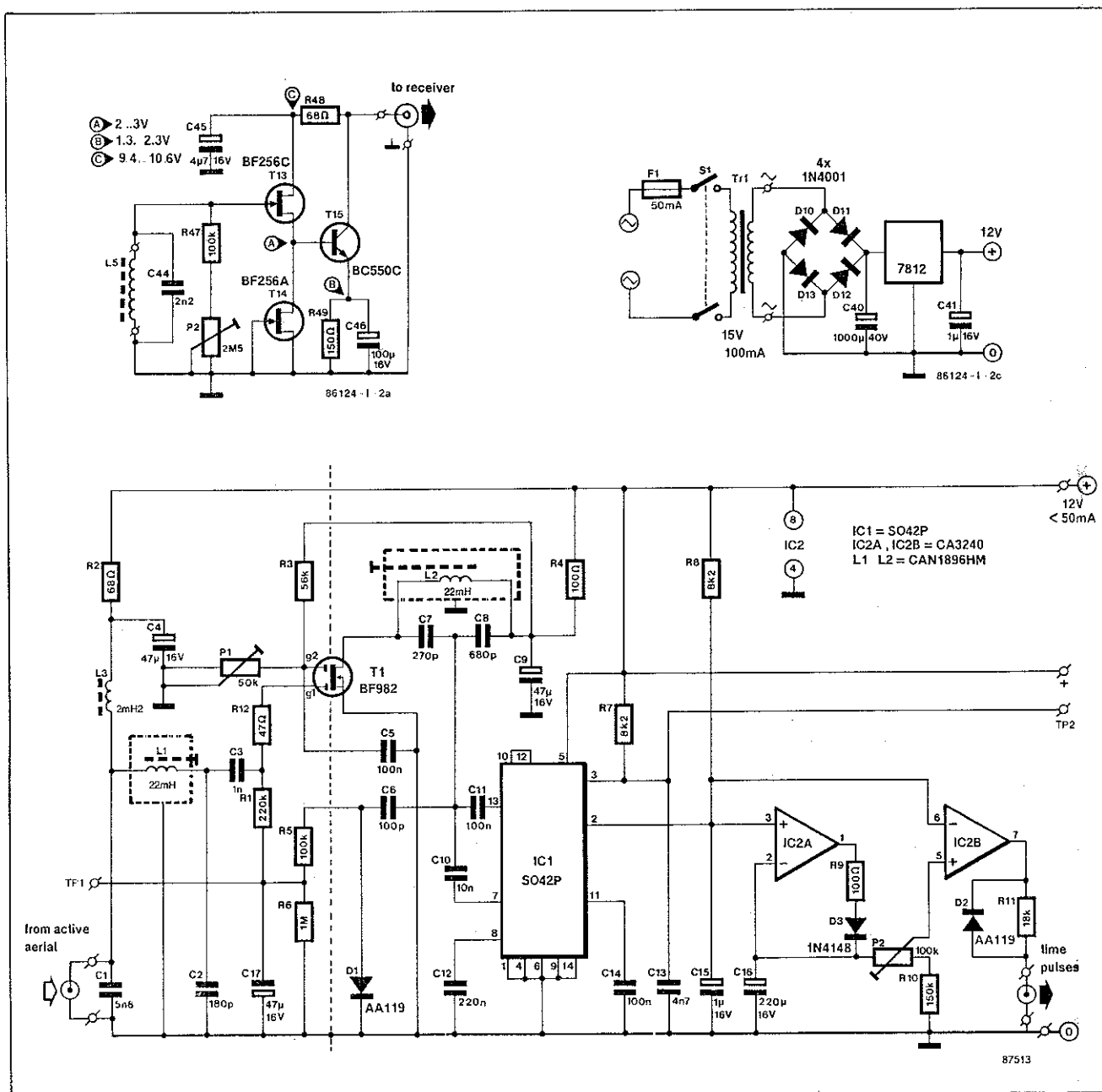


Fig. 1 Circuit diagram of the VLF time signal receiver.

sources of interference. The length of the screened cable between the active aerial and the main receiver board should not exceed 15 m or so

References:

- (1) DCF77 receiver and locked frequency standard. *Elektor Electronics* January 1988, p. 24-29.
- (2) Intelligent time standard. *Elektor Electronics* February 1988, p. 22-30.

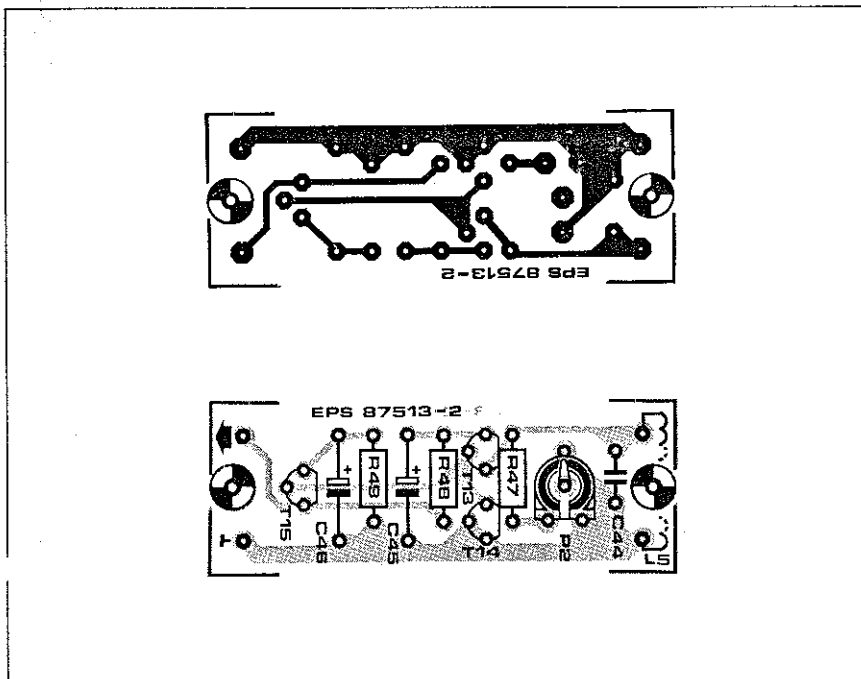


Fig. 2. Printed circuit board for the active aerial.

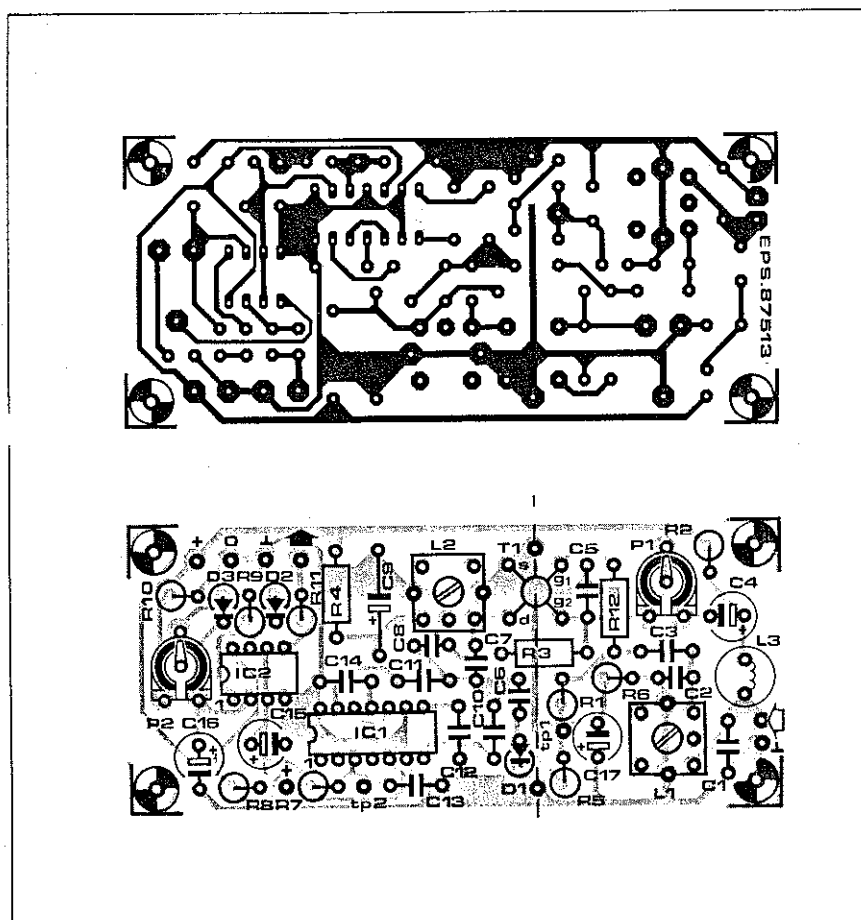


Fig. 3. Printed circuit board for the time signal receiver/demodulator.

Parts list

ACTIVE AERIAL:

Resistors ($\pm 5\%$):

R47 = 100K
R48 = 68R
R49 = 150R P2 = 2M5 preset H

Capacitors:

C44 = 2n2
C45 = 4 μ 7; 16 V; radial
C46 = 100 μ ; 16 V; radial

Semiconductors:

T13 = BF256C (Cricklewood)
T14 = BF256A (Cricklewood)
T15 = BC550C

Inductor:

L6 = see text Ferrite rod: e.g. Cirkit Type FRA (stock number 35-14147)

Miscellaneous:

PCB Type 87513-2 (see Readers Services page)

MAIN RECEIVER BOARD:

Resistors ($\pm 5\%$):

R1 = 220K
R2 = 68R
R3 = 56K
R4; R9 = 100R
R5 = 100K
R6 = 1M0
R7; R8 = 8K2
R10 = 150K
R11 = 18K
R12 = 47R
P1 = 50K preset H
P2 = 100K preset H

Capacitors:

C1 = 5n6
C2 = 180p
C3 = 1n0
C4; C17 = 47 μ ; 16 V; radial
C5; C11; C14 = 100n
C6 = 100p
C7 = 270p
C8 = 680p
C9 = 47 μ ; 16 V; axial
C10 = 10n
C12 = 220n
C13 = 4n7
C15 = 1 μ 0; 16 V; radial
C16 = 220 μ ; 16 V; radial

Inductors:

L1; L2 = 22mH variable; Toko 10PA series Type CAN1896HM (Cirkit stock number 35-18960)
L3 = 2mH2 radial choke; Toko Type 181LY-222 (Cirkit stock number 34-22202)

Semiconductors:

D1; D2 = AA119
D3 = 1N4148
T1 = BF982 (C-1 Electronics)
IC1 = SO42P (Bonex; C-1 Electronics; Universal Semiconductor Devices Ltd.)
IC2 = CA3240

Miscellaneous:

PCB Type 87513-1 (see Readers Services page)

Note: PCB Types 87513-1 and 87513-2 are supplied as a set and cannot be ordered separately

T

GE
Gen

Made
has
13 M
count
lator
retail
For a
813
weigh
380 n
5 kg.
The i
120-2
suppl
The i
acces
BNC
termi
an in
The
positi
GFG
angle
The
domi
which
contr
gener
a sep
erato

Main
sets t
the f
grada
put fr
accur
the r
trol, a
Fine
settin
other
kind
been
The f
eight
13 M
0.05 I
be ad
20:80
The
20 V

sources of interference. The length of the screened cable between the active aerial and the main receiver board should not exceed 15 m or so.

References:

- (1) DCF77 receiver and locked frequency standard *Elektor Electronics* January 1988, p. 24-29.
(2) Intelligent time standard *Elektor Electronics* February 1988, p. 22-30.

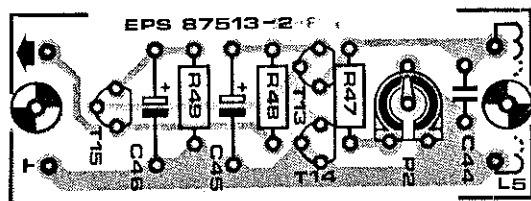
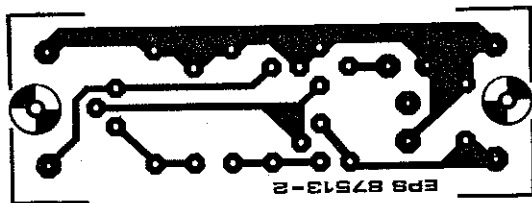


Fig. 2. Printed circuit board for the active aerial.

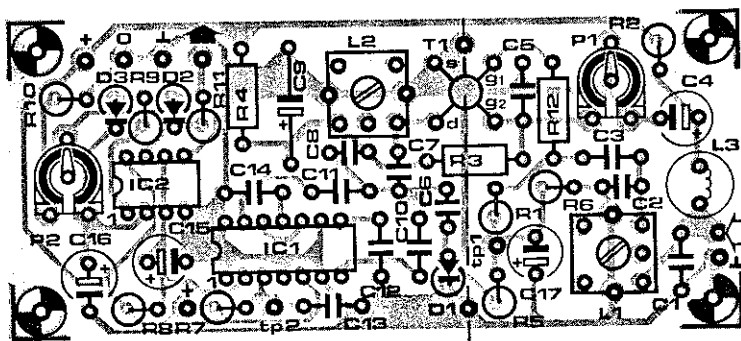
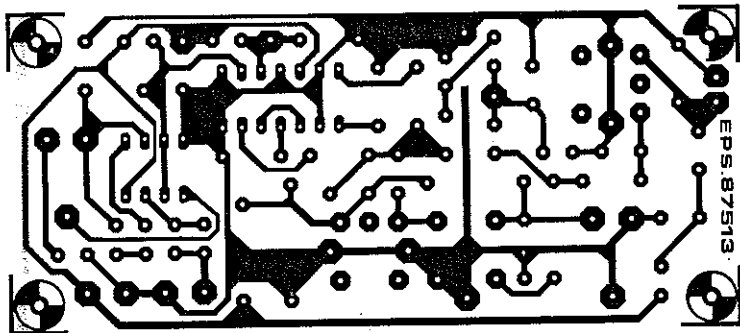


Fig. 3. Printed circuit board for the time signal receiver/demodulator.

Parts list

ACTIVE AERIAL:

Resistors ($\pm 5\%$):

R47 = 100K
R48 = 68R
R49 = 150R P2 = 2M5 preset H

Capacitors:

C44 = 2n2
C45 = 4 μ 7; 16 V; radial
C46 = 100 μ ; 16 V; radial

Semiconductors:

T13 = BF256C (Cricklewood)
T14 = BF256A (Cricklewood)
T15 = BC550C

Inductor:

L5 = see text Ferrite rod; e.g. Cirkit Type FRA (stock number 35-14147).

Miscellaneous:

PCB Type 87513-2 (see Readers Services page)

MAIN RECEIVER BOARD:

Resistors ($\pm 5\%$):

R1 = 220K
R2 = 68R
R3 = 56K
R4; R9 = 100R
R5 = 100K
R6 = 1M0
R7; R8 = 8K2
R10 = 150K
R11 = 18K
R12 = 47R
P1 = 50K preset H
P2 = 100K preset H

Capacitors:

C1 = 5n6
C2 = 180p
C3 = 1n0
C4; C17 = 47 μ ; 16 V; radial
C5; C11; C14 = 100n
C6 = 100p
C7 = 270p
C8 = 680p
C9 = 47 μ ; 16 V; axial
C10 = 10n
C12 = 220n
C13 = 4n7
C15 = 1 μ 0; 16 V; radial
C16 = 220 μ ; 16 V; radial

Inductors:

L1; L2 = 22mH variable; Toko 10PA series, Type CAN1896HM (Cirkit stock number 35-18960)
L3 = 2mH2 radial choke; Toko Type 181LY-222 (Cirkit stock number 34-22202)

Semiconductors:

D1; D2 = AA119
D3 = 1N4148
T1 = BF982 (C-I Electronics)
IC1 = SO42P (Bonex; C-I Electronics; Universal Semiconductor Devices Ltd.)
IC2 = CA3240

Miscellaneous:

PCB Type 87513-1 (see Readers Services page)

Note: PCB Types 87513-1 and 87513-2 are supplied as a set and cannot be ordered separately