

An Inexpensive Charger for Lithium-Ion Batteries

As we get ready for the warmer weather and dust off our portable equipment, the subject of batteries always comes to mind. But before rushing out to replace those Ni-Cads, zinc-carbons, and alkaline power sources, consider the latest.

As some of you may be aware, the newest rechargeable battery on the scene is the one using lithium-ion technology. This battery offers performance superior to the common nickel-cadmium type, since it does not have a "memory" and can be trickle charged continuously. You never have to "deep discharge" or recondition these devices, and even disposal is safe for the environment. Furthermore, individual lithium-ion cells provide 3 to 4.1 volts, which is much closer to the voltages needed by modern integrated circuits (such as the emerging 3.6 volt devices) than 1.2 volt Ni-Cads or 1.5 volt zinc-carbons. There is a small problem, however. Lithium-ion batteries are somewhat difficult to charge, since they require a constant current/constant voltage circuit that is quite different from their Ni-Cad counterparts. Fortunately, Linear Technologies has made the

job much easier with a new chip, which we describe this month.

The device we are referring to is the LTC1541. This chip, as shown in fig. 1, contains a precision voltage reference, comparator, and op amp which can be easily and inexpensively interconnected to form a complete lithium-ion charger, as we soon will see. It comes in an 8-pin package and contains no real surprises. The reference, by the way, is accurate to $\pm 0.4\%$ and the chip can be used for other applications needing these components as well.

The complete lithium-ion battery charger/input power supply is shown in fig. 2. In operation, the 2N2907 controls the battery charging current. It is driven by the output of the internal op-amp via the 2N3906. Since this portion of the circuit operates in a linear mode, the 2N2907 will dissipate up to 1 watt and should be adequately heat-sunk. The 0.15 ohm resistor senses battery charging current and feeds it to the positive op-amp input via the 2N3906. The internal reference is divided to 44 millivolts by the 100K and 3.83K resistors and applied to the negative or inverting input. The difference between the two drives the 2N2907 to produce 300 ma of charging current. At the same time, the divided bat-

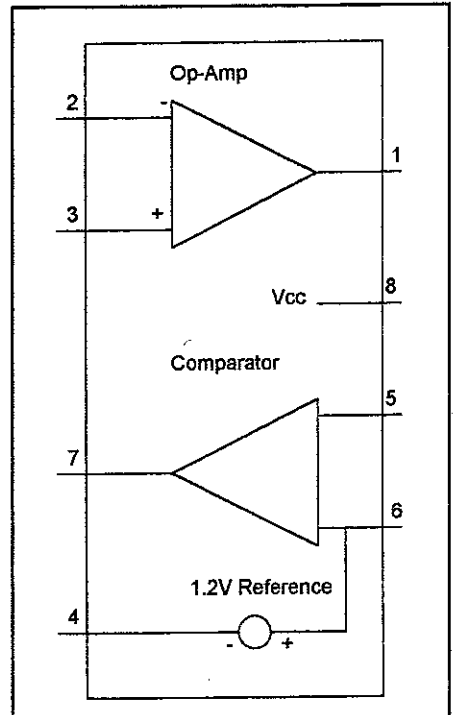


Fig. 1— Internal block diagram of the LTC1541.

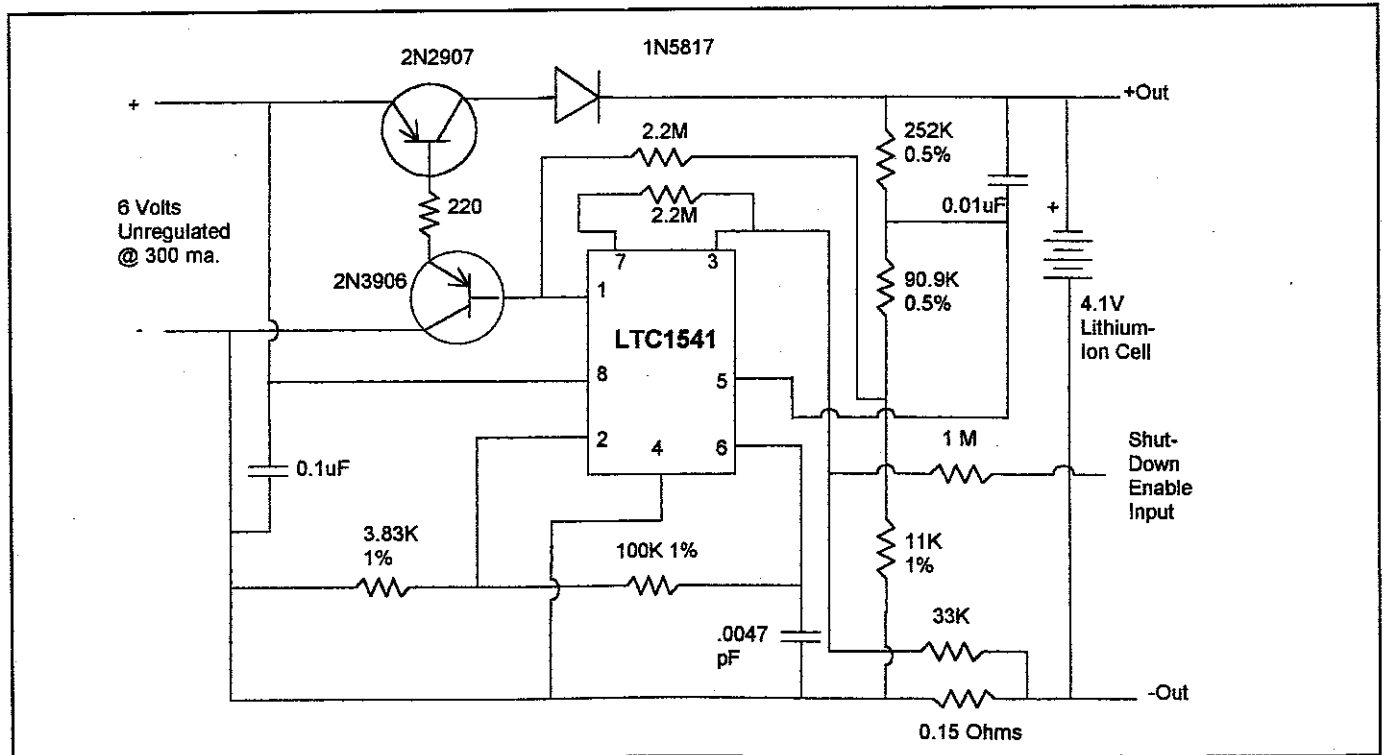


Fig. 2— Complete lithium-ion battery charger circuit.

tery voltage present at the junction of the 252K and 90.0K resistor is applied to the positive comparator input at pin 5. This is compared to the reference (internally connected to pin 6), and when 4.1 volts is reached, shuts down the linear regulator by controlling the op-amp via pin 3. A shut-down input is also provided to turn off the LTC1541 when the charging function is not required. This can be used to reduce current drawn by the chip when the battery is being used to power the external circuit.

Since both charging current and voltage are regulated by this circuit, the unregulated 6 volt input source is not critical and can come from a wall-type adapter. If the battery is also connected to the external circuitry it will power, the circuit will share the current. This means that with no external load, all current will be used to charge the battery. With some external load, the battery charging current will reduce in proportion to the current drawn by the load. In this way the circuit can be used to both charge the battery and power external circuitry at the same time. Now you can have an AC line powered device (via the wall adapter) which continues to operate in the event of a power failure. Pretty neat stuff!

If you require more information on this device, contact Linear Technologies at 1630 McCarthy Blvd., Milpitas, CA 95035-7417 (1-800-4-LINEAR, or on the web at <www.linear-tech.com>).

73, Irwin, WA2NDM

ORGANIZE AND PROTECT YOUR COPIES OF CQ

Now there's an easy way to organize and keep copies of your favorite magazine readily available for future reference.

Designed exclusively for CQ by Jesse Jones Industries, these custom-made titled cases and binders provide the luxury look that makes them attractive additions to your bookshelf, desk or any location in your home or office.

Each binder/case is covered durable leather-like material; title is hot stamped in gold.

Whether you choose cases or binders, you'll have a storage system that's durable and well organized to help protect your valuable copies from damage.

Quantity	Cases	Binders
One	\$ 8.95	\$11.25
Three	\$24.95	\$31.85
Six	\$45.95	\$60.75

Add \$1.50 per case/binder for postage and handling. Outside USA \$3.50 per case/binder. (U.S. funds only)

Credit cards accepted: AMEX, Visa, MC, Diners Club (Min. \$15) PA Residents add 7% sales tax Allow 4 to 6 weeks delivery

CQ Amateur Radio
Jesse Jones Industries, Dept. 95 CQ
499 East Erie Ave., Phil., PA 19134
1-800-825-6690

Say You Saw It In CQ

Amplifiers, ATU Down Converters & Hard-to-Find Parts

LINEAR AMPLIFIERS

HF Amplifiers
PC board and complete parts list for HF amplifiers described in the Motorola Application Notes and Engineering Bulletins:

AN779H (20W) AN 758 (300W)
AN779L (20W) AR313 (300W)
AN 762 (140W) EB27A (300W)
EB63 (140W) EB104 (600W)
AR305 (300W) AR347 (1000W)

2 Meter Amplifiers
(144-148 MHz)
(Kit or Wired and Tested)

35W - Model 335A, \$79.95/\$109.95
75W - Model 875A, \$119.95/\$159.95

HARD-TO-FIND PARTS

- RF Power Transistors
- Broadband HF Transformers
- Chip Caps - Kermet/ATC
- Metalclad Mica Caps - Unelco/Semco
- ARCO/SPRAGUE Trimmer Capacitors

We can get you virtually any RF transistor!
Call us for "strange" hard to find parts!

ATU Down Converters

(Kit or Wired and Tested)
Model ATV-3 (420-450)
(Ga AS - FET) \$49.95/\$69.95
Model ATV-4 (902-926)
(GaAS - FET) \$59.95/\$79.95

For detailed information and prices, call or write for our free catalog!

Phone
(937) 426-8600
FAX
(937) 429-3811

CCI Communication Concepts Inc.

508 Millstone Drive • Beavercreek, Ohio 45344-5840

e-mail: cci.dayton@pobox.com

www.communication-concepts.com

ADDITIONAL ITEMS


Heat Sink Material
Model 99 Heat Sink (6.5" x 12" x 1.6"), \$25
CHS-8 Copper Spreader (8" x 6" x 3/8"), \$24
Low Pass Filters (up to 300W)
for harmonics \$12.95
Specify 10M, 15M, 20M, 40M, 80M or 160M
HF Splitters and Combiners up to 2KW

CIRCLE 43 ON READER SERVICE CARD

QRO AMPLIFIERS™ DELIVER HIGH PERFORMANCE, SUPERIOR QUALITY, AND EXCEPTIONAL DURABILITY FOR A REASONABLE COST!

QRO HF-2000 NON-QSK

Price: \$1,795 US Dollars FOB Bryan, Ohio USA
Band Coverage: 160,80,40,20,17,15 (12 & 10 export; also usable in U.S.A. with license)
Output Power: 1500 W SSB, 1200 W CW
Drive Power: 120 watts for 1,500 watts output
Tube: Amperex 3-500ZG triode (2)
Transformer: 21 lb. Light Duty Hypersil
Line Voltage Requirement: 100/120/200/240V, 50/60Hz
Cabinet Size: 18" w x 15" d x 8-1/2" h
Shipping Wt: 65 lbs. UPS three cartons

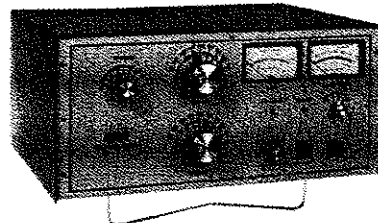

Tube: Svetlana 4CX1600B Tetrode (1)

QSK: Standard Feature

Line Voltage Requirement: 200/240V, 50/60Hz

Cabinet Size: 20" w x 19" d x 8" h

Shipping Wt: 100 lbs. UPS three cartons

QRO HF-2000 QSK

Price: \$2,095 US Dollars FOB Bryan, Ohio USA
Band Coverage: 160,80,40,20,17,15 (12 & 10 export; also usable in U.S.A. with license)
Output Power: 1500 W SSB, 1200 W CW
Drive Power: 120 watts for 1,500 watts output
Tubes: Amperex 3-500ZG triodes (2)
QSK: Standard Feature (Vacuum Relay)
Transformer: 32 lb. Heavy Duty Hypersil
Line Voltage Requirement: 100/120/200/240V, 50/60Hz
Cabinet Size: 18" w x 15" d x 8-1/2" h
Shipping Wt: 76 lbs. UPS three cartons

QRO HF-3KDX Mark II

(Export, Industrial, Scientific, and Medical Sales Only)

Price: \$4,295 US Dollars FOB Bryan, Ohio USA

Band Coverage: 160,80,40,20,15,12,10 meters

Output Power: 3500 W SSB, 2,000 W CW, 1,500 W Continuous

Drive Power: 70-90 watts for 3,500 watts output

Tubes: Svetlana 4CX1600B Tetrodes (2)

T/R Switching: 40 Amp Open Frame Relay

Voltage Requirement: 200/240V, 50/60Hz, 30 Amps

Cabinet Size: 20" w x 19" d x 8" h

Shipping Wt: 110 lbs. UPS three cartons

QRO HF-2500DX

Price: \$2,895 US Dollars FOB Bryan, Ohio USA
Band Coverage: 160,80,40,20,17,15 (12 & 10 export; also usable in U.S.A. with license)
Output Power: 1500 W Continuous Carrier
Drive Power: 50 watts for 1,500 watts output
Tube: Svetlana 4CX300A Tetrode (2)
QSK: Standard Feature
Line Voltage Requirement: 200/240V, 50/60Hz
Cabinet Size: 20" w x 19" d x 8" h
Shipping Wt: 100 lbs. UPS three cartons

FOR MORE DETAILS VISIT OUR HOME PAGE

<http://www.qrotec.com>

LICENSED AMATEURS ONLY...to request free brochures, or further details...Call Toll Free **1-800-956-2721**. Visa/Mastercard credit card or wire transfer payment orders accepted by telephone from 9:00 am to 6:00 pm eastern time Monday thru Friday. *Export orders welcome too!* QRO Amplifiers™ are made in the USA BY HAMS FOR HAMS™ and sold factory direct only.

We occasionally have demonstrator models available at a slight discount. If you are interested, please ask us about them.

QRO HF-3KDX

Price: \$3,295 US Dollars FOB Bryan, Ohio USA
Band Coverage: 160,80,40,20,17,15 (12 & 10 export; also usable in U.S.A. with license)
Output Power: 1500 W Continuous Carrier
Drive Power: 50 watts for 1,500 watts output

WE BUILD THEM LIKE THEY OUGHT TO BE!™

QRO™
TECHNOLOGIES

QRO TECHNOLOGIES, INC.
1117 West High Street
P.O. Box 939
Bryan, Ohio 43506 USA
Tel: (419) 636-2721 • Fax: (419) 636-6039
e-mail: qrotec@bright.net