

RF mixers

Joe Carr explains the importance of choosing the right rf mixer in all applications up to microwave.

My last two articles have developed the basic theory behind RF mixers, and introduced a simple mixer circuits. This month I take a look at higher performance mixer circuitry.

A mosfet double-balanced active mixer¹ is shown in Fig. 1. The dual-gate mixer is ideal for this type of application, but the fets need careful selection.

Instead of the 3N211 mosfets shown, 40673s could be used. These have the advantage of being relatively insensitive to casual electrostatic damage during handling, and are low cost. In addition, in a circuit such as this, the 40673 can provide between 15 and 20dB of conversion gain.

However, this gain is not without cost. The devices are relatively easily overdriven in the presence of large RF input signals. When this occurs the advantages of the device evaporate in increased intermodulation products and degraded noise performance.

The same circuit using 3N211 devices, or equivalent, will produce less conversion gain, of about -5 dB, but better overall performance. With local-oscillator injection of 8V peak-to-peak, and a 10dBm RF input signal, this circuit will exhibit a respectable third-order intercept point of +17dBm.

Bipolar alternative useful to 500MHz

An active double-balanced mixer based on n-p-n bipolar transistors² is shown in Fig. 2. This circuit is usable to frequencies around 500MHz.

Normally, the use of non-IC transistors in a circuit such as this normally requires matching of the transistors for best performance. That need is overcome by using a bit of degenerative feedback for $Tr_{1,2}$ in the form of unbypassed emitter resistors $R_{3,4}$.

The base circuits are driven with the

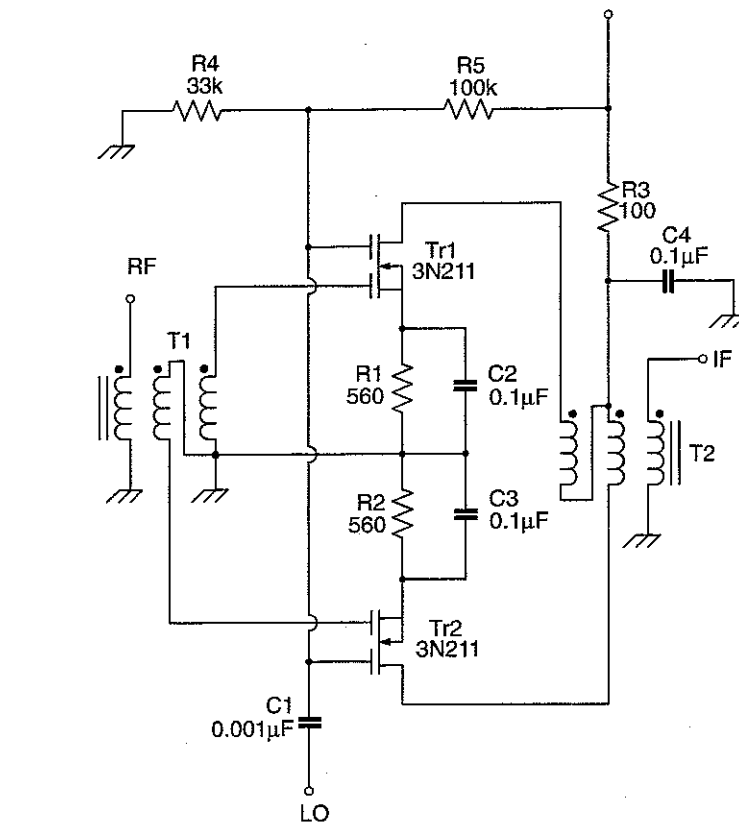


Fig. 1. The dual-gate mixer is useful, but the fets need to be chosen carefully for best performance.

LO signal from a balun transformer, T_1 in a manner similar to the earlier junction-fet circuit. The output transformer, however, is rather interesting.

It consists of four windings, correctly phased, with the IF being taken from the junction of two of the windings. The RF signal is applied to the remaining two windings of the transformer.

This mixer exhibits a third-order intercept of +33dBm, with a conversion loss of 6dB, and only 15 to 17dBm of LO drive power.

Benefits of quad mos and junction fets

Although using bipolar transistors can result in an active double-balanced

mixer with a high third-order intercept point, or TOIP, there is a trend towards using junction and mos fets.

Typical designs use four active devices. This approach is made easier by the fact that many IC makers are producing RF mos and junction fet products that include four matched devices in the same package.

Figure 3 shows a mixer circuit based on the use of four junction-fet devices ($Tr_{1,4}$). These transistors are arranged such that the source terminals of $Tr_{1,2}$ are tied together, as are the source terminals of $Tr_{3,4}$.

The source-pair terminals receive the RF input signal from transformer T_2 . The gates of these transistors are con-

Joseph J. Carr,
MSEE

Fig. 2. Bipolar mixers such as this are useful to 500MHz. Normally, discrete transistors in a circuit like this would need matching for best performance. Adding a little degenerative feedback gets round this problem.

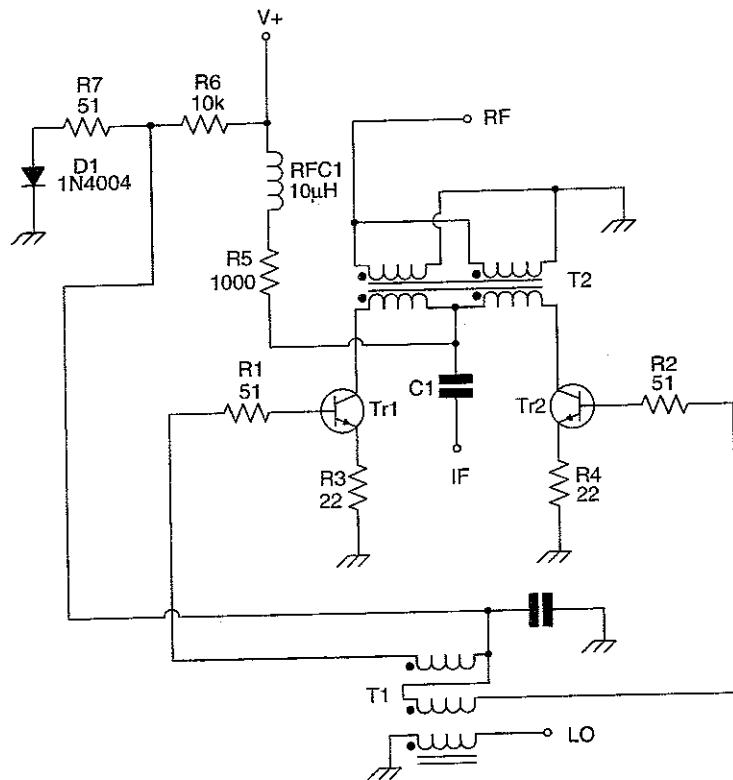


Fig. 3. Quad junction-fet balanced mixer. The fets need to be matched, but packages with four matched fets designed for such applications are readily available.

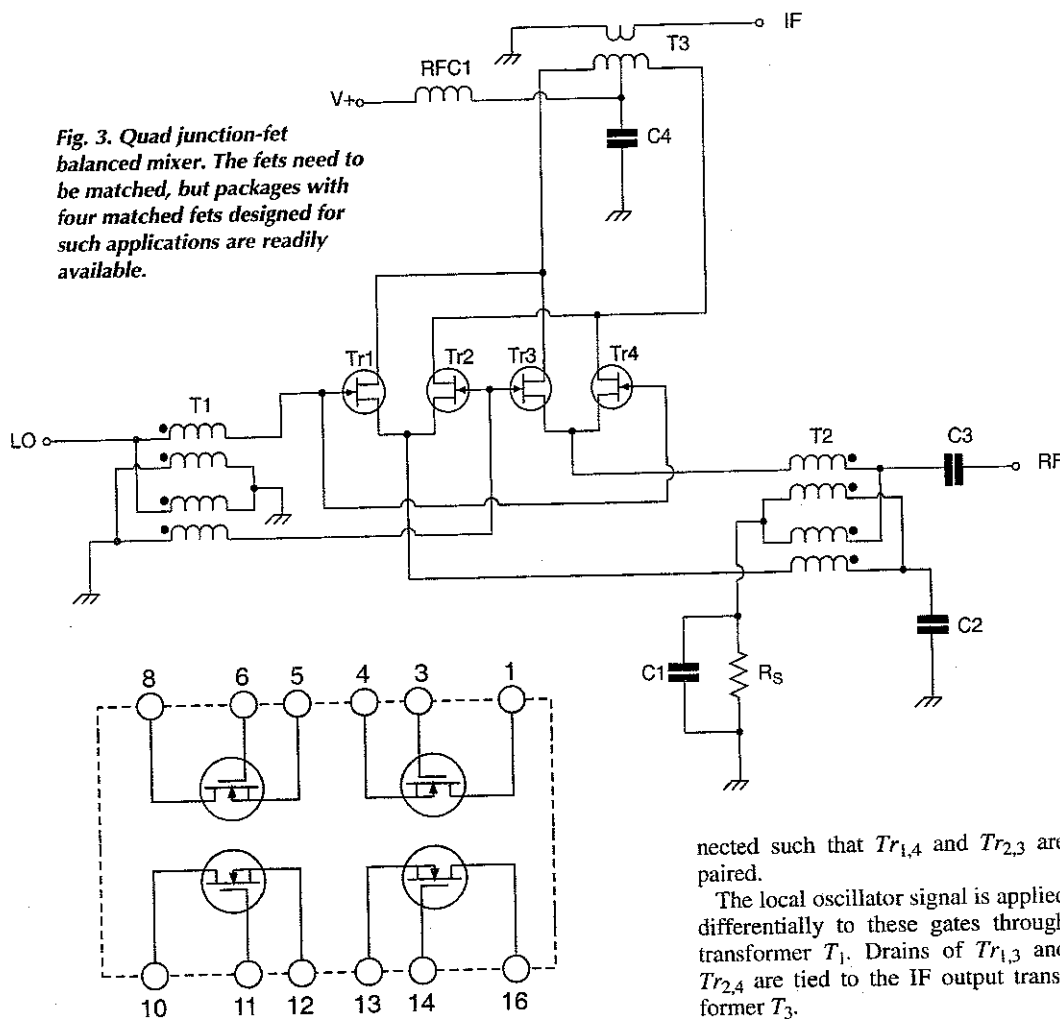


Fig. 4. Siliconix quad MOSFET device contains four fets that can be used independently. When connected as a ring, they form a mixer.

nected such that $Tr_{1,4}$ and $Tr_{2,3}$ are paired.

The local oscillator signal is applied differentially to these gates through transformer T_1 . Drains of $Tr_{1,3}$ and $Tr_{2,4}$ are tied to the IF output transformer T_3 .

There are several quad FET ICs on the market that have found favour as mixers in radio receivers. Siliconix's

SD5000 quad DMOS fet is shown in Fig. 4.

This device contains four fets that can be used independently. When connected as a ring, they form a mixer.

Calogic carries the theme a little further in its *SD8901* DMOS quad fet mixer IC, Fig. 5. The fets, $Tr_{1,4}$, are connected in a ring such that opposite gates are connected together to form two LO ports, LO_1 and LO_2 .

The RF signals are applied differentially across drain-source nodes $Tr_{1,2}$ and $Tr_{3,4}$. Similarly, the IF output is taken from the opposite pair of nodes: $Tr_{1,4}$ and $Tr_{2,3}$. The *SD8901* comes in an eight-pin metal can package.

The circuit for using the *SD8901*, Fig. 6, is representative of this class of mixers. The RF and IF output terminals are through transformers T_1 and T_2 , respectively.

The local-oscillator signal is applied directly to the LO_1 and LO_2 ports, but requires a divide-by-two circuit comprising a J-K flip-flop.

Note that this divider makes the LO signal a square wave rather than a sine wave. An implication of this circuit is that the LO injection frequency must be twice the expected LO frequency.

Gilbert-cell mixers

The Gilbert transconductance cell, Fig. 7, is the basis for a number of IC mixer — for example the *NE602* shown in Fig. 8, and analog multiplier devices like the *LM1496*.

The Gilbert mixer consists of two cross-connected n-p-n pairs fed from a common current source. The RF signal is differentially applied to the transistors that control the apportioning of the current source between the two differential pairs. The local oscillator signal drives the base connections of the differential pairs.

Integrated Gilbert-cell devices such as the Philips/Signetics *NE602* in Fig. 8 are used extensively in low-cost radio receivers. The Gilbert cell is capable of operating to 500MHz. An on-board oscillator can be used to 200MHz.

One problem seen on such devices is that they often trade off dynamic range for higher sensitivity.

Passive double-balanced mixers

The diode double-balanced mixer, Fig. 9, is one of the more popular double-balanced mixer approaches. It has the obvious advantage over active mixers of not requiring a DC power source.

The circuit uses a diode ring, $D_{1,4}$, to perform the switching action. In Fig. 9 only one diode per arm is shown, but some commercial double-balanced mixers use two or more diodes per arm.

This configuration is capable of 30 t

60dB of port-to-port isolation, and is not difficult to apply.

With proper design, it is easy to build passive diode double-balanced mixers with frequency responses from 1 to 500MHz.

Commercial models that work into the microwave region are not hard to find. Intermediate-frequency outputs of typical diode double-balanced mixers can be DC to about 500MHz.

The diodes used in the ring can be ordinary silicon small-signal diodes such as 1N914 or 1N4148, but these are not as good as hot-carrier Schottky diodes like the 1N5820, 1N5821 and 1N5822.

Whichever diodes you choose though, they should be matched for use in the circuit. Diode differences can degrade a mixer's performance.

The usual approach is to match the diode forward voltage drop at some specified standard current, such as 5 to 10mA, depending on the normal forward current rating of the diode. It is also important to match the junction capacitance of the diodes.

The mixer in Fig. 9 uses two balun transformers, T_1 and T_2 , to couple to the diode ring. The double-balanced nature of this circuit depends on these transformers, and as a result the LO and RF components are suppressed in the IF output.

Diode double-balanced mixers are characterised according to their drive level requirement, which is a function of the number of diodes in each arm of the ring. Typical values of drive required for proper mixing action are

0dBm, +3dBm, +7dBm, +10dBm, +13dBm, +17dBm, +23dBm and +27dBm.

Figure 10 shows the internals of a commercially available passive double-balanced mixer made by Mini-Circuits (PO Box 166, Brooklyn, NY, 11235, USA; Phone 714-934-4500; Web site <http://www.minicircuits.com>). These type no. SBLx and SRAx devices are available in a number of different characteristics, Table 1.

The standard package for SRA/SBL devices is shown in Fig. 11. Non-insulated pins are grounded to the case. Pin-outs for common SRA/SBL devices are shown in Table 2.

The regular SRA/SBL devices use a local-oscillator drive level of +7dBm, and can accommodate RF input levels up to +1dBm. The devices will work at lower drive levels, but performance deteriorates rapidly, so it is not recommended.

Note that the IF output port is split into pins 3 and 4. Some models tie the ports together, but for others an external connection must be provided for the device to work.

The nice thing about this type of commercially available mixer is that the system impedances are already set to 50Ω. Otherwise, impedance matching would be necessary for them to be used in typical RF circuits.

Note, however, that if a circuit or system impedance is other than 50Ω, then a mismatch loss will be seen unless steps are taken to effect an impedance match.

The problem becomes considerably

greater when a mismatch occurs at the IF port of the mixer. The mixer works properly only when it is connected to a matched resistive load. Reactive loads, and mismatched resistive loads deteriorate performance.

Figure 12 shows a circuit using a passive diode double-balanced mixer. The diplexer is a critical component to this type of circuit.

Proper loading

The diplexer is a passive RF circuit that provides frequency selectivity at the

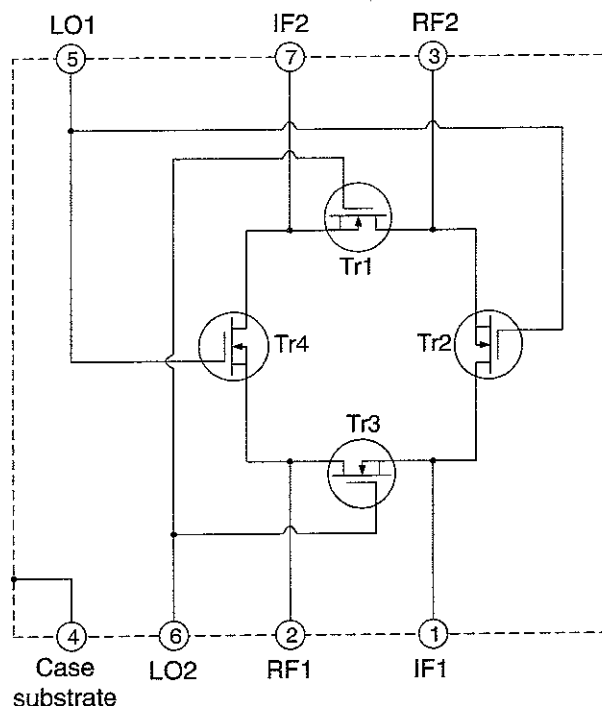


Fig. 5. In Calogic's SD8901 mixer, fets Tr_{1-4} are connected in a ring such that opposite gates are connected together to form two LO ports, LO_1 and LO_2 . RF signals are applied differentially.

Fig. 6. Typical mixer application circuit using the SD8901. The local-oscillator signal is applied directly to the LO_1 and LO_2 ports on pins 5 and 6, but a divide-by-two circuit is needed so the LO signal is a square-wave – not a sine wave.

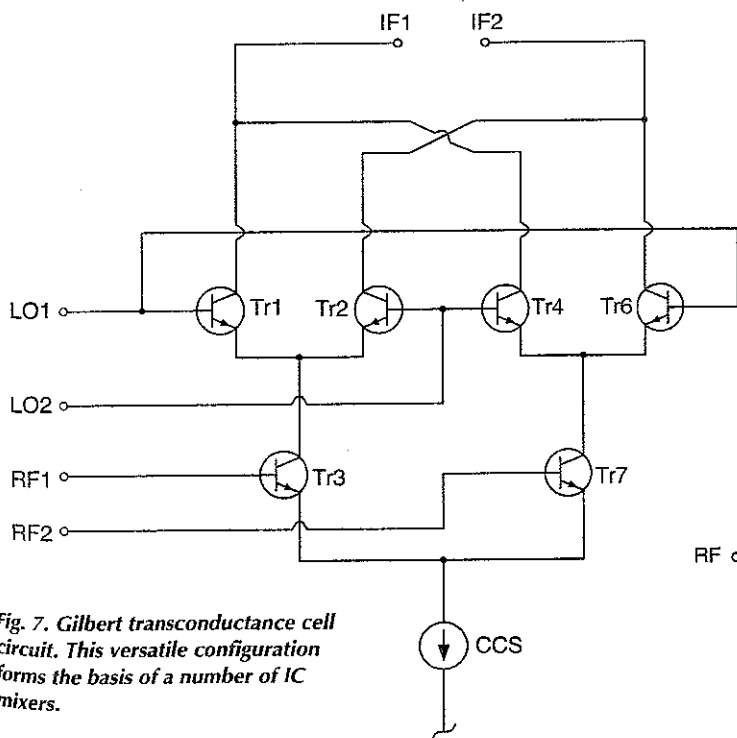
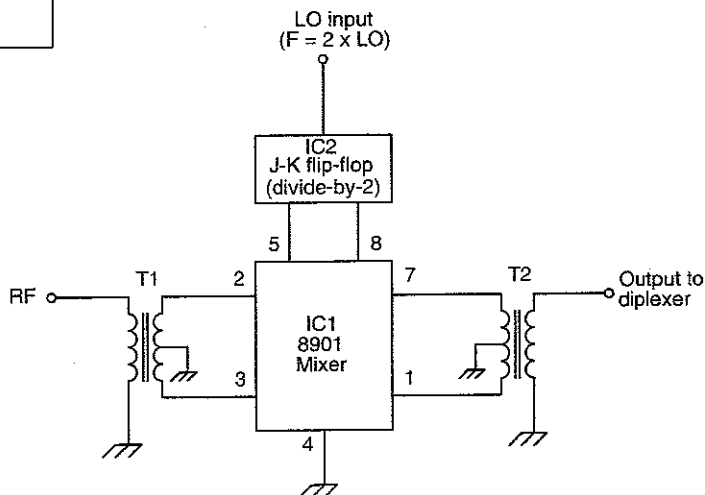


Fig. 7. Gilbert transconductance cell circuit. This versatile configuration forms the basis of a number of IC mixers.

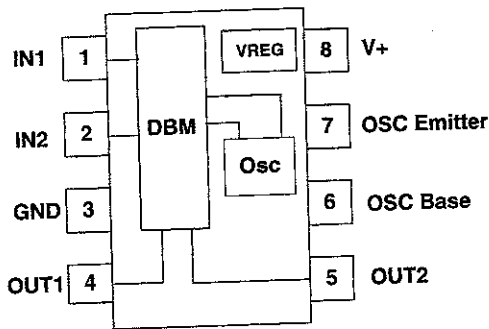


Fig. 8. One IC based on the Gilbert-cell principle is the NE602.

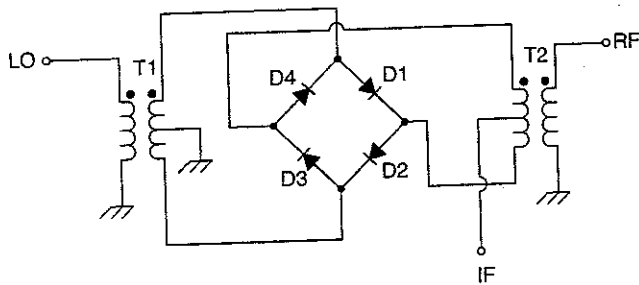


Fig. 9. Involving diodes instead of active switches, the passive double-balanced mixer has the benefit of not needing a DC power source.

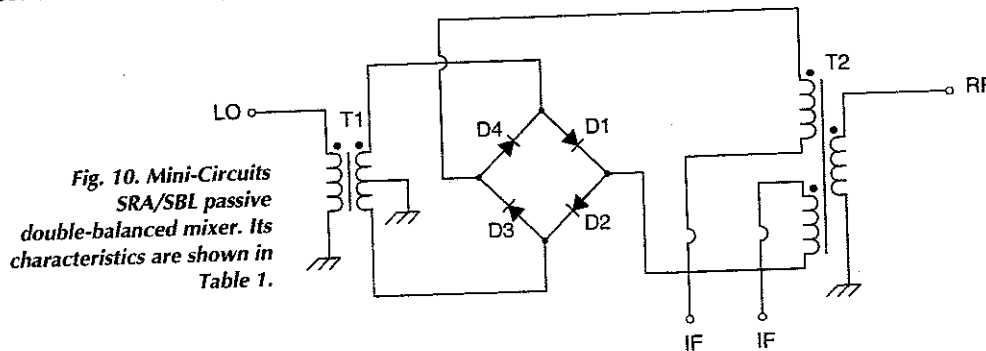


Fig. 10. Mini-Circuits SRA/SBL passive double-balanced mixer. Its characteristics are shown in Table 1.

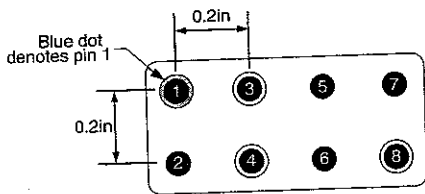


Fig. 11. Package details of the double-balanced mixer in Fig. 10.

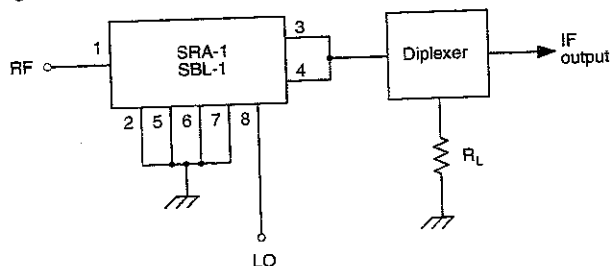


Fig. 12. Terminating a passive double-balanced mixer with a diplexer.

Table 1. Key performance figures for Mini-Circuits SBLx and SRAx passive double-balanced mixers, Fig. 11.

Type No	LO range (MHz)	IF range (MHz)	Mid-band loss (dB)
SRA-1	0.5-500	DC-500	5.5-7.0
SRA-1TX	0.5-500	DC-500	5.5-7.0
SRA-1W	1-750	DC-750	5.5-7.5
SRA-1-1	0.1-500	DC-500	5.5-7.5
SRA-2	1-1000	DC-500	5.5-7.5
SBL-1	1-500	DC-500	5.5-7.0
SBL-1X	10-1000	5-500	5.5-7.5
SBL-1Z	10-1000	DC-500	5.5-7.5
SBL-1-1	0.1-400	DC-400	5.5-7.0
SBL-3	0.025-200	DC-200	5.5-7.5

Table 2. Pin designations of SBLx and SRAx passive double-balanced mixers.

Type No	LO	RF	IF	GND	Case
SRA-1	8	1	3,4	2,5,6,7	2
SRA-1TX	8	1	3,4	2,5,6,7	2
SRA-1W	8	1	3,4	2,5,6,7	2,5,6,7
SRA-1-1	8	1	3,4	2,5,6,7	2
SRA-2	8	3,4	1	2,5,6,7	2,5,6,7
SBL-1	8	1	3,4	2,5,6,7	2
SBL-1X	8	1	3,4	2,5,6,7	2
SBL-1Z	8	1	3,4	2,5,6,7	XX
SBL-1-1	8	1	3,4	2,5,6,7	XX
SBL-3	8	1	3,4	2,5,6,7	XX

binates two frequencies, F_1 and F_2 , to produce an output spectrum of $mF_1 \pm nF_2$, where m and n are integers representing the fundamental and harmonics of the two frequencies.

In some cases, you will only be interested in the difference frequency, so you will want to use the low-pass output of the diplexer, Fig. 14a). The high-pass output is terminated in matched load so that signal transmitted through the high-pass filter is fully absorbed in the load.

The exact opposite situation is shown in Fig. 14b). Here we are interested in the sum frequency, so the high-pass output port of the diplexer is used, and low-pass output port is terminated in resistive load. In this case, the signal passed through the low-pass filter section will be absorbed by the load.

Bandpass diplexers

Figures 15 and 16 show two different bandpass diplexer circuits common used at the outputs of mixers. The circuits use a bandpass filter approach rather than two separate filters.

Figure 15 represents a π -network approach, while the version in Fig. 16 is an L-network. In both cases,

$$Q = \frac{f_o}{BW_{3dB}}$$

and,

$$\omega = 2\pi f_o$$

output, while looking like a constant resistive impedance at its input terminal.

Figure 13 shows a generalisation of the diplexer. It consists of a high-pass filter and a low-pass filter that share a common input line, and are balanced to present a constant input impedance.

With appropriate design, the diplexer will not exhibit any reactance reflected back to the input terminal – eliminating the reflections and voltage/standing-wave ratio problem. Yet, at the same time it separates the high and low frequency components into two separate signal channels.

The idea is to forward the desired frequency to the output and absorb the unwanted frequency in a dummy load.

Figure 14 shows the two cases. In each case, a mixer nonlinearly com-

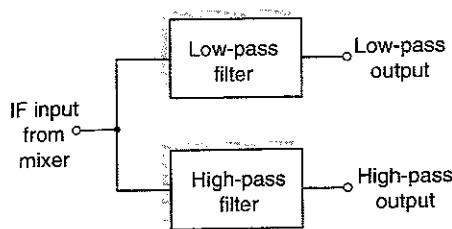


Fig. 13. A passive diplexer following the mixer provides selectivity while looking like a constant resistive impedance at its input terminals.

where f_0 is the centre frequency of the passband in hertz, BW_{3dB} is the desired bandwidth in hertz and Q is the relative bandwidth.

For the circuit of Fig. 15,

$$L_2 = \frac{R_o Q}{\omega}$$

$$L_1 = \frac{R_o}{\omega Q}$$

$$C_2 = \frac{1}{R_o Q \omega}$$

$$C_1 = \frac{Q}{\omega R_o}$$

And for the circuit of Fig. 16,

$$L_2 = \frac{R_o Q}{\omega}$$

$$L_1 = \frac{R_o}{\omega Q}$$

$$C_1 = \frac{1}{L_1 \omega^2}$$

$$C_2 = \frac{1}{L_2 \omega^2}$$

A dual double-balanced mixer

The normal passive diode mixer provides relatively high third-order intercept and -1dB compression points. It also provides a high degree of port-to-port isolation. Because of the switching action of the diodes in the ring, they are shut off at the instances where they would feed through the other ports.

But where an even higher degree of performance is needed, designers sometimes opt for the dual double-balanced mixer as shown in Fig. 17. The -1dB compression point is usually ≤ 4 dB.

Image-reject mixers

In cases where very good image rejection performance is needed in a receiver, a circuit such as Fig. 18 can be used. This circuit uses a pair of passive double-balanced mixers, a 0° power splitter and two 90° power splitters to form an image reject mixer.

The local oscillator ports of mixer-1 and mixer-2 are driven in-phase from a master local-oscillator source. The RF input, however, is divided into quadrature signals and applied to the respective RF inputs of the two mixers.

The IF outputs of the mixers are then recombined in another quadrature splitter, to form separate USB and LSB IF outputs.

VHF/UHF microwave mixers

When the frequencies used for LO, RF and IF begin to reach into the VHF and above region, the design approaches change a bit.

Figure 19 shows a simple single diode unbalanced mixer. Variants of this circuit have been used in UHF television and other types of receivers. The circuit is enclosed in a shielded space in which a strip inductor L_1 and variable capacitor C_1 form a resonant circuit.

The LO and RF signals are applied to the mixer through coupling loops to L_1 . A UHF signal diode is connected to L_1 at a point that matches its impedance.

External to the mixer chamber, an IF filter is used to select the mixer prod-

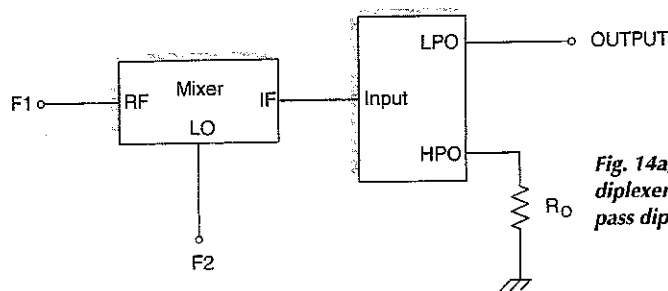


Fig. 14a) Low-pass diplexer; b) high-pass diplexer.

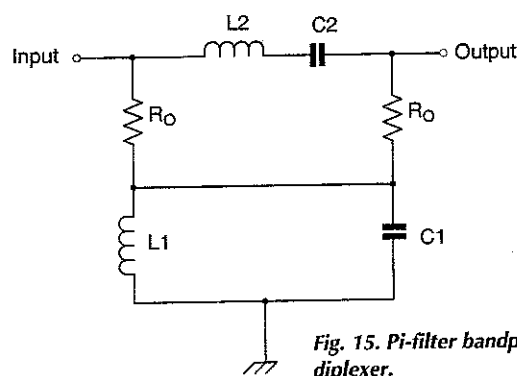
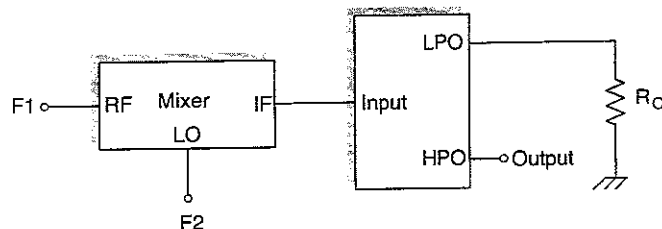


Fig. 15. Pi-filter bandpass diplexer.

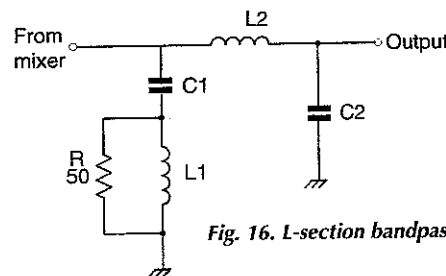


Fig. 16. L-section bandpass diplexer.

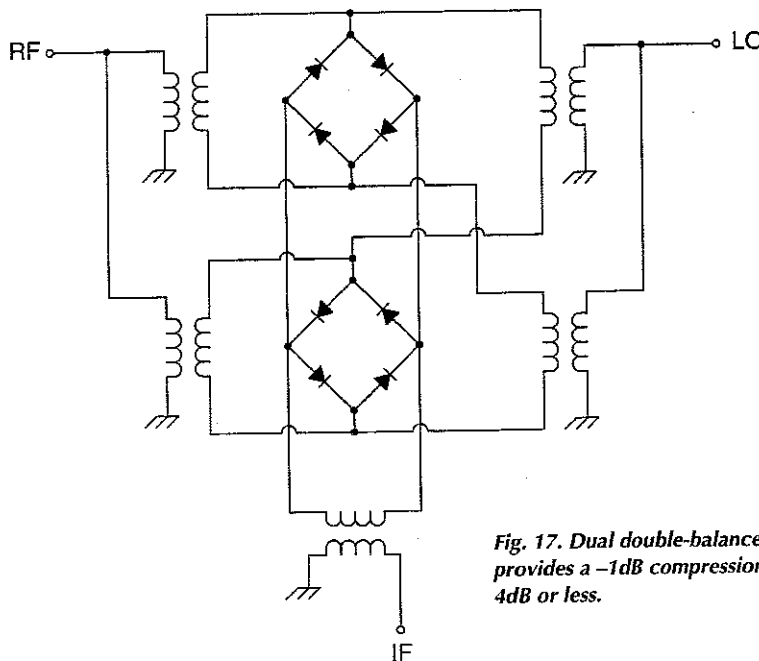


Fig. 17. Dual double-balanced mixer provides a -1dB compression point of 4dB or less.

to
F1
ep-
nar-
ter-
so
out-
The
n a
tted
ully

own
d in
pass
and
in a
gnal
sec-

erent
only
these
each,

work
g. 16

uct desired for the IF section of the particular receiver.

A single-balanced mixer is shown in Fig. 20. This mixer circuit uses two diodes, D_1 and D_2 , connected together, and also to the ends of a half-wavelength 100Ω transmission line. The LO signal is applied to D_2 and one end of the transmission line. IF and RF filters

are used to couple to the RF and IF ports.

These mixers suffer from RF and LO components appearing in the output. Figure 21 shows an improved version that will solve the problem. It is used in the UHF and microwave regions.

The LO and RF input signals are applied to two separate ports of a

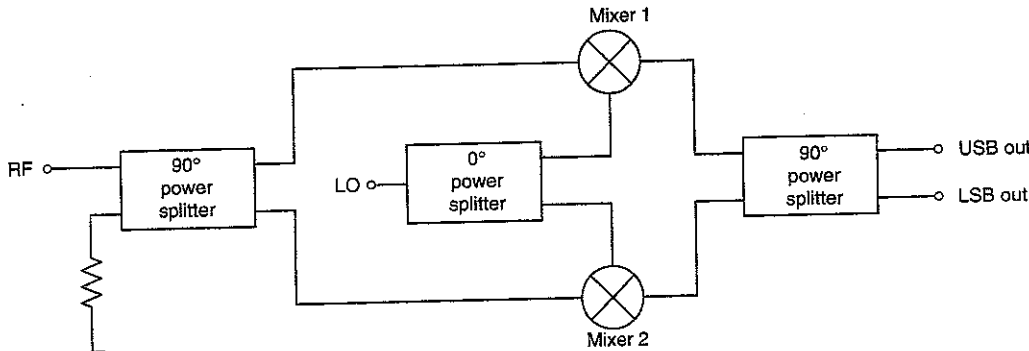


Fig. 18. Image-rejection is improved by using two passive double-balanced mixers together with power splitters.

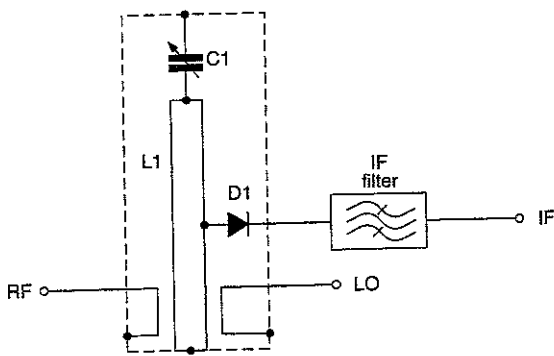


Fig. 19. Simple single-ended diode mixer for VHF/UHF.


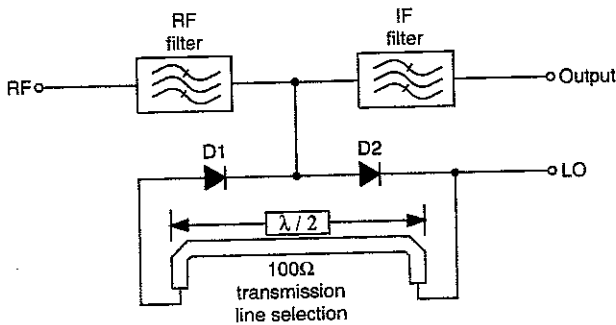


Fig. 20. Such UHF single-balanced mixers suffer from RF and LO components appearing in the output.

Fig. 21. Microwave mixer is an improvement over the single-balanced mixer of Fig. 20, significantly reducing RF and LO components in the output.

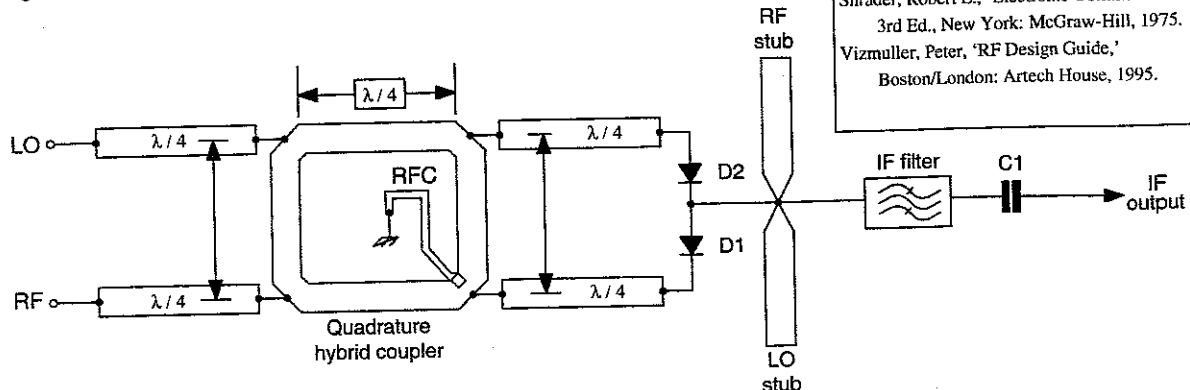

quadrature hybrid coupler. The input and output filtering are made using printed-circuit-board transmission lines.

Each of the lines is a quarter wavelength, although the actual physical lengths must be shortened by the velocity factor of the printed circuit board being used. A printed circuit RF choke is used to provide a return connection for the diodes.

Note the RF and LO stubs at the output of the mixer, prior to the input of the IF filter. These stubs are used to suppress RL and LO components that pass through the mixer.

References

1. DeMaw, D. and G. Collins, 'Modern Receiver Mixers for High Dynamic Range', *QST*, May 1981; Newington, CT, USA: ARRL.
2. Rohde, U., 'Key Components of Modern Receiver Design,' Pt 1, *QST*, May 1994. Newington, CT, USA:ARRL, pp. 29-32.

Need more information?

Carr, Joseph J., 'Microwave and Wireless Communications Technology,' Boston: Newnes 1997.

Carr, Joseph J., 'Secrets of RF Circuit Design,' 2nd edition, New York, McGraw-Hill 1996.

Gilbert, B., 'Demystifying the Mixer,' self-publish monograph, 1994.

Hagen, Jon B., 'Radio-Frequency Electronics: Circuits and Applications,' Cambridge UK, Cambridge Univ. Press, 1996.

Hardy, James, 'High Frequency Circuit Design,' Reston, VA: Reston Publishing Co. (a division of Prentice-Hall) 1979.

Hawker, P. (ed), 'Super-Linear HF Receiver Front Ends,' Technical Topics, *Radio Communication*, Sep 1993, pp. 54-56.

Hayward, W., 'Introduction to Radio Frequency Design,' (Newington, CT: ARRL, 1994).

Horowitz P. and Hill, W., 'The Art of Electronics' 2nd ed, New York: Cambridge University Press, 1989.

Joshi, S., 'Taking the Mystery Out of Double-Balanced Mixers,' *QST*, Dec 1993, pp. 32-34

Kinley, R. Harold, 'Standard Radio Communications Manual: With Instrumentation and Testing Techniques,' Englewood Cliffs, NJ: Prentice Hall, 1985.

Laverghetta, Thomas S., 'Practical Microwaves,' Indianapolis, IN: Howard W. Sams, 1984.

Liao, Samuel Y., 'Microwave Devices & Circuits' Englewood Cliffs, NJ: Prentice-Hall, 1990.

Makhinson, J., 'High Dynamic Range MF/HF Receiver Front End,' *QST*, Feb. 1993, pp. 21-28. Also see Feedback, *QST*, Jun 1993, p 73.

Rohde U., Whitaker, J. and Bucher, T., 'Communications Receivers,' 2nd Ed., New York: McGraw-Hill Book Co, 1988.

Rohde U. and Bucher, T., 'Communications Receivers: Principles and Design,' New York: McGraw-Hill Book Co, 1988.

Rohde, U., 'Key Components of Modern Receiver Design,' Pt 2, *QST*, June 1994, Newington, USA: ARRL, pp. 27-31.

Rohde, U., 'Key Components of Modern Receiver Design,' Pt 3, *QST*, July 1994, Newington, USA: ARRL, pp. 42-45.

Rohde, U., 'Testing and Calculating Intermodulation Distortion in Receivers,' *Q* July 1994, Newington, CT, USA:ARRL, pp 3-4.

Sabin, Williams (1970). 'The Solid-State Receiver' *QST*, May 1970; Newington, CT, USA: AR pp. 35-43.

Sabin, William E., and Schoenike, Edgar O., ed 'HF Radio Systems & Circuits,' 2nd Ed., Atlanta: Noble Publishing, 1998.

Shrader, Robert L., 'Electronic Communication,' 3rd Ed., New York: McGraw-Hill, 1975.

Vizmler, Peter, 'RF Design Guide,' Boston/London: Artech House, 1995.