

# 12-bit analogue i/o via LPT

Although simple, Yongping Xia's LPT analogue interface resolves to 12 bits.

Equipped with a-to-d and d-to-a converters, a pc can perform many measurement and control functions. Figure 1 shows an easy way of providing 12-bit a-to-d and d-to-a conversion. Driven by the software below, the circuit interfaces with the pc through its printer port.

The MAX176 is a complete serial 12-bit a-to-d converter with a built-in track/hold circuit and a voltage reference. Two signals – clock and convert start – are needed to drive the chip. Once started, the a-to-d conversion result is sent out through the DATA pin in two's complement, high-to-low serial order. Analogue input is buffered by IC<sub>B</sub> with range of -5V to +5V. The MAX176 needs +5V and -15V power supplies and provides a -5V reference output.

The MAX543 is a 12-bit serial d-to-a converter. Its current output is converted to voltage by IC<sub>1A</sub>. Required -5V reference is provided by a MAX176. Resistors R<sub>1,4</sub> adjust the d-to-a converter offset and gain respectively. The d-to-a converter's output range is also -5V to +5V.

The a-to-d and d-to-a conversion procedures shown are in C. In this application, two printer port addresses (0x37c and 0x37d) are used. One is for output and the other input. Note that the base address may differ between computers. You should find details in your user guide.

The d-to-a conversion procedure converts 12-bit data in serial order and sends it to MAX543 through the printer port pin 5. Conversion data is stored in 'data out'. An output register named 'out' is used to map the base address printer port. The a-to-d conversion procedure generates

MAX176 required CL(oc)K and CONV(ersion start) signals through pins 2 and 3 of the printer port, reads serial data via printer port pin 15, and returns the reorganised a-to-d conversion result.

These procedures can be included in any C-based application program. If an a-to-d conversion is needed, call the a-to-d procedure and it will return the result. If a d-to-a conversion is required, simply call the d-to-a procedure and pass the data to the procedure. Conversion time depends on the type of pc is used. It takes around 75µs for a-to-d and 68µs for d-to-a on a 50MHz 486 machine.

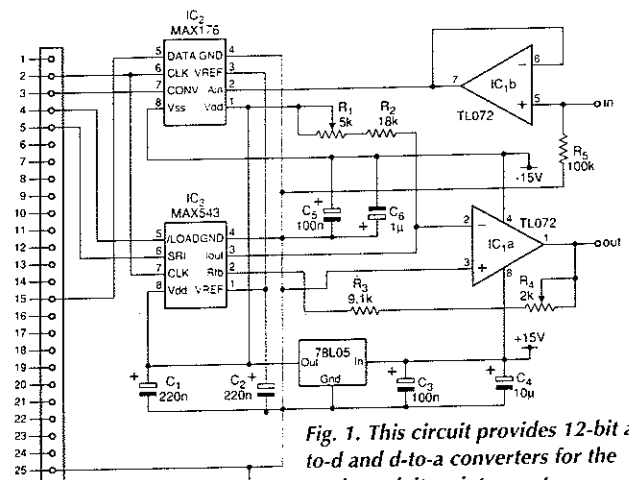


Fig. 1. This circuit provides 12-bit a-to-d and d-to-a converters for the pc through its printer port.

**Assembly language for reading and writing the analogue data converters via the pc's LPT port.**

```
#include <stdio.h>
#include <dos.h>
#include <conio.h>
#define OUT_PORT 0x37c /* base address */
#define IN_PORT 0x37d /* base address + 1 */
#define CLOCK_HIGH 0x01 /* set clock bit high */
#define CLOCK_LOW 0x0e /* set clock bit low */
#define CONVST_HIGH 0x02 /* set start conversion bit high */
#define CONVST_LOW 0xf /* set start conversion bit low */
#define LOAD_HIGH 0x04 /* set load bit high */
#define LOAD_LOW 0xb /* set load bit low */
#define DAC_HIGH 0x08 /* set data out bit high */
#define DAC_LOW 0xf /* set data out bit low */
void dac(int data out);
int adc(void);

/* D-to-A conversion procedure */
void dac(int data out)
{
    int i, out;
    out = 0x04; /* set DAC's LOAD to be high */
    for (j=0; j<12; j++) /* send out 12-bit DAC data */
    {
        if (data out < 0x800) /* if bit 11 is low, */
        {
            out = out & DAC_LOW; /* set output bit = 0 and */
            data out *= 2; /* double DAC data */
        }
        else /* if bit 11 is high, */
        {
            out = out | DAC_HIGH; /* set output bit = 1 and */
            data out = (data out - 0x800) * 2; /* double DAC data after set */
        }
        /* bit 11 to be 0 */
        outportb(OUT_PORT, out); /* send out */
        out = out | CLOCK_HIGH; /* turn CLOCK high */
        outportb(OUT_PORT, out); /* send out */
        out = out & CLOCK_LOW; /* turn CLOCK low */
        outportb(OUT_PORT, out); /* send out */
    }
}
```

```
out = out & LOAD_LOW; /* turn LOAD low */
outportb(OUT_PORT, out); /* send out */
out = out | LOAD_HIGH; /* turn LOAD high */
outportb(OUT_PORT, out); /* send out */
}

/* A-to-D conversion procedure */
int adc(void)
{
    int i, data, out;
    data=0; /* clean data */
    out = 0x04 | CLOCK_HIGH; /* set CLOCK and DAC's LOAD high */
    outportb(OUT_PORT, out); /* send out */
    out = out & CLOCK_LOW; /* turn CLOCK low */
    outportb(OUT_PORT, out); /* send out */
    out = out | CLOCK_HIGH; /* turn CLOCK high */
    outportb(OUT_PORT, out); /* send out */
    out = out | CONVST_HIGH; /* turn A/D CONVERT START high */
    outportb(OUT_PORT, out); /* send out */
    out = out & CLOCK_LOW; /* turn CLOCK low */
    outportb(OUT_PORT, out); /* send out */
    out = out & CONVST_LOW; /* turn A/D CONVERT START low */
    outportb(OUT_PORT, out); /* send out */
    out = out | CLOCK_HIGH; /* turn CLOCK high */
    outportb(OUT_PORT, out); /* send out */
    out = out & CLOCK_LOW; /* turn CLOCK low */
    outportb(OUT_PORT, out); /* send out */
    for (i=0; i<12; i++) /* get 12-bit conversion data */
    {
        out = out | CLOCK_HIGH; /* CLOCK high */
        outportb(OUT_PORT, out); /* send out */
        data = data * 2 + (inportb(IN_PORT & 0x08) / 8); /* update */
        out = out & CLOCK_LOW; /* CLOCK low */
        outportb(OUT_PORT, out); /* send out */
    }
    return (data); /* return A/D conversion result */
}

main()
{
    /* your application */
}
```