

£100 WINNER

Analogue-to-printer port interface

Costing much less than an a-to-d card, a pair of analogue multiplexers and an a-to-d converter will connect up to 256 analogue inputs to any pc with a printer port.

A matrix formed by the analogue inputs is controlled in X and Y directions by the two 4067B multiplexers, in turn controlled by code from the computer. Firstly, the IC₂ multiplexer connects one end of the selected X input to ground, IC₁ connecting the other end to the input of the TLC548 a-to-d converter, which sends it in the form of serial binary code to the pc. Other inputs on the same Y coordinate are not connected to ground and do not affect the selected input.

First four bits of address 378₁₆ control IC₁, the last four being for IC₂. For example, 00000000 selects X0Y0 and 00000001 selects X1Y0. On address 379₁₆, the multiplexer transmits the binary back to the computer; 37A₁₆ controls the clock and clears the converter.


Toh Yue Khing
Singapore

Qbasic listing for controlling the printer port analogue capture system.

```

CLS
DO
x=0
y=0
FOR x = 0 to 15
LOCATE 1,4*x+5
PRINTx
FOR y = 0 TO 15
PRINT y
LOCATE 21, 21
port=y+x* 16
OUT &H378, port      'sent address to
                        analog multiplexer
'code for getting data for ADC
OUT &H37A, 1           'clear the chip data
OUT &H37A, 3           'sent a clock pulse
OUT &H37A, 2
a = INP(&H379) AND 8   'get the first bit
a=a* 16
OUT &H37A, 3
OUT &H37A, 2
b = INP(&H379) AND 8   'get the second bit
b=b*8
a=a+b
OUT &H37A, 3
OUT &H37A, 2
b = INP(&H379) AND 8   'get the third bit
b=b*4
a=a+b
OUT &H37A, 3
OUT &H37A, 2
b=INP(&H379) AND8   'get the four bit
b=b*16
a=a+b
OUT &H37A, 3           'compute the result
OUT &H37A, 2
b = INP(&H379) AND 8   'get the fifth bit
b=b/2
a=a+b
OUT &H37A, 3
OUT &H37A, 2
b = INP(&H379) AND 8   'get the six bit
b=b/4
a=a+b
OUT &H37A, 3
OUT &H37A, 2
b = INP(&H379) AND 8   'get the seven bit
b=b/8
a = a + b
OUT &H37A, 3
LOCATE y+2, 4*x+5
PRINT CHR$(255); CHR$(255),
CHR$(255);           CHR$(255) 'clear
the previous number
LOCATE y+2, 4 * x+ 5
PRINT INT(a/255 * 5 * 10) / 10 'round off to 1
decimal place
NEXT y
NEXT x
LOOP UNTIL INKEY$ = CHR$(27)  'loop
until "ESC" key is pressed

```

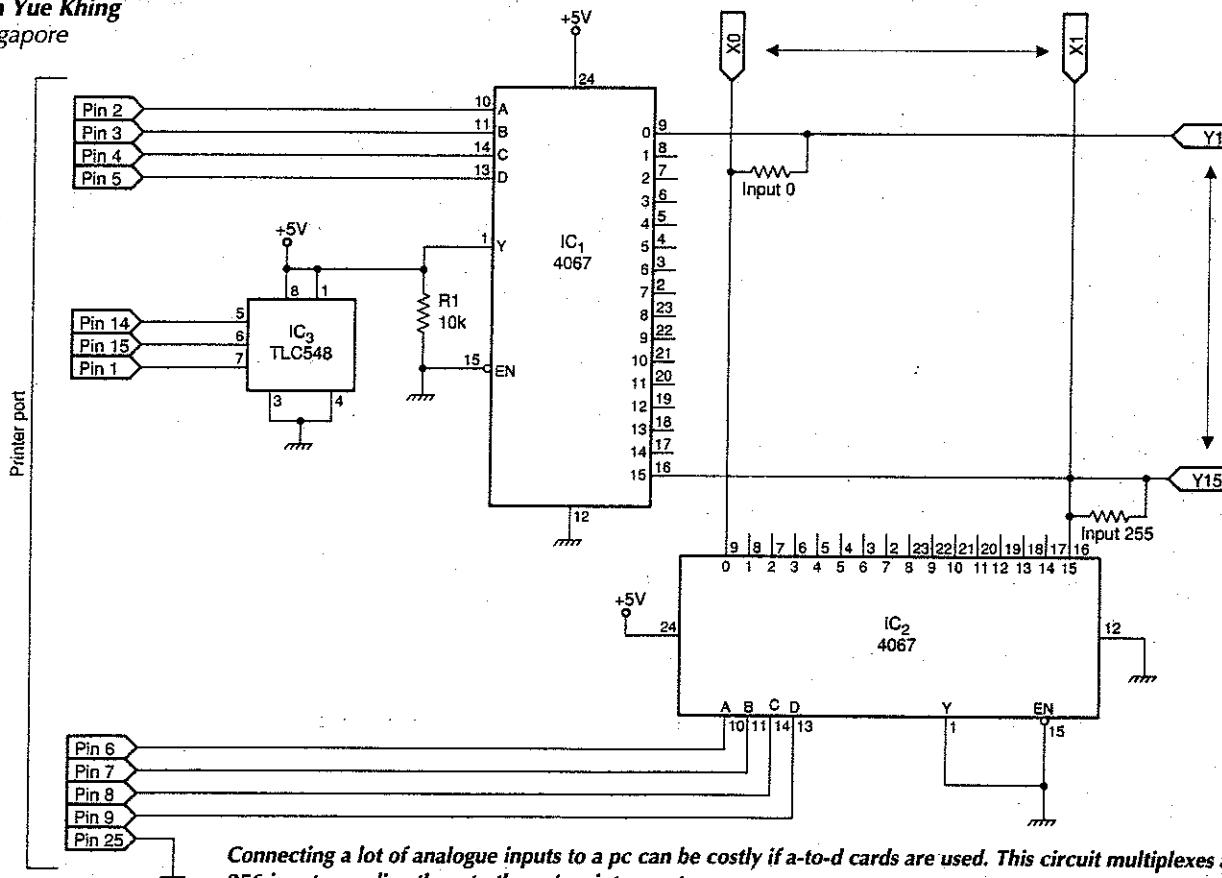

Connecting a lot of analogue inputs to a pc can be costly if a-to-d cards are used. This circuit multiplexes and converts 256 inputs, sending them to the pc's printer port.