

# Eprom programmer/copier


Having previously used a pc-based method of programming eeproms, I produced this device to free the pc for other work.

A donor microwire memory device is read by the circuit one byte at a time, the information then being programmed into a recipient, which is automatically erased when the process starts; all locations are written. Furthermore, instead of the manual input needed by the pc programmer, this only needs one four-second switch operation. You do, of course, have to make one donor using the pc or some other method; donors can be kept to guard against hiccups of the hard disk. Pressing the switch starts the programming operation, which halts on completion; led 1 flashes while programming is in operation and led 2 glows on completion; opening the switch primes the PIC16C84 for another run, but switch the power off when changing the recipient chip.

Opcode is shown here, but I can supply a 3.5in disk; my e-mail address is brian@briano.demon.co.uk or you can use ordinary post.

**Brian Olliver**  
12, Fountain Drive  
St Georges  
Telford TF2 9DP

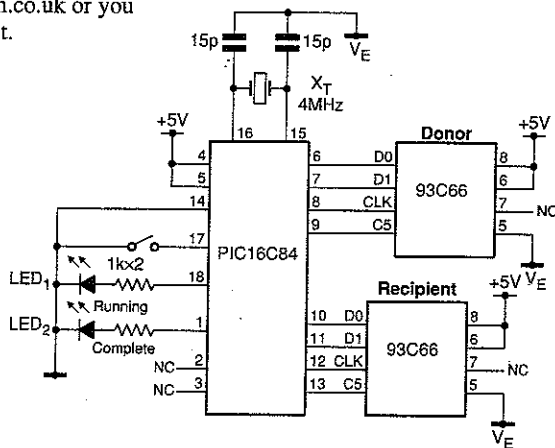Instead of typing up a pc, use this programmer with donor and recipient devices to program eeproms.



```
:100000004A280028861086110611000086158614DD
:100010000000061500000000061100348612861349
:100020000613000086178616000006170000000061
:10003000061300348A1406150000061C8A100611E7
:1000400000348D010830910003108D0D1A200D1021
:100050008A180D14910B252800348A1E3128861623
:100060003228861206170000061300341208910089
:100070008A12901B8A162D20900D910B382800347F
:10008000120891000A10901B0A142D20900D910B5C
:100090004228003401306500850111306600860178
:1000A0000518502885140E20023092000030900070
:1000B000362008309200C0309000362086130000B1
:1000C000B52000308C000220023092008030900079
:1000D000402008309200C089000402021200D089C
:1000E000970021200D089800861183286E30960015
:1000F00000000000000000000000000960B7828BF
:10010000950B762800340E2002309200403090008B
:10011000362008309200C08900036201708900016
:10012000362018089000362086130A309500762075
:100130008C0F6328A728851005156430950076205C
:100140000511643095007620051850289C280E2053
:1001500002309200003090003620083092000030CB
:1001600090003620861300009B280E20023092005B
:100170000030900036200830920080309000362009
:0C018000861300003C309500762008008003B
:00000001FF
```

# Calculator chip as maths coprocessor and display

Using a cheap microcontroller can make digital instruments cost-effective in small numbers, but the cost of displays and their demands on the processor pose a problem.

One solution to both problems is to use the ic and display from a cheap calculator as a combined coprocessor and display controller, all calculation and display functions then being carried out by this purpose-designed processor; the main microcontroller is then

left to pursue its own affairs.

Calculator keypads are normally multiplexed and may be emulated from the microcontroller by monitoring column outputs and pulling the appropriate row input line high or low, depending on the calculator used.

The diagram shows an alternative: two cmos analogue multiplexers, IC<sub>3,4</sub>, will simulate the keypad directly, simplifying the software interface and reducing the number of port


lines used. Only five lines, RB<sub>0,4</sub>, are needed for calculators using the 6 by 4 or 7 by 4 matrix. Since these lines are only used when writing to the coprocessor, they can be multiplexed for other purposes – possibly using the enable pin on IC<sub>3</sub> to disable display writes. An unused column address in IC<sub>3</sub> is otherwise used as a No-op command and each digit or operand entry is achieved by writing one five-byte to the display controller.

As you can see from the diagram, the calculator keypad can be kept as a free control panel by using the spare 4:1 multiplexer in IC<sub>4</sub> and the extra port lines RB<sub>5,6</sub>. Selecting No-op on RB<sub>0,2</sub> and the row address on RB<sub>3,4</sub> allows RB<sub>6</sub> to be monitored for a pulse. If columns rise in sequence, the active key column can be determined from the time delay from the first column at RB<sub>5</sub>, or a priority encoder could be used to indicate a keystroke directly.

A variety of arithmetic functions is possible with eight-digit precision, even from cheap calculators; not only the basic functions, but with a little ingenuity, accumulation, average, delta and many others.

You can measure the mains frequency accurately without long gate times by using a PIC16X in timer mode and the calculator to find the reciprocal. Functions not normally found in commercial counter-timers are percentage or frequency change; these can be performed easily using this method.

**Anthony New Bristol**

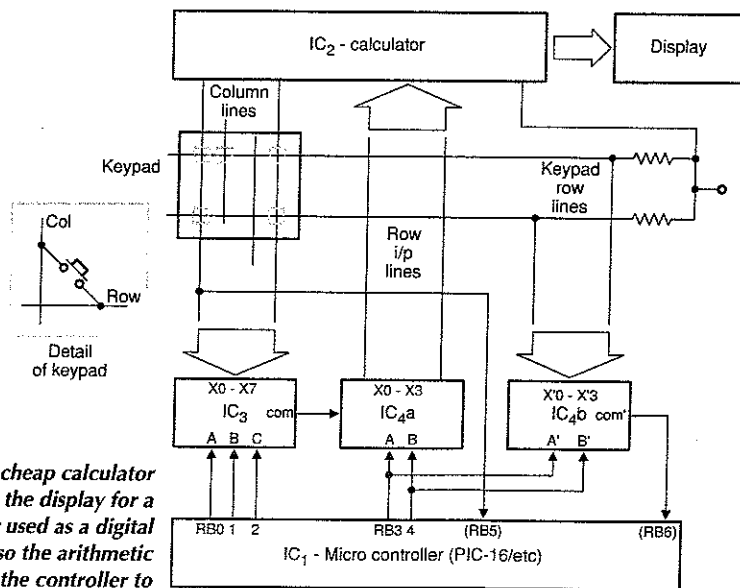

Innards of a cheap calculator provide not only the display for a microcontroller used as a digital instrument, but also the arithmetic functions to free the controller to